
First Name

Last Name

First let
of last na

UW Userid

ECE 327 Midterm

2013t1 (Winter)

Instructions and General Information

- 100 marks total. Time limit: 1 hour, 20 minutes (80 minutes)
- No books, no notes, no computers. Calculators are allowed
- If you need extra paper, request some from a proctor.
- Write neatly. To earn partial credit, you must show the formulas you are using and all of your work.
- **The proctors and instructors will not answer questions, except in cases where an error on the exam is suspected. If you are confused about a question, write down your assumptions or interpretation.**
- **Justifications of answers will be marked according to correctness, clarity, and concision.**

		Total Marks	Approx. Time	Page
Q0	!!Almost Free!!	<input type="text"/>	2	2
Q1	VHDL Semantics	<input type="text"/>	20	15
Q2	Dataflow Diagram and Control Table	<input type="text"/>	20	15
Q3	The Sleet, the Snow, and the Slush	<input type="text"/>	20	15
Q4	State Machines	<input type="text"/>	20	15
Q5	Dataflow Diagram with Memory	<input type="text"/>	20	15
Totals		<input type="text"/>	100	77

Q0 (2 Marks) !!Almost Free!!

(estimated time: 2 minutes)

Q0a (1 Mark) Best part

What is the best part of the course?

Q0b (1 Mark) Most improve

What one thing could be done to most improve the course for the remainder of the term?

Q1 (20 Marks) VHDL Semantics

(estimated time: 15 minutes)

For the VHDL program below, calculate the values for the signals a1, b1, c1, a2, b2, and c2 at 15ns.

NOTES:

1. All of the processes are in the *same architecture*.
2. The signals a1, b1, c1, a2, b2, and c2 are declared to be unsigned(3 downto 0).
3. **For full marks you must justify your answer, using text and/or the waveform diagram. You may, but are not required to, show a delta-cycle simulation.**

```
process begin
  clk1 <= '0';
  wait for 10 ns;
  clk1 <= '1';
  wait for 10 ns;
end process;
```

```
process begin
  a <= to_unsigned( 1, 4 );
  wait for 10 ns;
  a <= to_unsigned( 2, 4 );
  wait for 20 ns;
  a <= to_unsigned( 3, 4 );
  wait for 20 ns;
end process;
```

```
process begin
  b <= to_unsigned( 7, 4 );
  wait until rising_edge(clk1);
  b <= to_unsigned( 8, 4 );
  wait until rising_edge(clk1);
  b <= to_unsigned( 9, 4 );
  wait until rising_edge(clk1);
end process;
```

```
process (clk1) begin
  clk2 <= clk1;
end process;
```

```
process begin
  c <= to_unsigned( 10, 4 );
  wait until rising_edge(clk2);
  c <= to_unsigned( 11, 4 );
  wait until rising_edge(clk2);
  c <= to_unsigned( 12, 4 );
  wait until rising_edge(clk2);
end process;
```

```
process begin
  wait until rising_edge(clk1);
  a1 <= a;
  b1 <= b;
  c1 <= c;
end process;
```

```
process begin
  wait until rising_edge(clk2);
  a2 <= a;
  b2 <= b;
  c2 <= c;
end process;
```



Q2 (20 Marks) Dataflow Diagram and Control Table

(estimated time: 15 minutes)


In this question you will do register allocation and draw the control-table for the dataflow diagram shown below.

NOTES:

- The optimization goal is to *minimize the total number of multiplexers and chip-enables*. More precisely, minimize the sum of the number of flip-flops that need a chip enable, and the number of 2:1 multiplexers for both registers and the subtracter. You may combine 2:1 multiplexers to create larger multiplexers. (e.g., two 2:1 muxes can be combined to create a 3:1 multiplexer.)
- You shall *not* change the allocations that have been done.

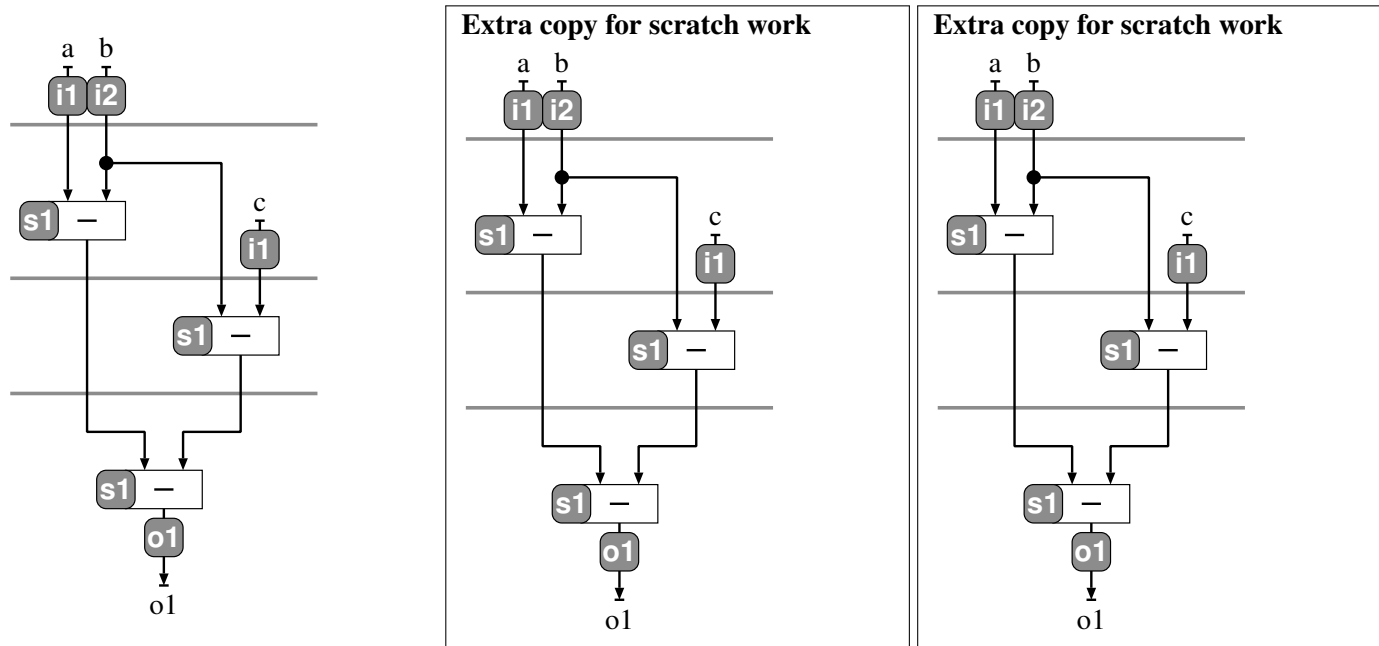Q2a (9 Marks) Register Allocation

Allocate registers for the dataflow diagram.



Q2b (9 Marks) Control Table


Draw the control table for the dataflow diagram.

NOTES:

- Label each row and column of the table clearly.
- The system shall support an *unpredictable number of bubbles* between valid parcels. If you do not know how to support an unpredictable number of bubbles with this system, you may earn *part marks* by writing a \checkmark in the box at the end of this note and answering the question for parcels that *arrive as soon as possible (ASAP)*.

I am answering for ASAP parcels, not an unpredictable number of bubbles.

- Do *not* do don't-care instantiation.

 

Q2c (2 Marks) Analysis

For each register that you used and the subtracter, give the number of 2:1 multiplexers that it needs.

For each register that you used, use a \checkmark in the box for “Yes” or “No” to answer whether it needs a chip-enable signal.

	r1		r2		r3		r4		s1
num 2:1 muxes									
needs chip-enable?	Yes	No	Yes	No	Yes	No	Yes	No	
	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	

Q3 (20 Marks) The Sleet, the Snow, and the Slush

(estimated time: 15 minutes)

Each of the code fragments in Q3a–Q3c is intended to implement the schematic below, such that the behaviour of z with respect to the input signals a , b , and clk is the same in both the VHDL code and the schematic. The behaviour of internal signals does not matter.


NOTES:

1. For each of the code fragments Q3a–Q3c:

- Answer whether the code is *legal*.
- If the code is *illegal*: explain why, and proceed to the next code fragment.
- Answer whether the output z is *correct* with respect to the schematic.
- If the code is *incorrect*: explain why and continue by answering whether the code is synthesizable.
- Answer whether the code is *synthesizable*.
- If the code is *unsynthesizable*: explain why, and proceed to the next code fragment.
- List the signals in the code that are flip-flops.
- Answer whether the code adheres to good coding practices, according to the guidelines for ECE 327.
- If the code does *not follow good coding practices*: explain why.

2. All signals are `std_logic`.

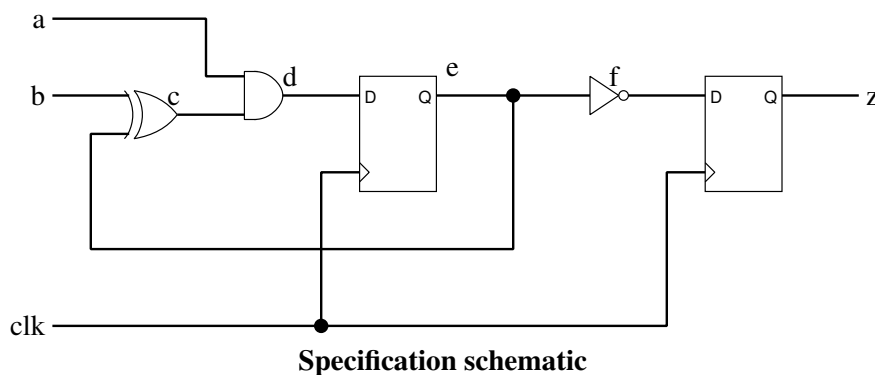3. When listing the flip-flops, list the signals in *alphabetical order*.



Q3a

```
process begin
  wait until rising_edge(clk);
  c <= a;
end process;
```

```
process (c, d ) begin
  if d = '0' then
    e <= '0';
  else
    e <= c;
  end if;
end process;
```

```
d <= b xor e;
```

```
process begin
  wait until rising_edge(clk);
  z <= not e;
end process;
```

	Yes	No
Legal	<input type="checkbox"/>	<input type="checkbox"/>
Correct	<input type="checkbox"/>	<input type="checkbox"/>
Synthesizable	<input type="checkbox"/>	<input type="checkbox"/>
Signals that are flip-flops	<input type="checkbox"/>	
Good Practice	<input type="checkbox"/>	<input type="checkbox"/>

Explanation if illegal or incorrect:

Explanation if unsynthesizable or bad practice:

Q3b

```
process begin
  wait until rising_edge(clk);
  c <= a;
  d <= b;
end process;
```

```
e <= d xor g;
f <= c and e;
```

```
process begin
  wait until rising_edge(clk);
  g <= f;
end process;
```

```
z <= not g;
```

	Yes	No
Legal	<input type="checkbox"/>	<input type="checkbox"/>
Correct	<input type="checkbox"/>	<input type="checkbox"/>
Synthesizable	<input type="checkbox"/>	<input type="checkbox"/>
Signals that are flip-flops	<input type="checkbox"/>	
Good Practice	<input type="checkbox"/>	<input type="checkbox"/>

Explanation if illegal or incorrect:

Explanation if unsynthesizable or bad practice:

Q3c

```
process (clk) begin
  if rising_edge(clk) then
    if a = '0' then
      e <= '0';
    else
      e <= a xor e;
    end if;
  end if;
  z <= not e;
end process;
```

	Yes	No
Legal	<input type="checkbox"/>	<input type="checkbox"/>
Correct	<input type="checkbox"/>	<input type="checkbox"/>
Synthesizable	<input type="checkbox"/>	<input type="checkbox"/>
Signals that are flip-flops	<input type="text"/>	
Good Practice	<input type="checkbox"/>	<input type="checkbox"/>

Explanation if illegal or incorrect:

Explanation if unsynthesizable or bad practice:

Q4 (20 Marks) State Machines

(estimated time: 15 minutes)


Each of the state machines in Q4a–Q4c is intended to count the number of times that $b = '1'$ while $a = '1'$. The behaviour is described precisely in the table below, which defines the action to perform on P in terms of conditions on the inputs a and b :

Input conditions		Action
a	b	
'0'	–	set P to 0
'1'	'0'	no change to P
'1'	'1'	increment P


NOTES:

 1. The *latency* between the inputs a and b and the output P may be *zero or more* clock cycles. The waveforms below illustrate the behaviour with a latency of 0 and 1.
2. When $a = '0'$, the state machine may require multiple clock cycles of $a = '0'$ before the next clock cycle in which $a = '1'$. These clock cycles of $a = '0'$ are called *bubbles*.
3. For each of the state machines Q4a–Q4c, answer whether the state machine is *correct* with respect to the intended behaviour.
4. If the state machine is *correct*, answer what is the *minimum number of bubbles* that the state machine requires in order to work correctly.
5. If the state machine is *incorrect*, explain either how the machine’s behaviour differs from the intended behaviour or how the state machine could be modified to fix the incorrect behaviour.
6. The input a is guaranteed to be $'0'$ for first four clock cycles.


Latency = 0: increment P in same clock cycle as $b = '1'$:



 Latency = 1: increment P in next clock cycle after $b = '1'$:



Q4a

 


Yes No

Machine is correct

If correct: number of bubbles

If incorrect, explanation:

Q4b

 


Yes No

Machine is correct

If correct: number of bubbles

If incorrect, explanation:

Q4c

 

Yes No

Machine is correct

If correct: number of bubbles

If incorrect, explanation:

Q5 (20 Marks) Dataflow Diagram with Memory*(estimated time: 15 minutes)*

Draw a dataflow diagram that implements the specification:

```
M[a] = b;  
M[c] = d;  
z = M[c] + M[c+1];
```

NOTES:

1. It is guaranteed that $a \neq c$.
2. Inputs shall be *registered*
3. Outputs may be *either combinational or registered*
4. Memory has registered inputs and combinational outputs (same as in class)
5. The memory shall be *dual-ported*. If you do not know how to answer the question with dual-ported memory, you may earn *part marks* by writing a \surd in the box at the end of this note and answering the question for *single-ported memory*.

I am answering for *single-ported memory*, not dual-ported memory.

6. Optimization goals in order of decreasing importance:

(a) minimize *latency*

(b) minimize *area*

i. input ports

ii. registers (*excluding* memory)


iii. adders

iv. output ports

(c) minimize *clock period*

7. Input values may be read in any clock cycle, but each input value shall be read exactly once.
8. Optimizations to the pseudocode are allowed, so long as the final values on z and M are correct.

Q5a (15 Marks) Dataflow Diagram

 

Q5b (2 Marks) Bubbles

What is the minimum number of bubbles between valid parcels for your dataflow diagram?

Q5c (3 Marks) Parcel Schedule

Should this system require that parcels arrive as soon as possible (ASAP parcels) or should the system support an unpredictable number of bubbles between parcels? **For full marks, you must justify your answer.**

		Unpredictable
	ASAP	num of bubbles
Parcel schedule	<input type="checkbox"/>	<input type="checkbox"/>

Justification:
