

Low Power RFICs for Transceiver Applications

M. Jamal Deen

Microelectronics Research Laboratory


**Department of Electrical and Computer Engineering,
McMaster University, Hamilton, ON L8S 4K1 Canada
E-mail: jamal@mcmaster.ca**

IEEE Circuits and Systems Society (18th May 2004)

RF & Wideband Projects

- Rizwan Murji – RFICs for wireless applications
- Sasan Naseh – Reliability of RFICs
- Wai Leung Ngan – Mismatch effects on oscillators
- Nabeel Jafferli – Low-voltage, low-power mixers
- Ahmed Fakhr – Low-voltage, micro-power oscillators
- Saman Asgaran – RF noise modeling and RF LNAs
- Samar Abdelsayed – RF PA and integrated antenna
- Munir Eldesouki – RF PA and integrated filter
- Juan Ranuárez – CMOS distributed amplifiers
- Ehab El-Badry – SiGe distributed amplifiers
- Guennadi Kouzaev – Modeling of passives
- Ognian Marinov – Instrumentation ICs


The Wireless Transceiver

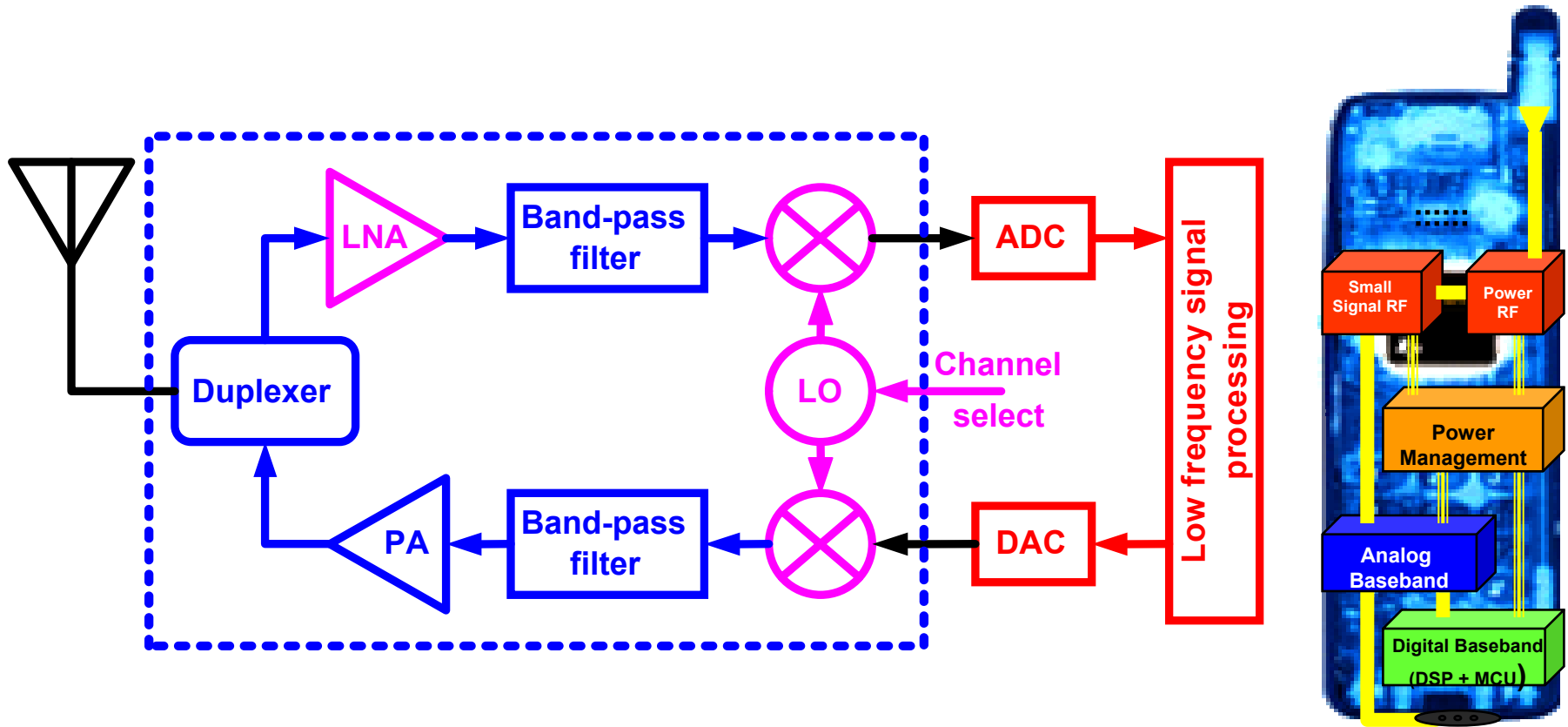

Outline of Talk

- **Mixers**
 - ◆ **Gilbert cell and body-input mixers**
- **Oscillators**
 - ◆ **VCO with AAC and micro-power VCO**
- **Hot-carrier effects on RFICs**
- **Mismatch effects**
- **Subthreshold operation**
- **Conclusions**

RF CMOS Mixer Trends

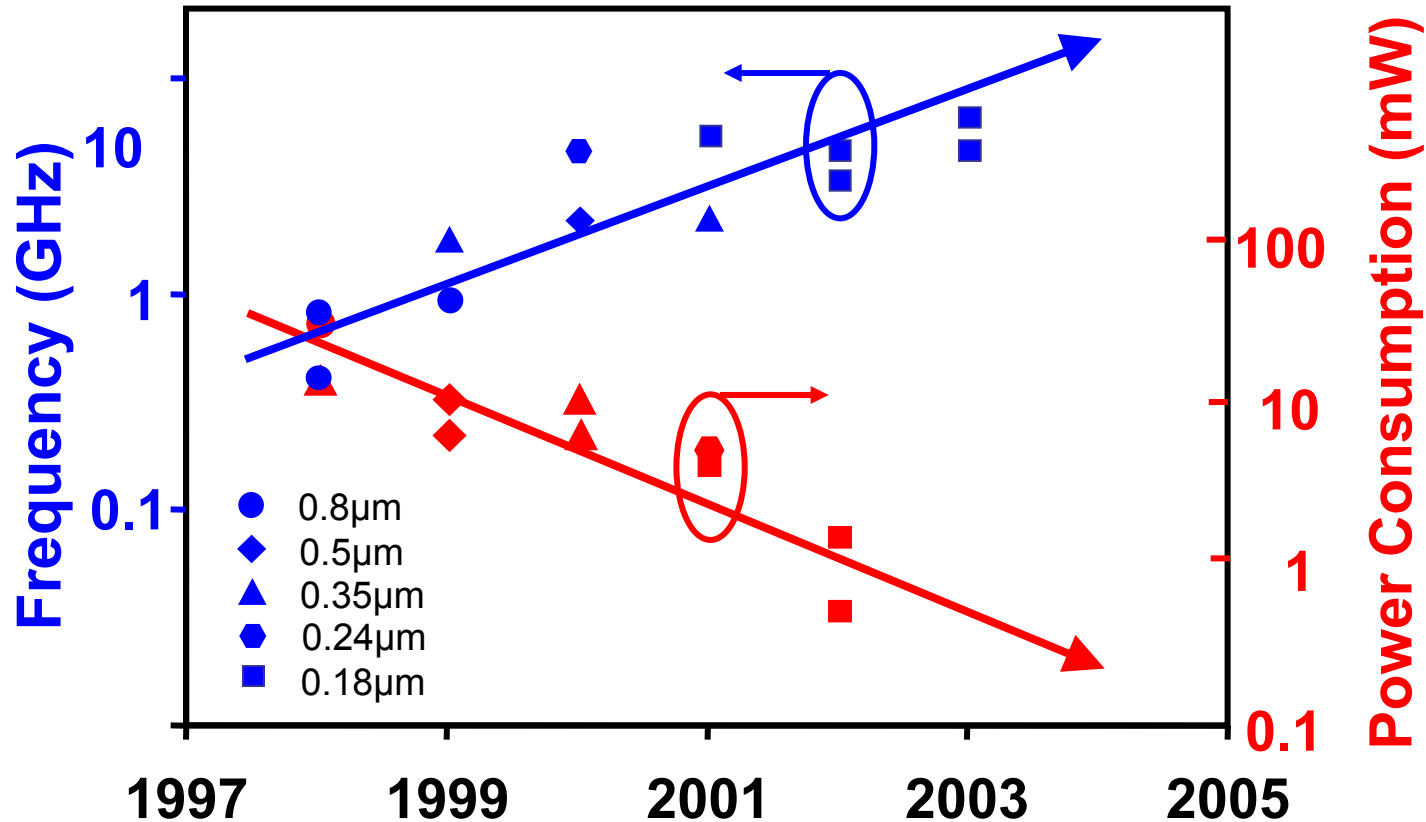

- Frequency and power vs. year of published high-frequency CMOS mixer designs and expected trend

Mixer Characteristics

- Power Consumption

$$V_{DD} \times I_{DD}$$

- Conversion Gain

$$10 \log \left(\frac{P_{out}(\omega = \omega_{IF})}{P_{in}(\omega = \omega_{RF})} \right)$$

- Linearity (IIP3)

- Noise Figure


$$NF = \frac{SNR_{input}}{SNR_{output}}$$

$$FoM = 20 \log(f_{RF}) + CG - NF + IIP3 - 10 \log(P_C)$$



f_{RF} normalized to 1Hz, CG in dB, NF in dB, IIP3 in dBm and P_C normalized to 1W

RF CMOS Mixer

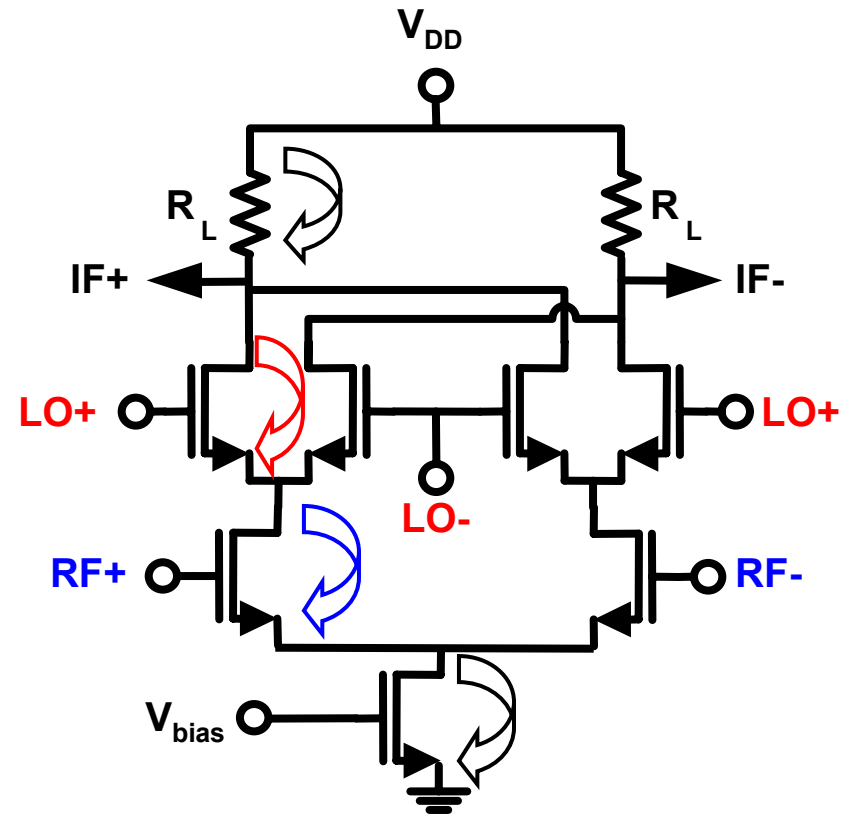- Gilbert-cell mixer introduced in 1968 (with BJTs)
- Most popular mixer circuit
- Low voltage operation issues
 - ◆ stacked transistors
 - ◆ degrades linearity and conversion gain



Gilbert Mixer - g_m Cell Technique

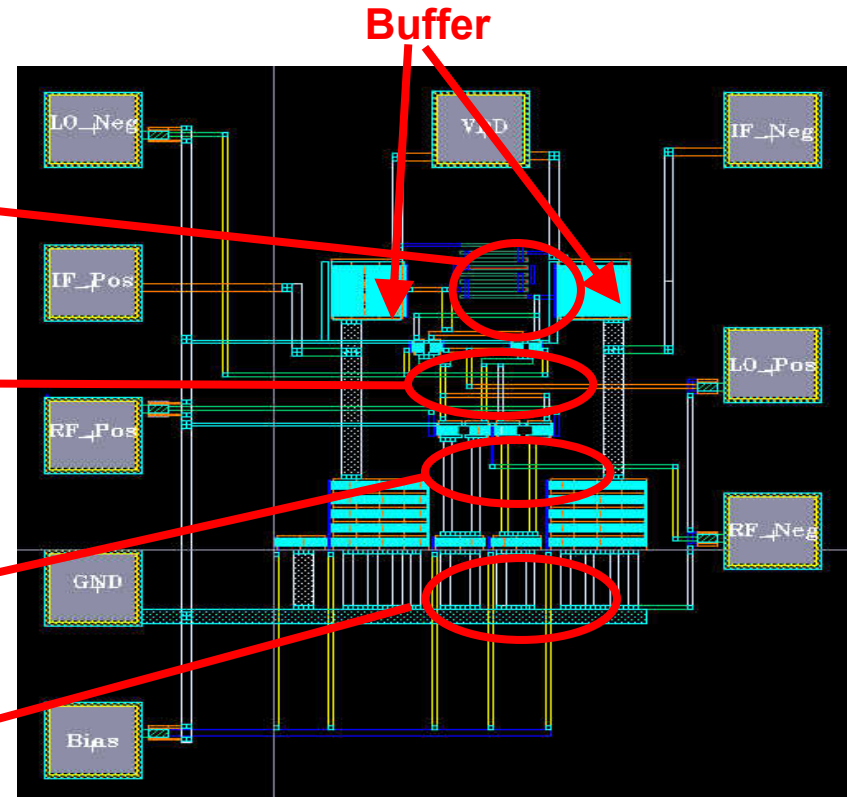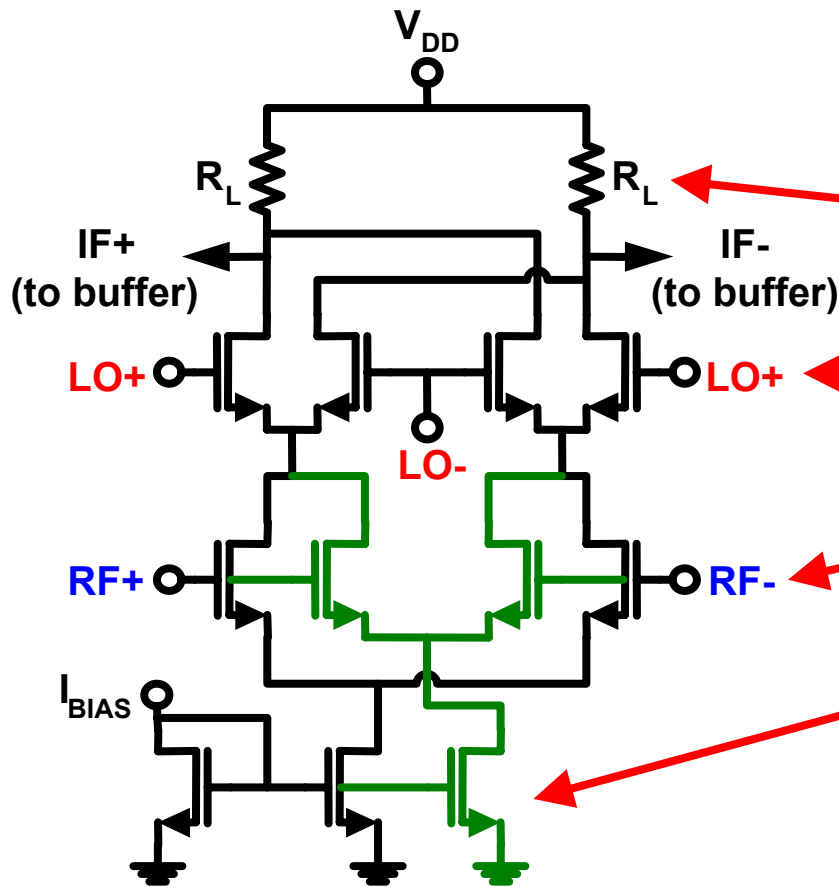


Supply voltage/Power	1.2V/3.95mW	SSB Noise Figure/IIP3	17dB/8dBm
RF Input/Conversion Gain	1.9GHz/-2dB	FoM/Technology	199dB/0.18 μ m

$$FoM = 20\log(f_{RF}) + CG - NF + IIP3 - 10\log(P_C)$$

Body-Input Mixer

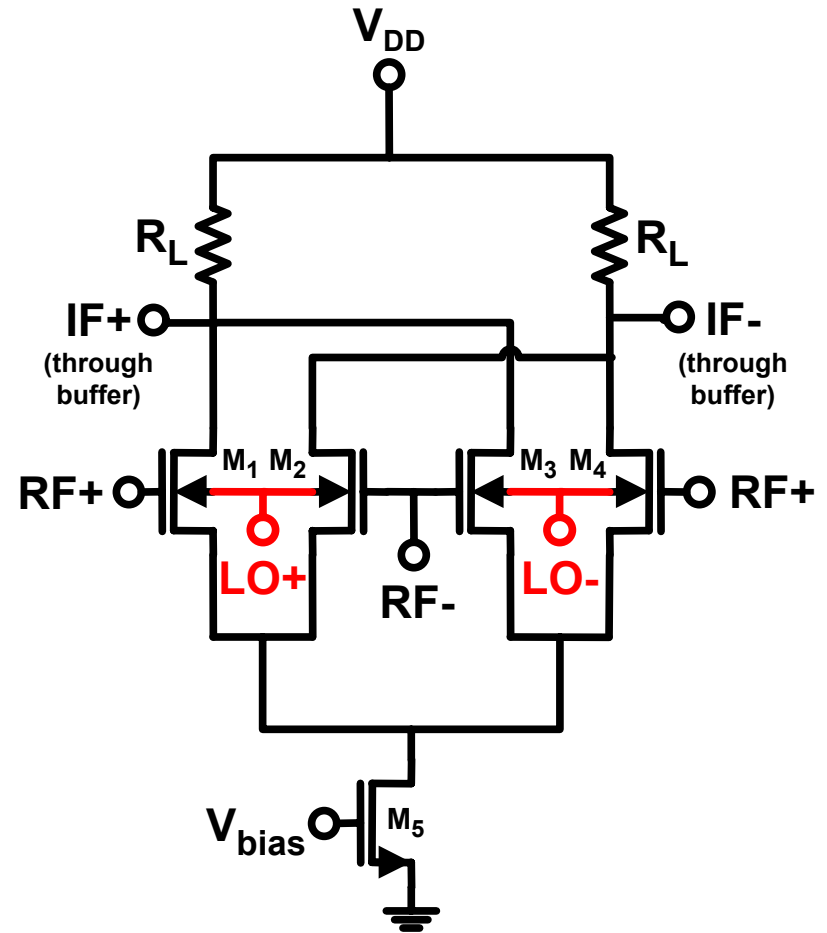- True four-terminal MOSFET
 - ◆ Body used as large-signal input for LO
- Lowers minimum supply voltage
- Designed for low power consumption




Body-Input Mixer

- **Advantages**

- ◆ low-voltage, low-power operation possible
- ◆ good CG, NF; acceptable IIP3



- **Disadvantages**

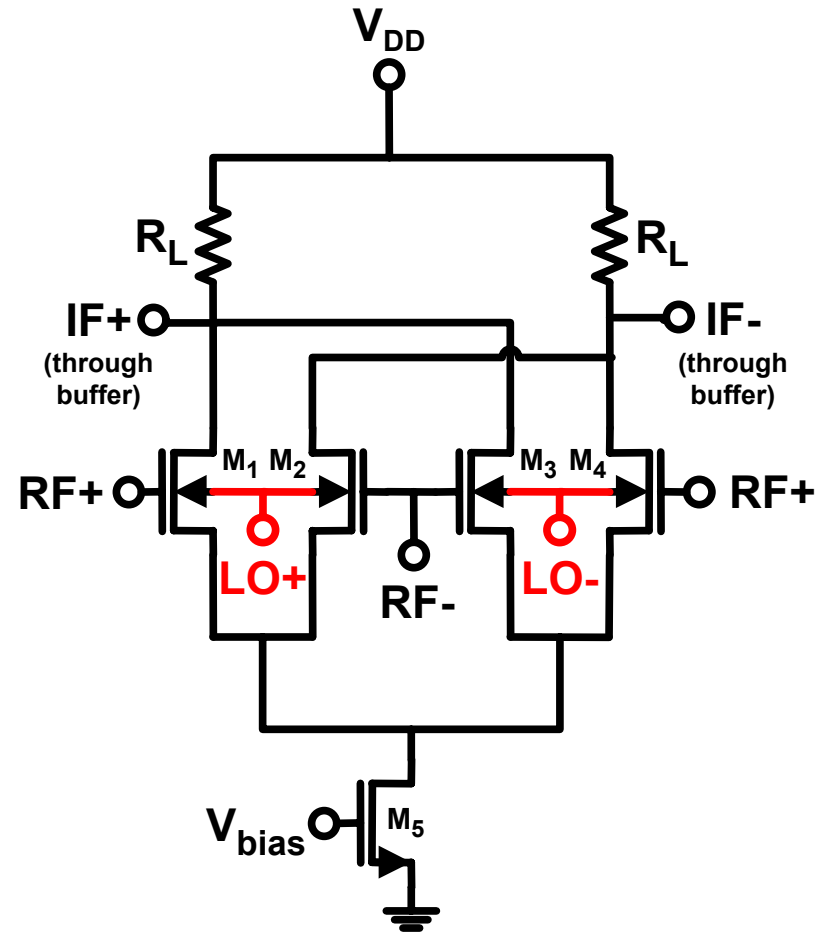- ◆ high LO power requirement
- ◆ low gain compression




Body-Input Mixer

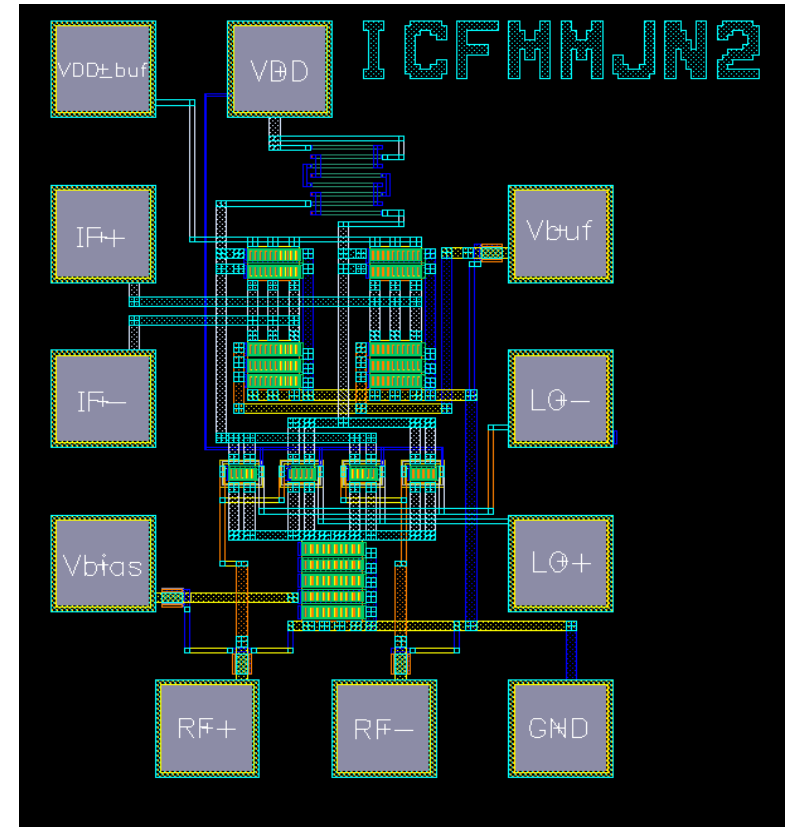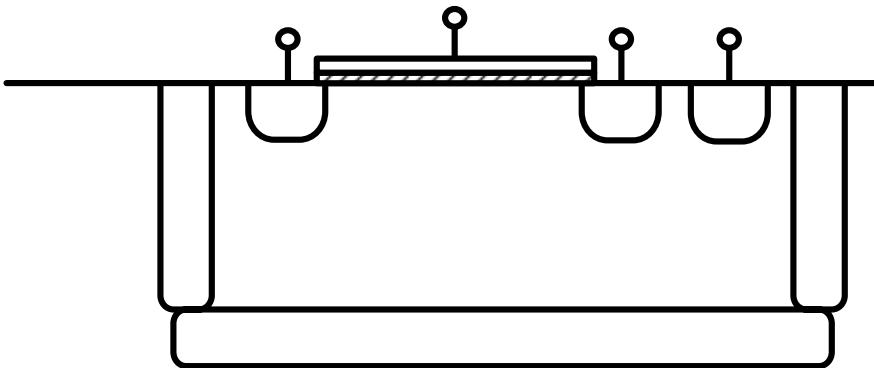
- Designed in TSMC's 0.18 μm CMOS process
- Deep n-well required for this design, available in this process



Results - Linearity

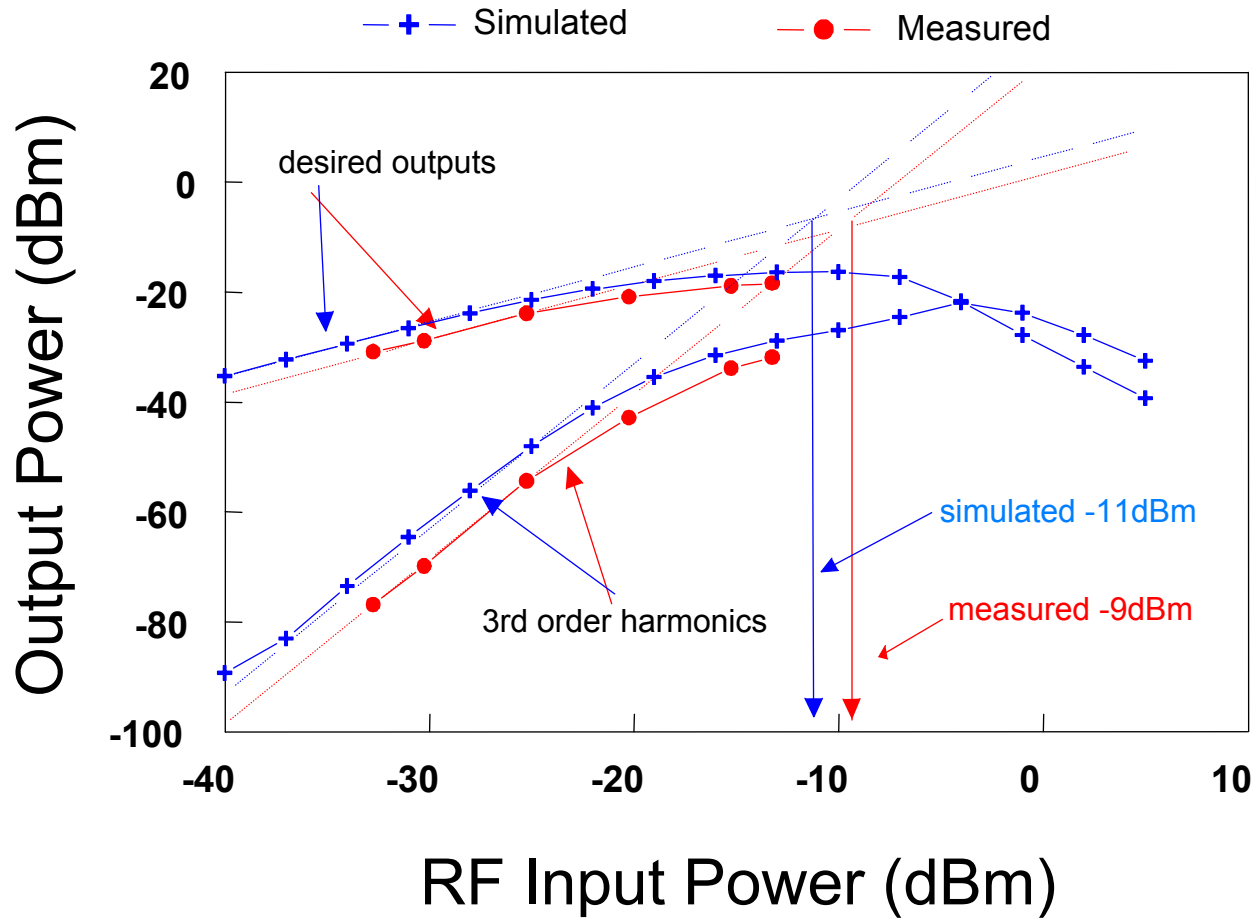

Results – Voltage Supply Effects

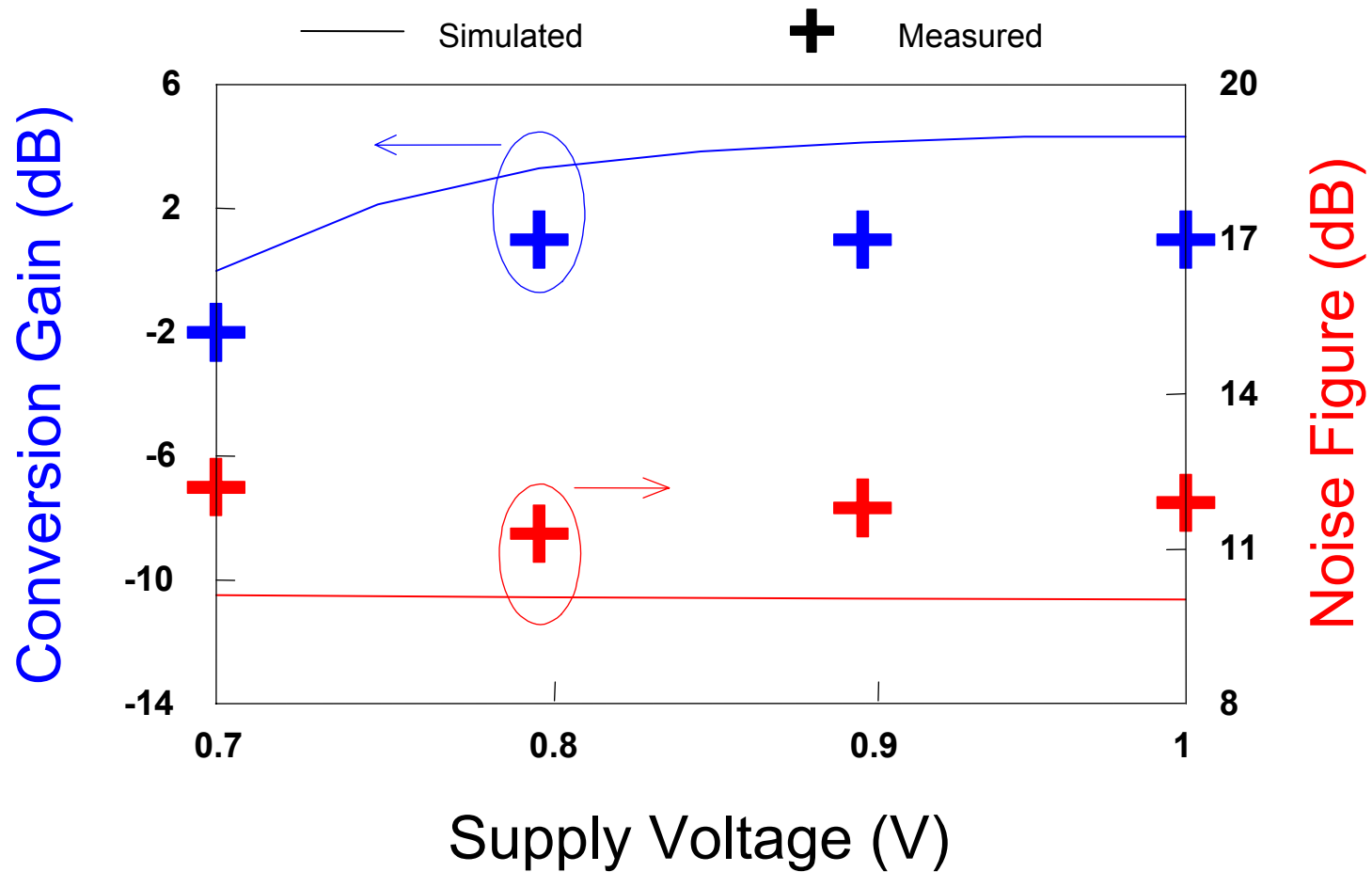


Results - Summary

Supply Voltage (V)	0.8
Current (mA)	0.5
Power Consumption (mW)	0.4
RF Input Frequency (GHz)	1.9
LO Input Frequency (GHz)	1.65
RF Input Power (dBm)	-25
LO Input Power (dBm)	0
IF Output Frequency (MHz)	250
Conversion Gain (dB)	1
SSB Noise Figure (dB)	11
IIP3 (dBm)	-9

Comparisons


	Tech- nology	f_{RF} GHz	CG dB	NF dB	IIP3 dBm	P_C mW	FoM
<i>Body-input</i>	<i>0.18μm</i>	<i>1.9</i>	<i>1</i>	<i>11</i>	<i>-9</i>	<i>0.4</i>	<i>201</i>
Gilbert Cell – 2003	0.18μm	1.9	-2	17	8	4	199
Taris et al – 2003	0.18 μ m	2.4	10	14	-5	12	198
Debono et al – 2001	0.35 μ m	0.9	2	13.5	3.5	4.7	194
Kan et al – 2000	0.8 μ m	0.9	-8.4	28	25.5	1.5	196

Trends - VCO Frequency

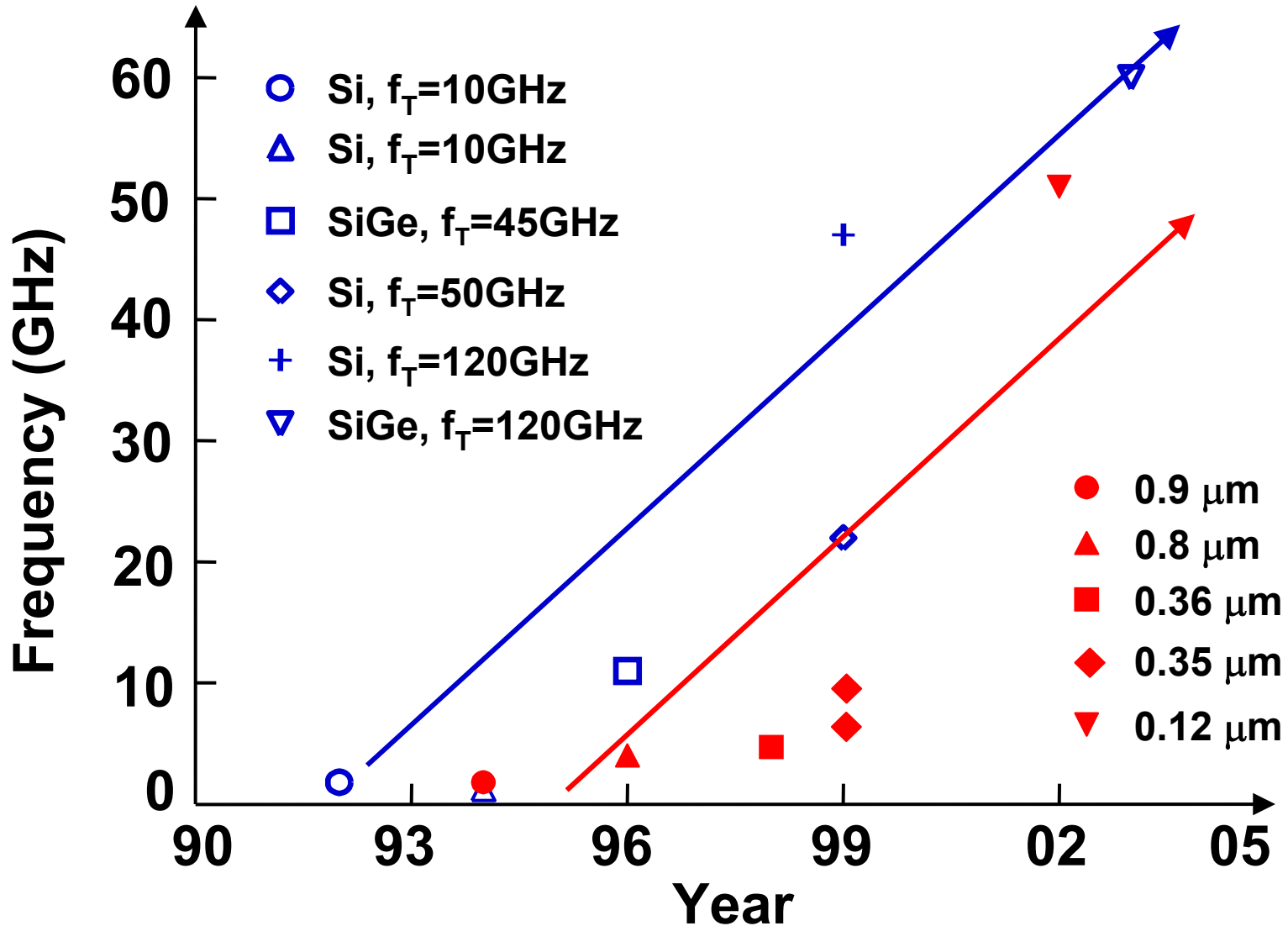

Oscillator Phase Noise

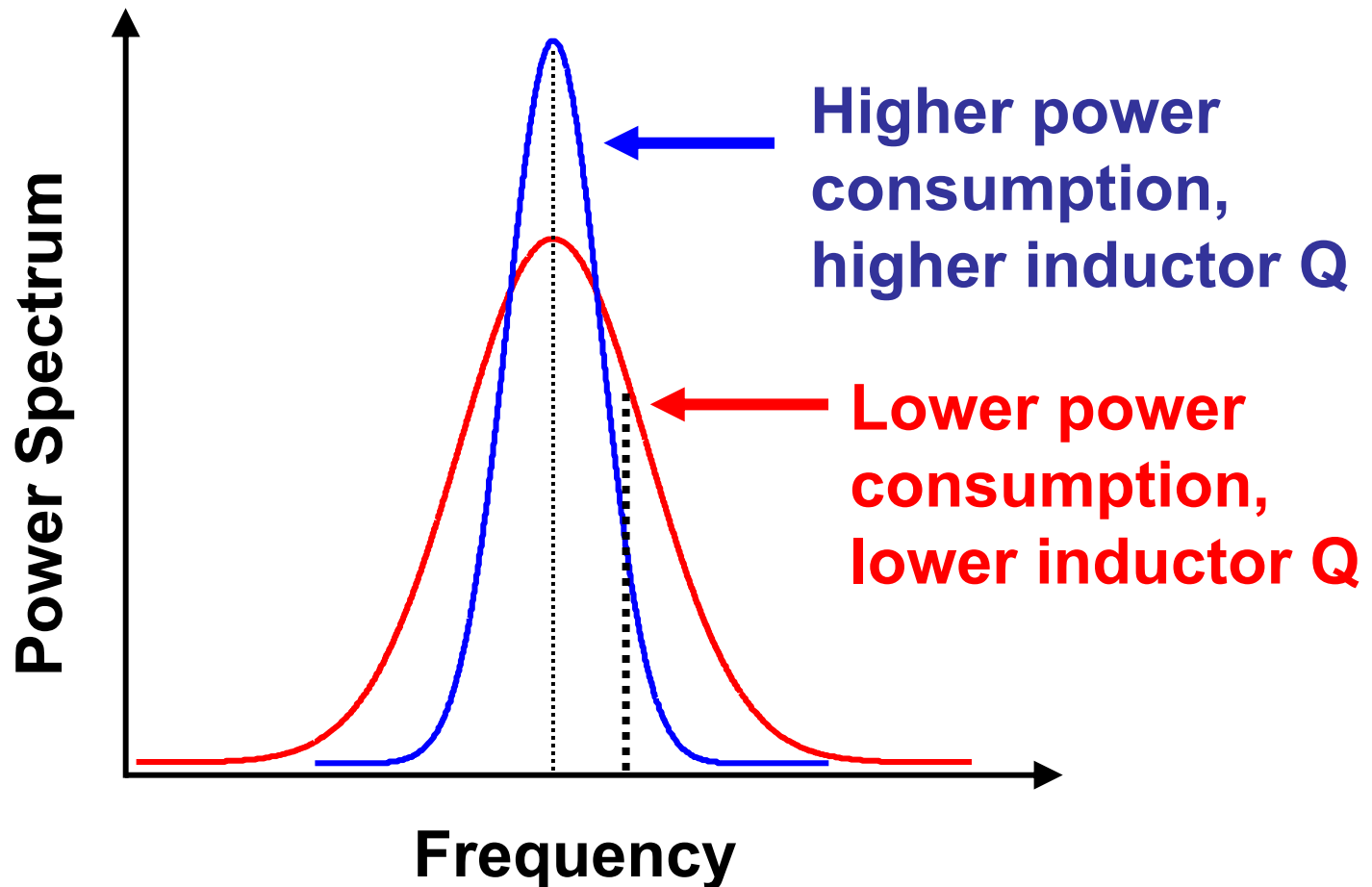- Effect of power consumption and inductor quality on oscillator



Why a VCO with AAC?

- **VCO requirements**

- ◆ Low phase noise implementation
- ◆ Low power implementation
- ◆ Large tuning range (VCO gain)
- ◆ Additional issues of a practical implementation can be solved with an AAC circuit


- **AAC allows**

- ◆ A fast and reliable start up
- ◆ The oscillator to be set to its optimal bias point in terms of noise, while still biasing it with the optimal current at startup
- ◆ A well defined level of output power

- **AAC disadvantages**

- ◆ Larger area required for AAC
- ◆ Slight increase in power consumption due to AAC circuitry

VCO with AAC implementation


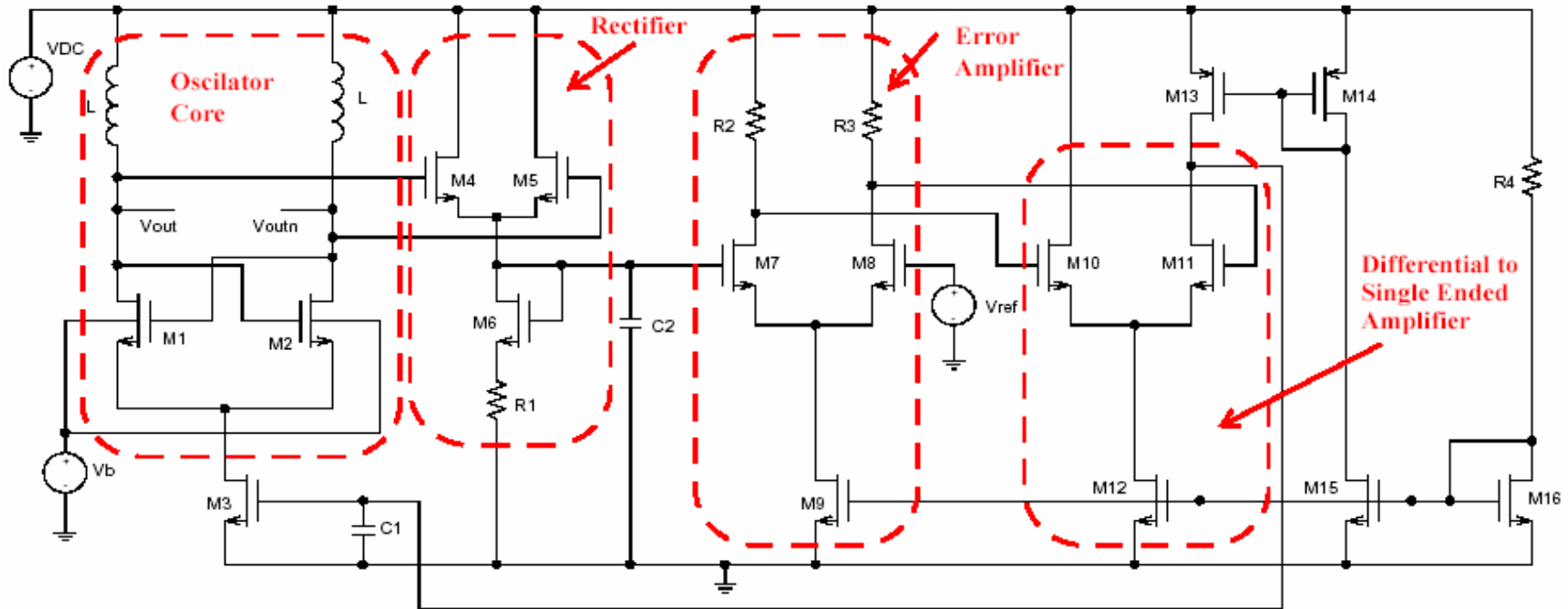


- Frequency is tuned by V_{bs} of the cross-coupled M1-M2 pair
- Output amplitude controlled by V_{ref}

$$f_o = \frac{1}{2\pi \sqrt{L \cdot C_{tk}}}$$



$$f_o = \frac{1}{2\pi \sqrt{L \cdot (C_{tk} + C_{AAC})}}$$

Spiral Inductor Model

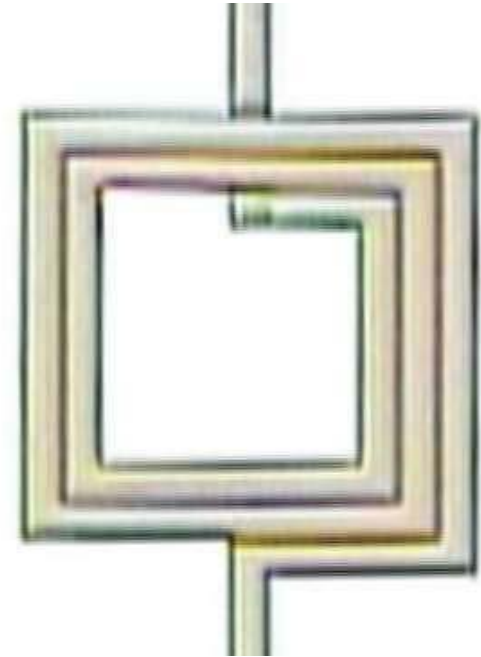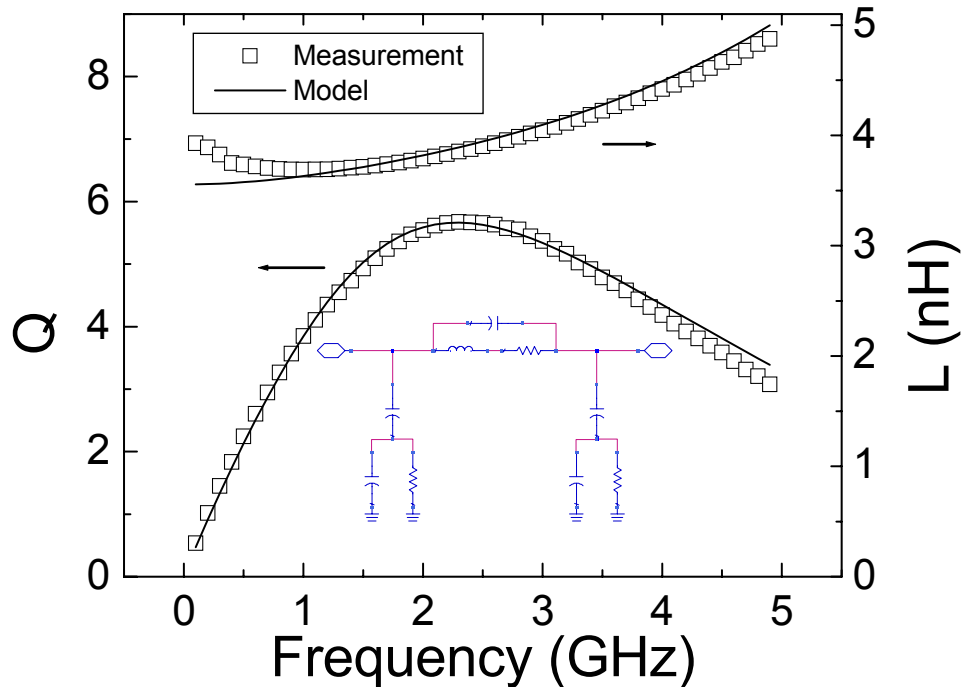



- Good equivalent circuit model at the frequency of interest (4 GHz)
- Q of ~4 at 4 GHz
- Currently investigating other types of components as inductors such as microstrip line or coplanar wave guide

Measured Tuning Range

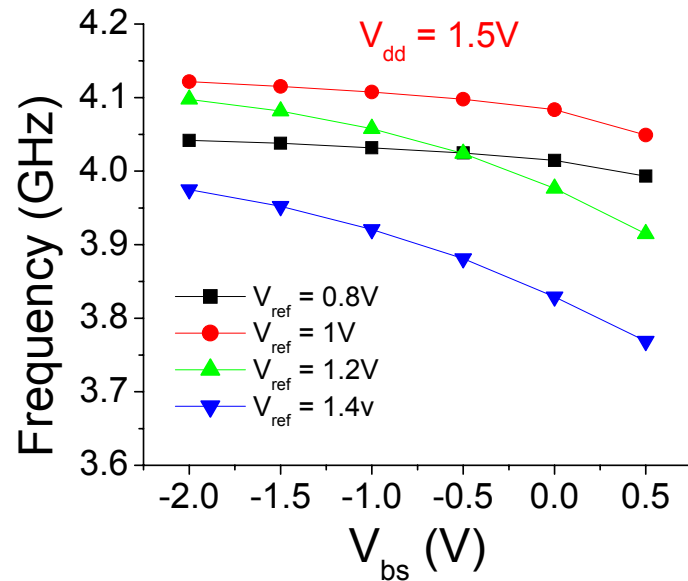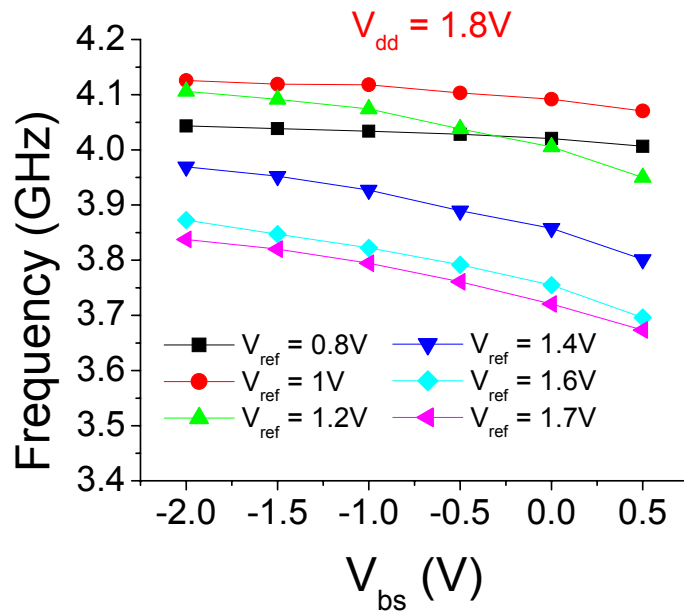

- Tuning range investigated for 2 supply voltages:
 - ◆ At $V_{dd} = 1.8V$ the tuning range is **452.4 MHz**
 - ◆ At $V_{dd} = 1.5V$ the tuning range is **353 MHz**
- As V_{bs} becomes more reversed biased, the frequency increases

Spectrum & Phase Noise at 1.8V

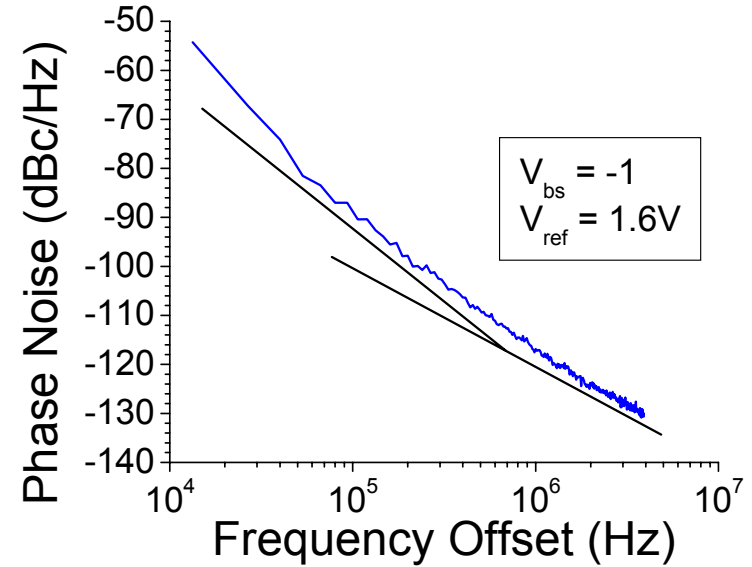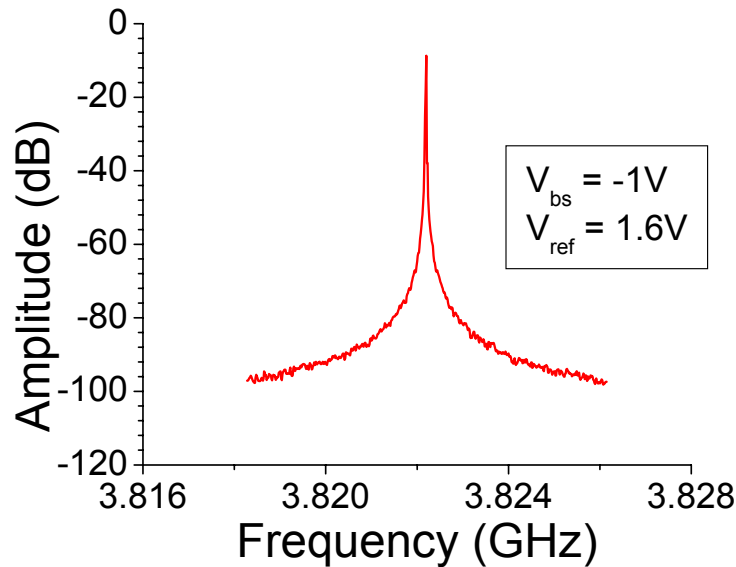

- Spectrum and phase noise shown for $V_{bs} = -1V$, $V_{ref} = 1.6V$ and $V_{dd} = 1.8V$
- Peak is -8.7dBm at 3.822GHz
- $PN@100kHz = -88.7dBc/Hz$, $PN@600kHz = -111.11dBc/Hz$ and $PN@1MHz = -116.88dBc/Hz$

Figure of Merit


$$FOM = 20 \log \left(\frac{\omega_o}{\Delta\omega} \right) - \phi - 10 \log P - 20 \log Q$$

Ref.	Q	f_o (GHz)	ϕ (dBc/Hz)	P (mW)	FOM
[1]	16	0.8	-124@1MHz	4.32	151.6
[2]	15	2	-99@100kHz	13.2	150.3
[3]	5.5	10.02	-102@1MHz	3.7	161.5
[4]	8	2.56	-123@1MHz	14	161.6
This Work	4.2	3.82	-116.9@1MHz	7.24@1.8V	167.6
This Work	4.2	3.88	-114.7@1MHz	4.47@1.5V	167.6


- [1] M. A. Margarit, J. L. Tham, R. G. Meyer and M. J. Deen, "A low-noise, low-power VCO with automatic amplitude control for wireless applications," *IEEE J. Solid-St. Circuits*, vol. 34(6), pp. 761-771, 1999.
- [2] A. Zanchi, C. Samori, S. Levantino and A. Lacaita, "A 2-V 2.5GHz-104-dBc/Hz at 100kHz fully integrated VCO with wide-band low-noise automatic amplitude control," *IEEE J. Solid-St. Circuits*, vol. 26(4), pp. 611-619, April 2001.
- [3] R. Murji and J. M. Deen, "A Low-Power, 10 GHz Back-Gated Tuned Voltage Controlled Oscillator with Automatic Amplitude and Temperature Compensation," *ISCAS 2004*, Vancouver, BC, Canada, 4 pages, (23-26 May, 2004)
- [4] J. W. M. Rogers et al, "A study of digital and analog automatic-amplitude control circuitry for voltage-controlled oscillators," *IEEE J. Solid-St. Circuits*, vol. 38(2), pp. 352-356, 2003.

Summary of Results and Layout


Parameter	Summary
Supply Voltage	1.8 V 1.5 V
Current Consumption	0.520 to 4.2 mA 0.515 to 2.9 mA
Power Consumption	0.936 to 7.56 mW 0.77 to 4.35 mW
Best Phase-Noise @1MHz offset (dBc/Hz)	-116.9@3.82GHz -114.7@3.88GHz
Maximum Operating Frequency	4.12 GHz 4.12 GHz
Tuning Range	451MHz 353 MHz
Area	1.18 x 1.2 mm ²
Technology	TSMC 0.18 μm

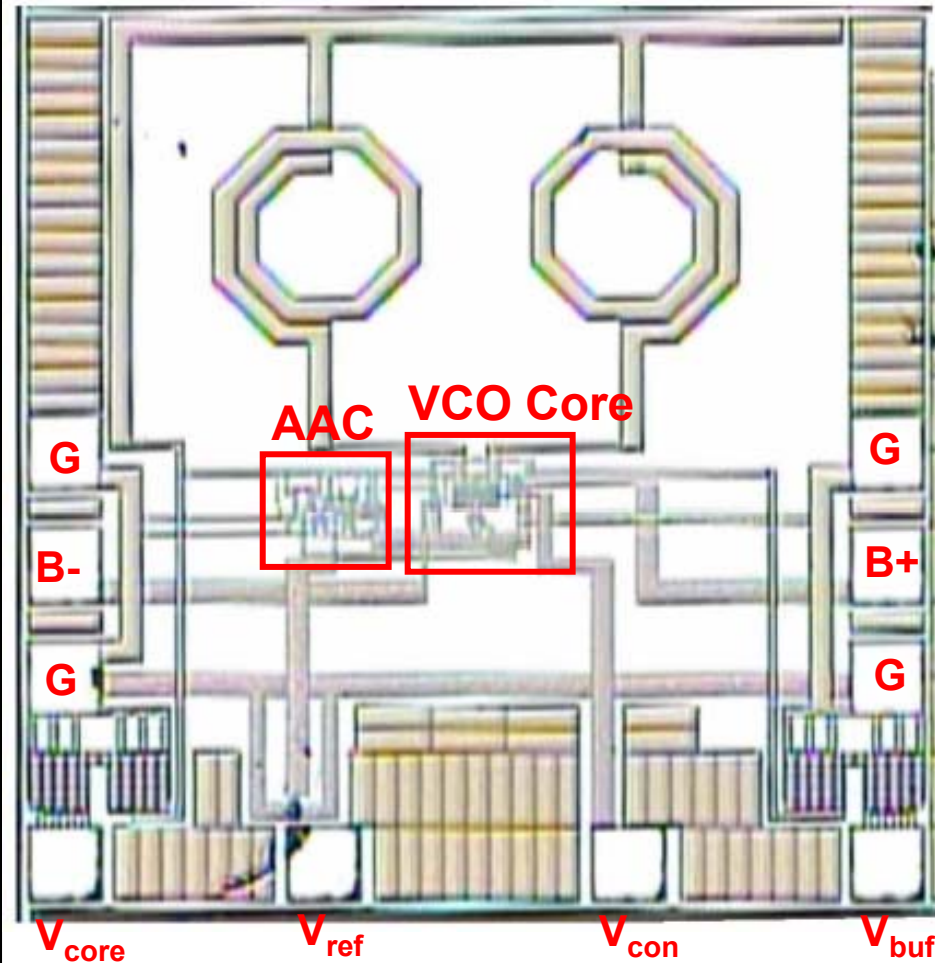

Background - Noise in VCO

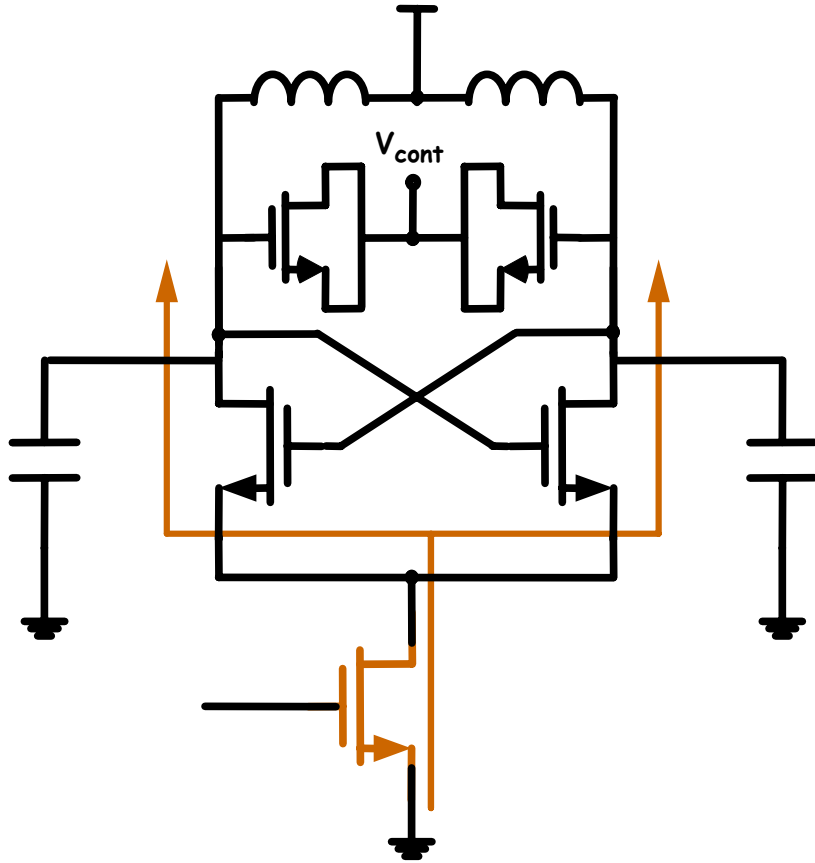


Flicker Noise and
Noise at Harmonics

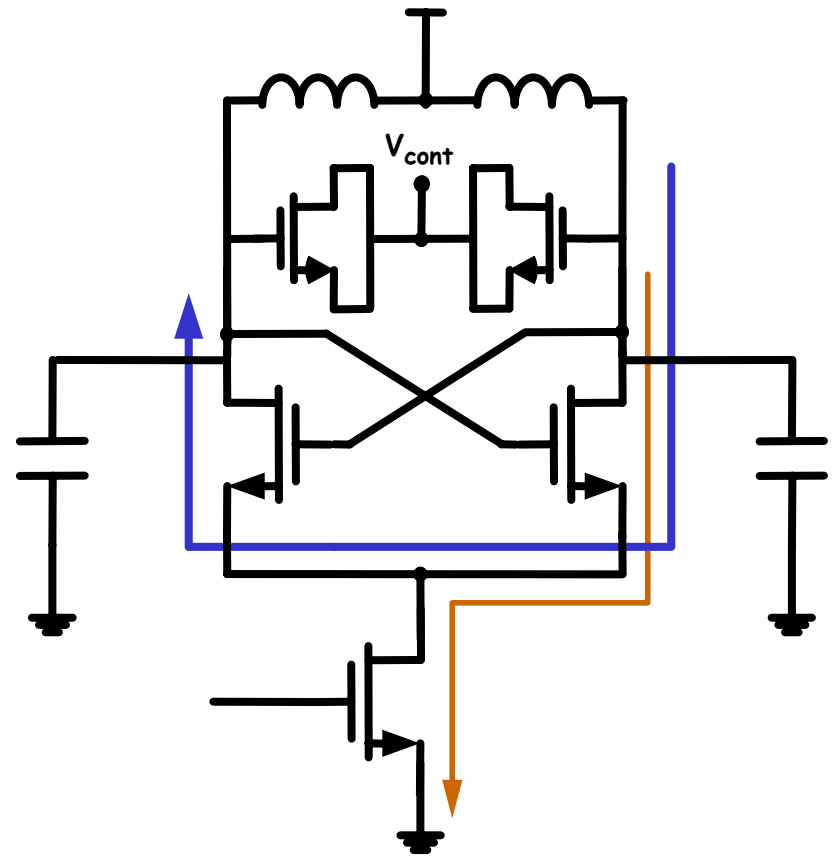


Even Harmonics
Odd Harmonics

Background - Noise Filtering

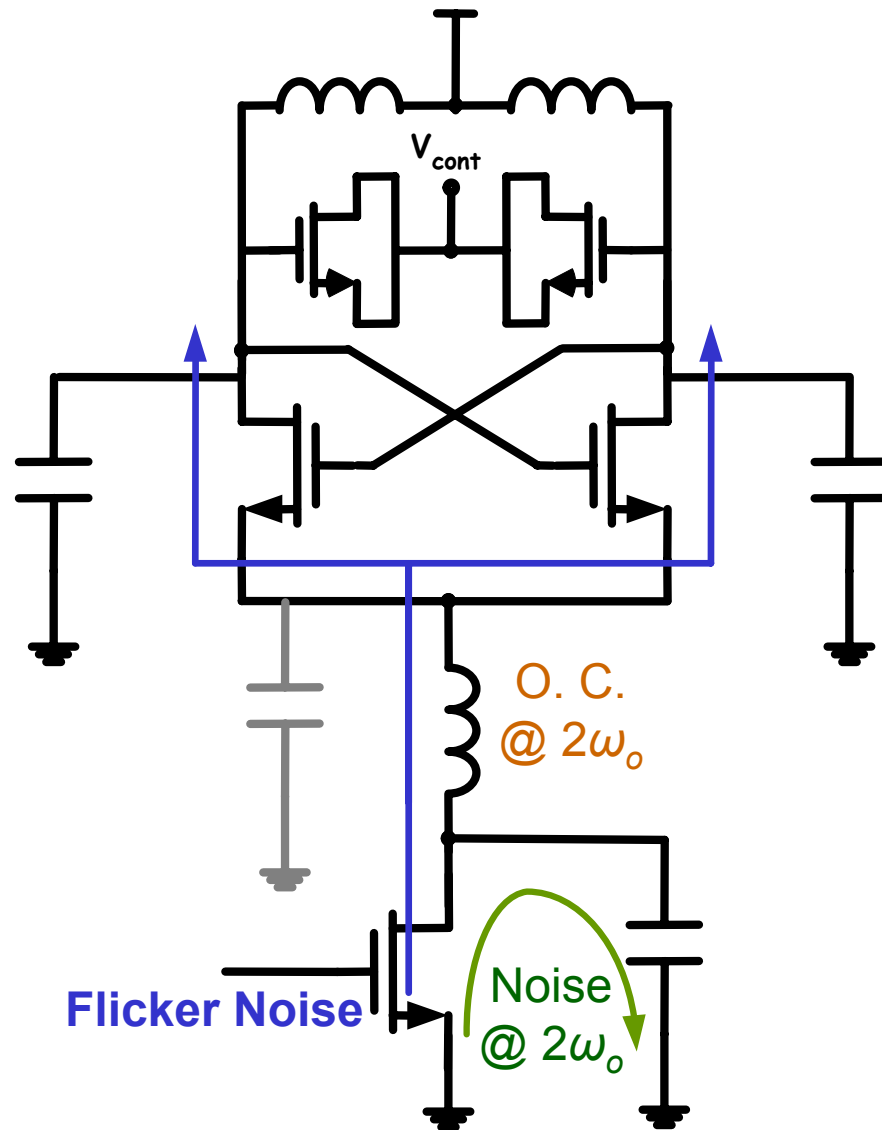

Background – Noise Filtering

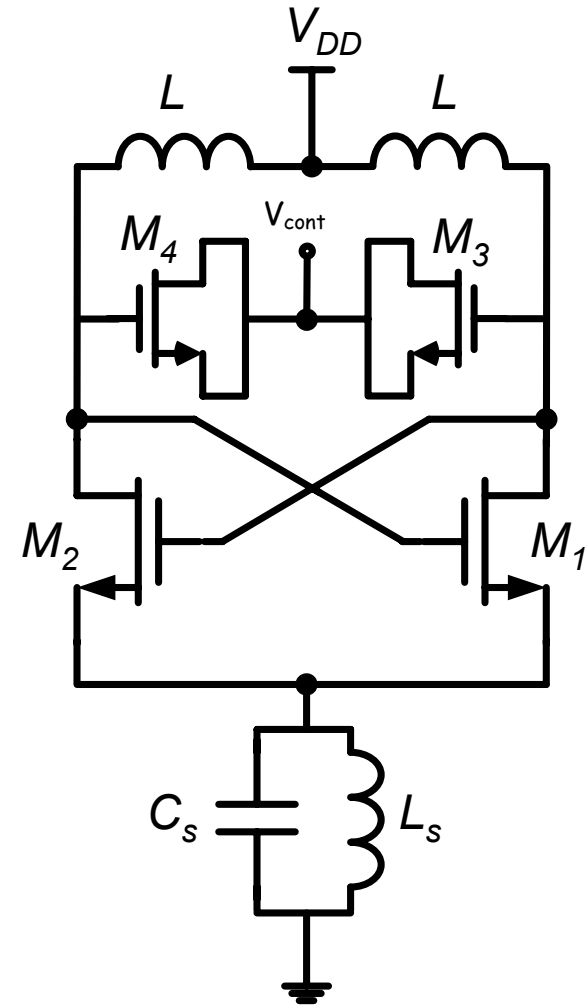- **Voltage-Biased Oscillator**
- **Advantages**
 - ◆ Low phase noise
 - ◆ Low voltage applications
- **Disadvantages**
 - ◆ High current consumption



Low-Voltage, Low-Power


- **Power = $I \times V_{DD}$**

- **Condition of oscillation**

$$g_m \cdot R_L > 1, \quad R_L \sim Q(\omega L)$$

- **Phase noise**
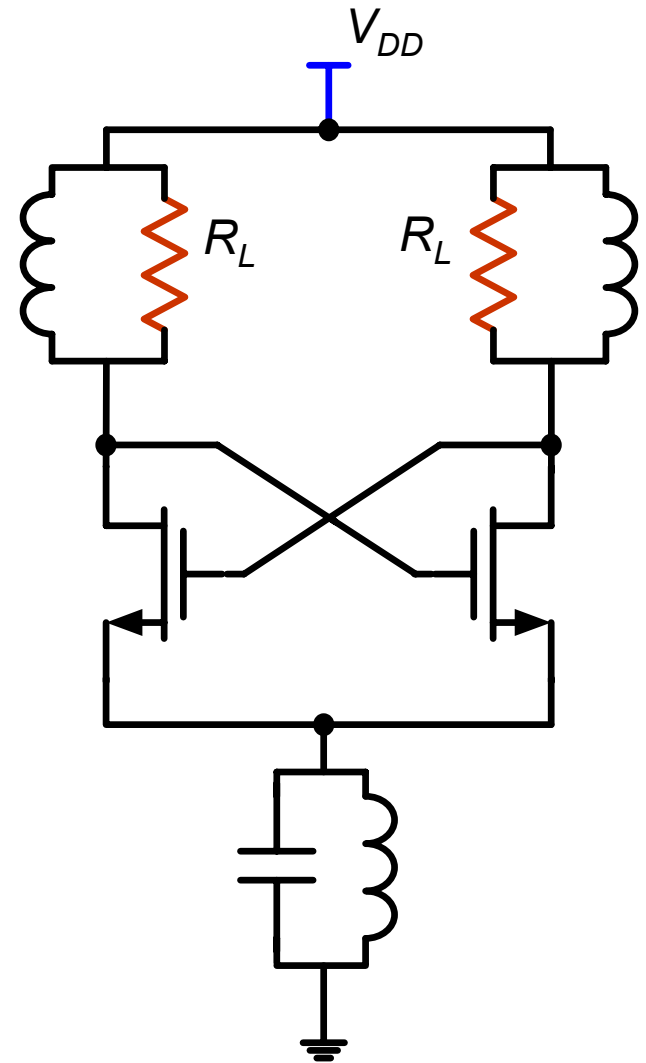
$$L(\omega_m) \propto \frac{1}{V_o^2} \frac{kT}{C} \frac{\omega_o}{Q} \frac{1}{\omega_m^2}$$



Low-Voltage, Low-Power


- Minimize I_D for a given g_m

For normal operation


$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$

For sub-threshold



$$g_m = \frac{I_D}{n\phi_t}$$

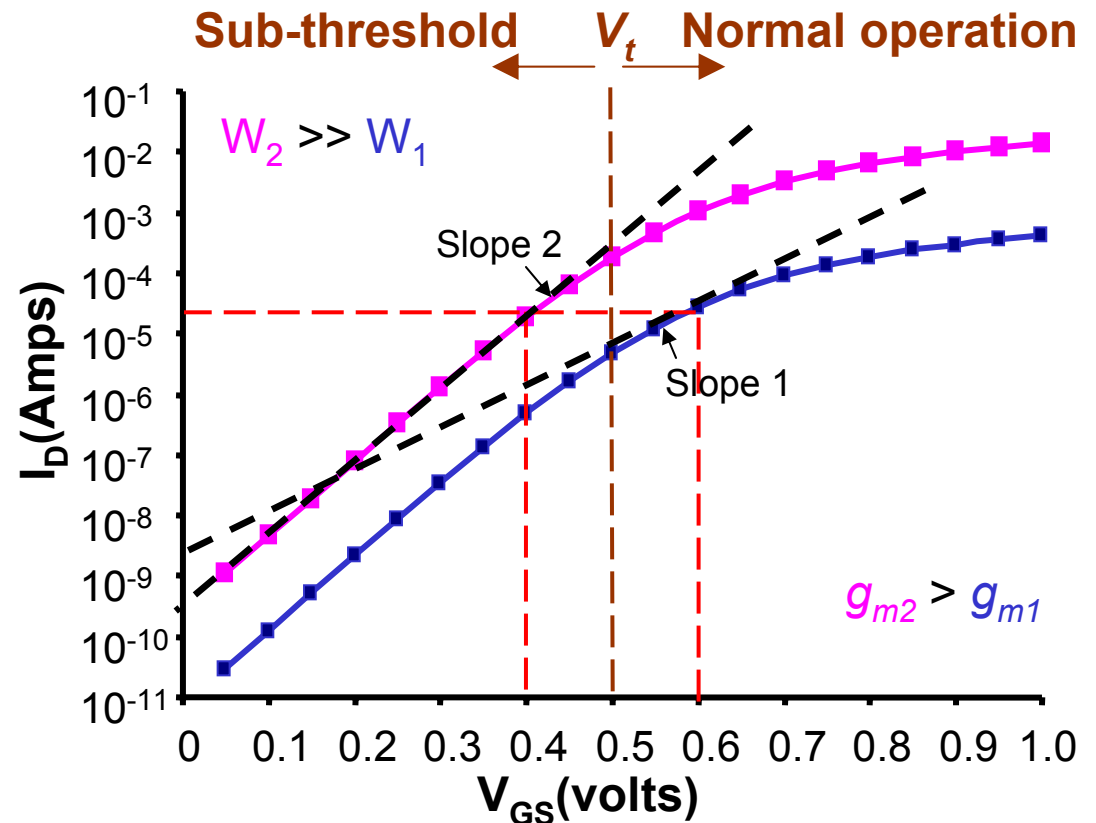

Oscillator Design

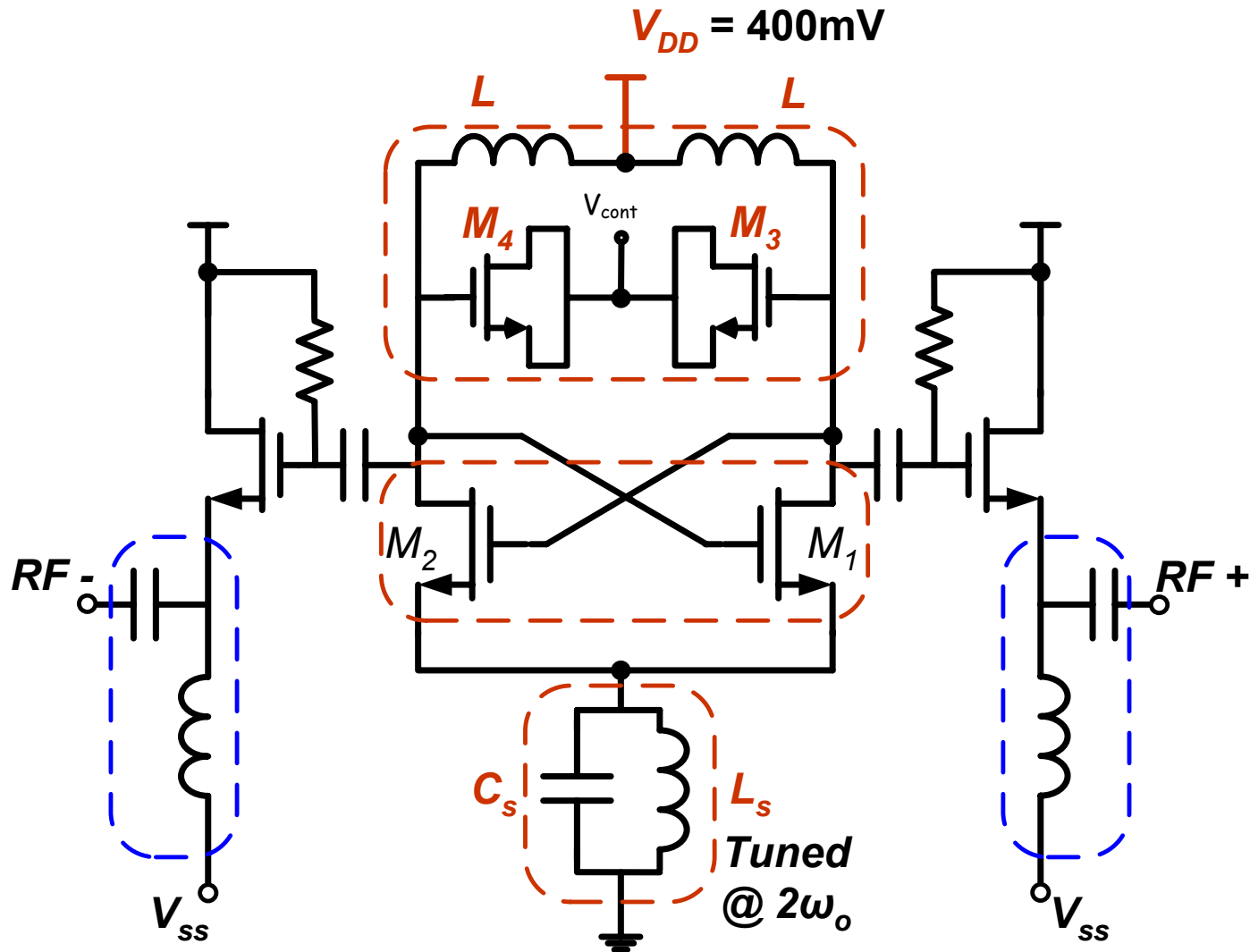


Results – Frequency and PN

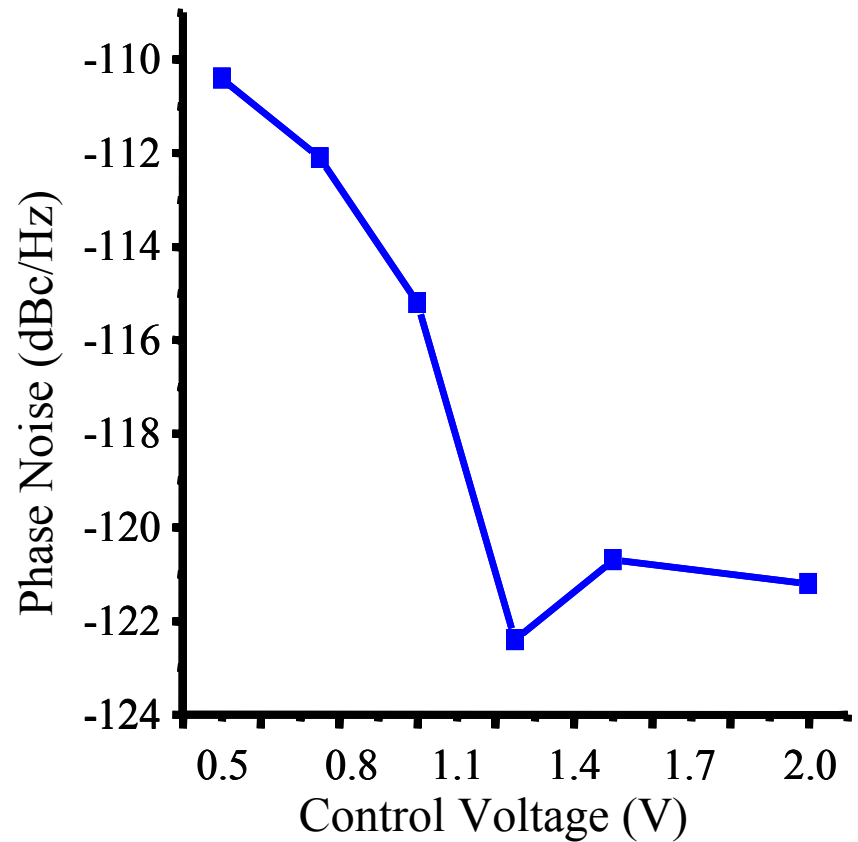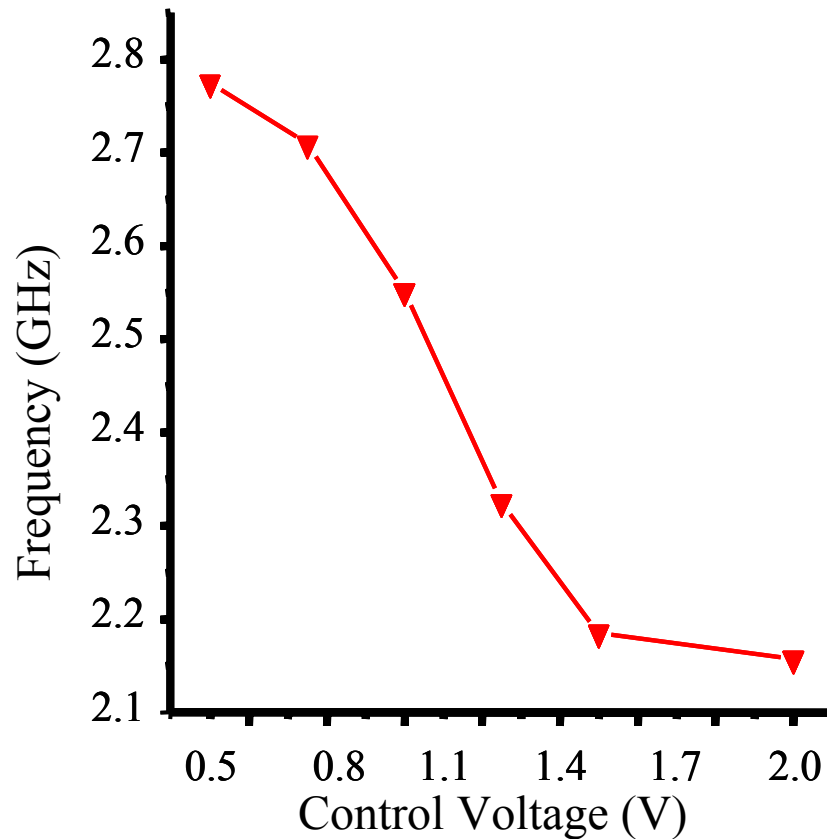

Results – PN and Power

- Effect of current-source tank circuit

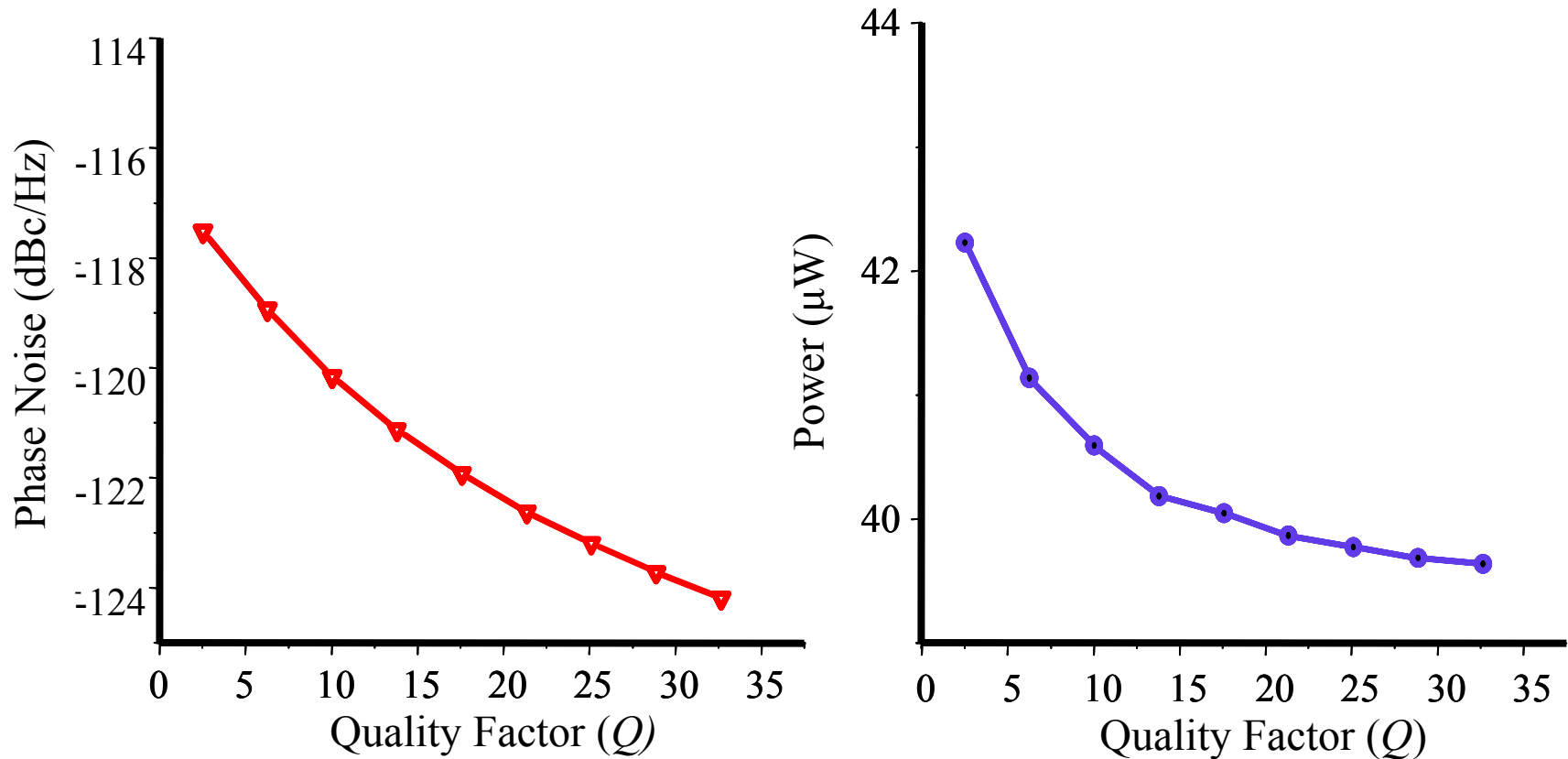

Comparisons



$$FoM = 20 \cdot \log\left(\frac{f_o}{f_m}\right) - PN - Power (dBm) - 20 \cdot \log(Q)$$

References	Q	f_o (GHz)	PN	Power (mW)	FoM
This work	60	2.4	-123@1MHz	0.04	168.5
Troedsson, ASIC, 2002	13	2.4	-124@1MHz	5.5	161.6
Troedsson, RAWCON 2002	13.4	2.4	-130@3MHz	1.98	162.5
Mostafa, 2000	5	10	-101@100kHz	9	158.9

Hot Carrier Reliability - RF CMOS



- **Reducing the channel length of MOSFETs into deep submicron**
 - ◆ CMOS is now very attractive for RFICs
- **With channel length reduction**
 - ◆ Electric fields increase because of V_{DD} and L scaling
 - ◆ Hot carriers become an important reliability issue
- **HC damages lead to degradation of parameters of CMOS RF circuit**
 - ◆ Lower gain, higher noise figure, higher phase noise, ...

Hot Carriers in NMOSFETs

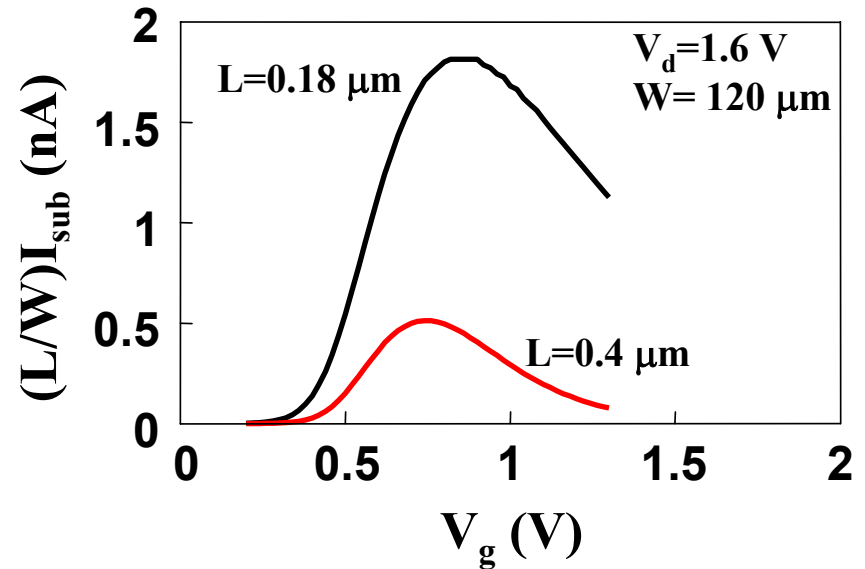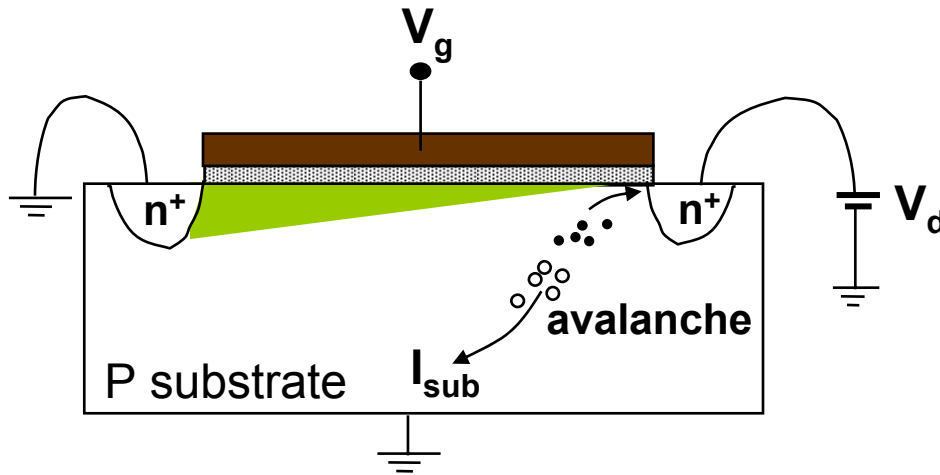



- Physical effects caused by hot carriers are interface traps and oxide trapped charges
- Substrate current can be used as a measure of stress

HC Effects - Device Performance



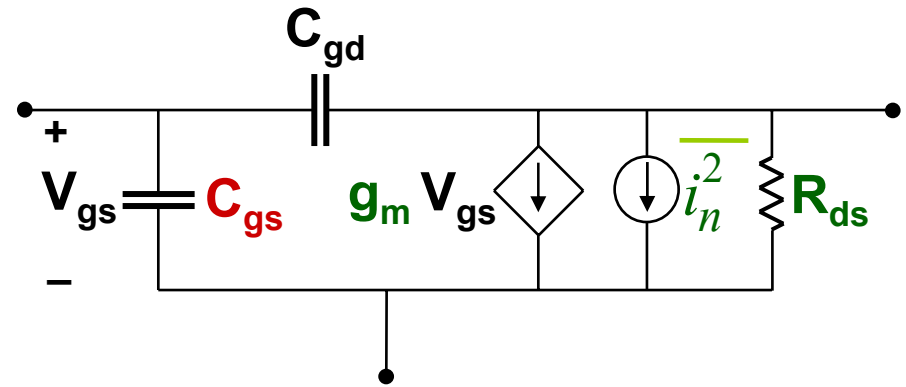
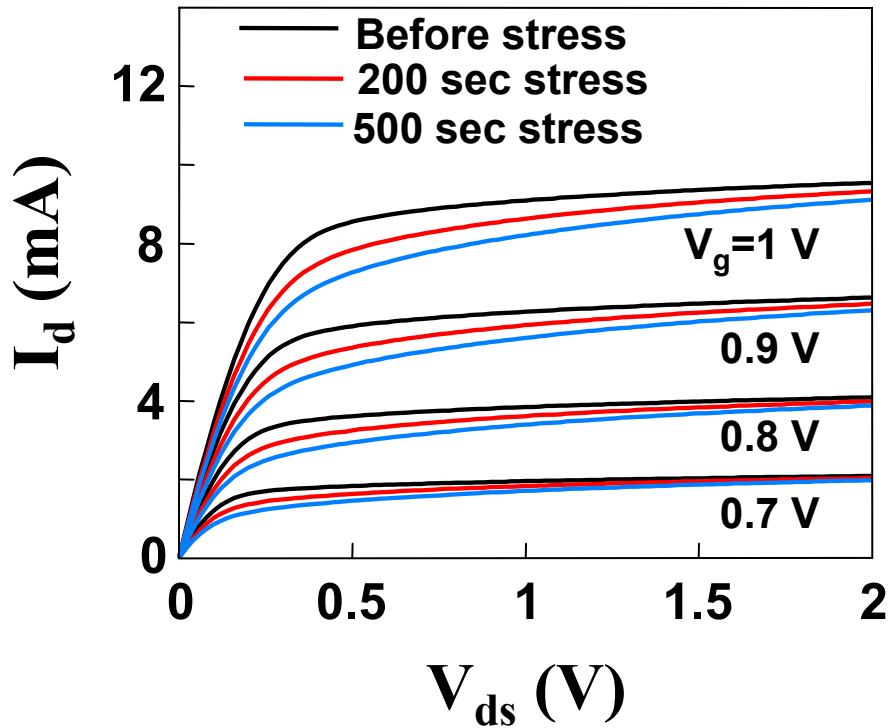


- HC deteriorate parameters such as V_{th} , g_m , g_{ds} , C_{gs} , and channel noise
- RF performance deterioration are manifested by degradation of f_T and f_{max}



HC Effects on RF Circuits: LNA

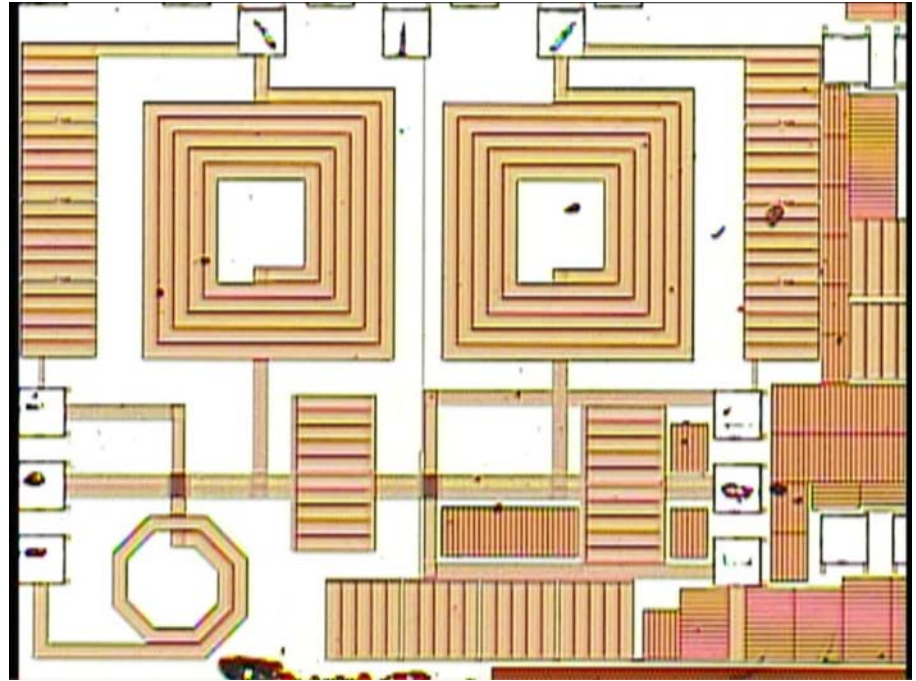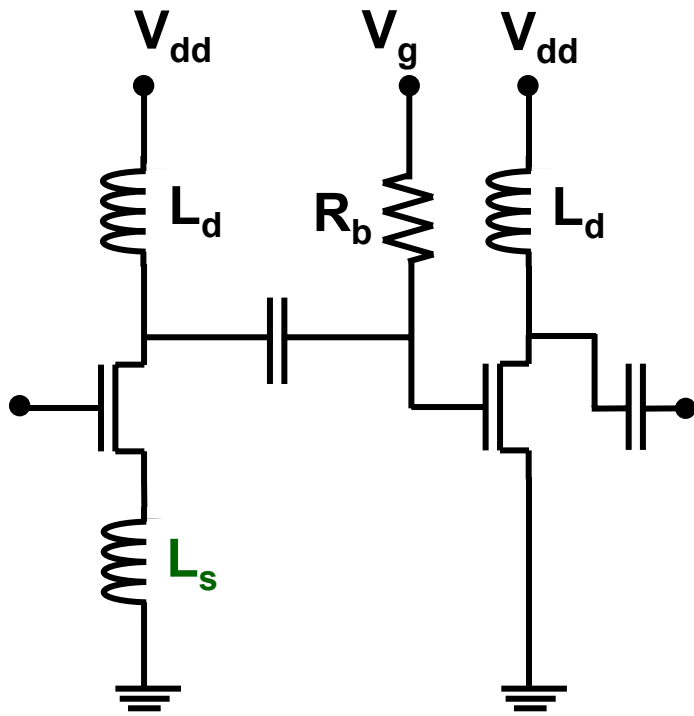

HC Effects on Gain, NF

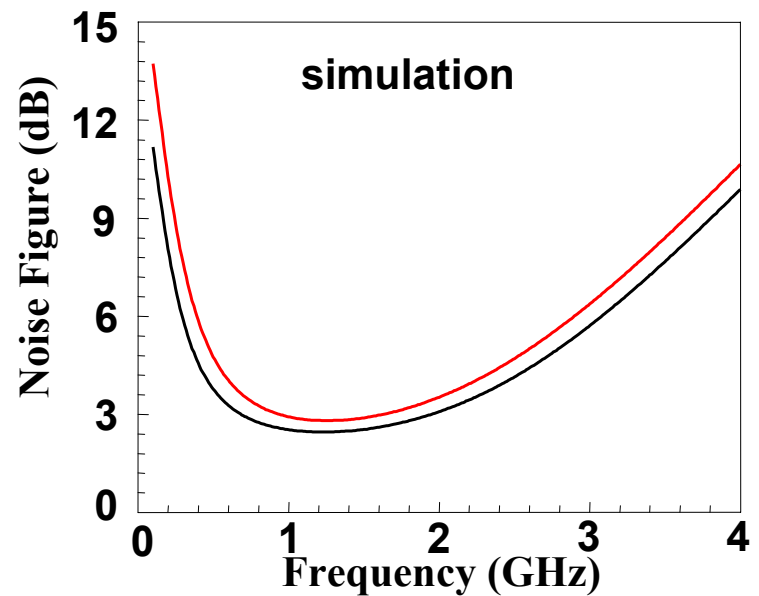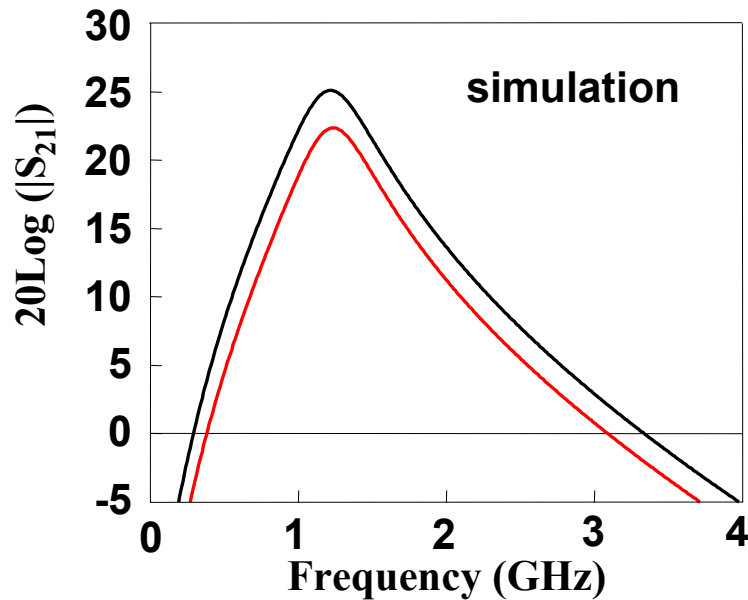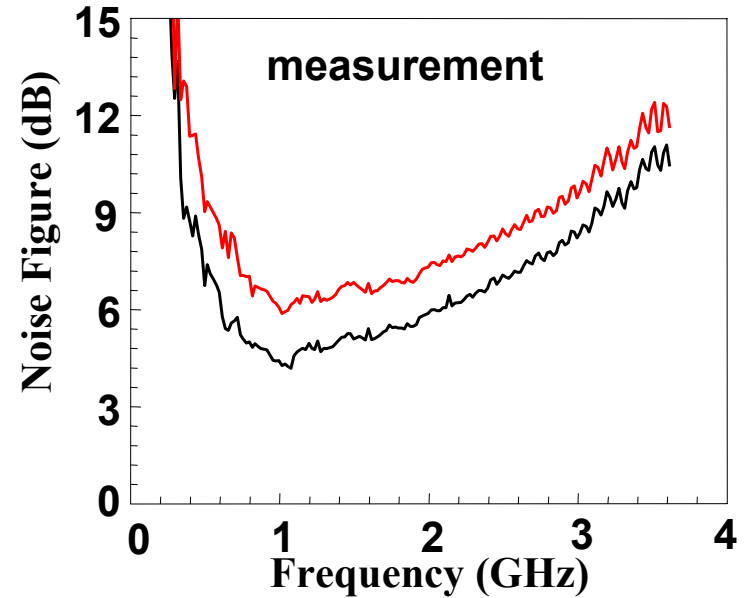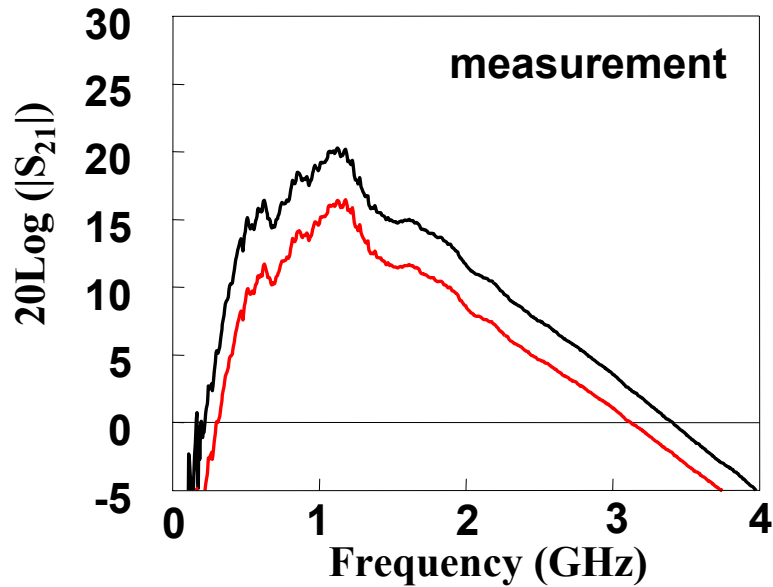

HC Effects on Linearity

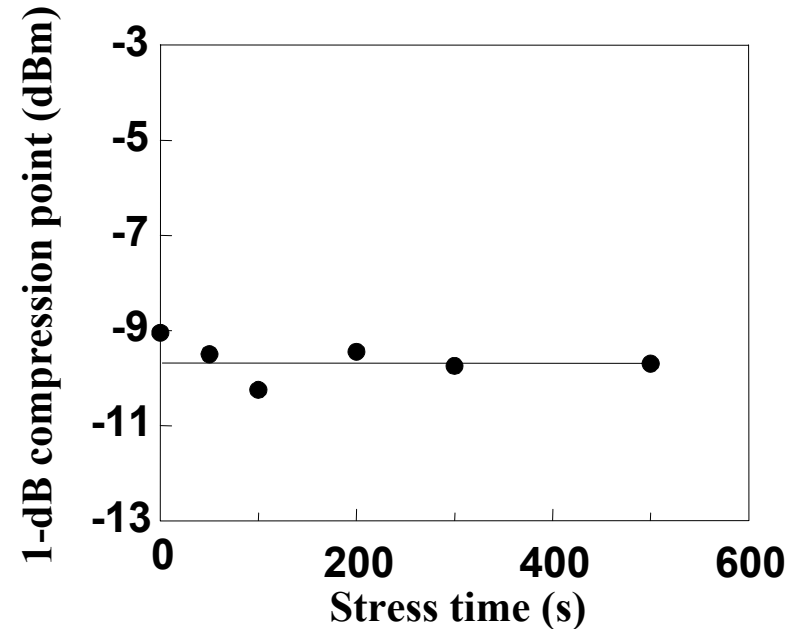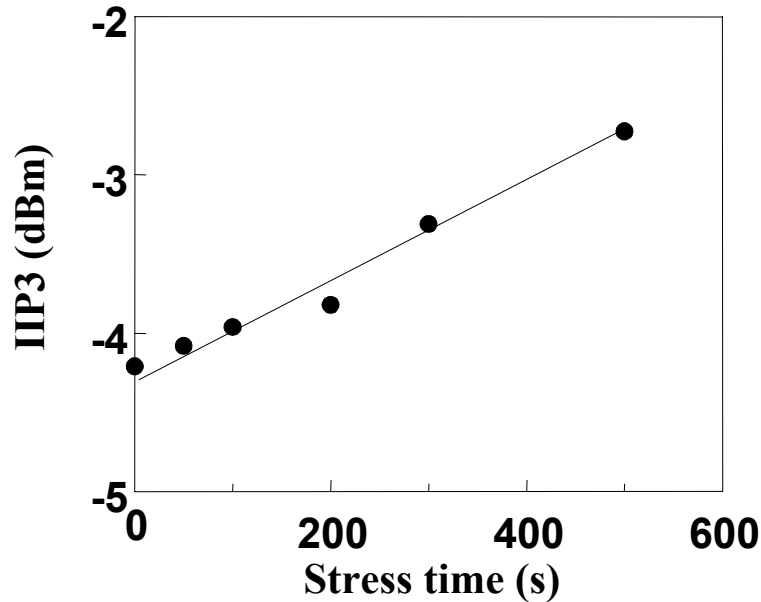


- Linearity might be affected by HC

Mismatch Issues - Oscillator


- Increasing use of CMOS for RFICs
- Process- and design-induced mismatch effects will become increasingly important
- Few publications on mismatch at high frequencies
- Many published research at lower frequencies
- Better prediction of RFICs' performance

Oscillator Mismatch Issues

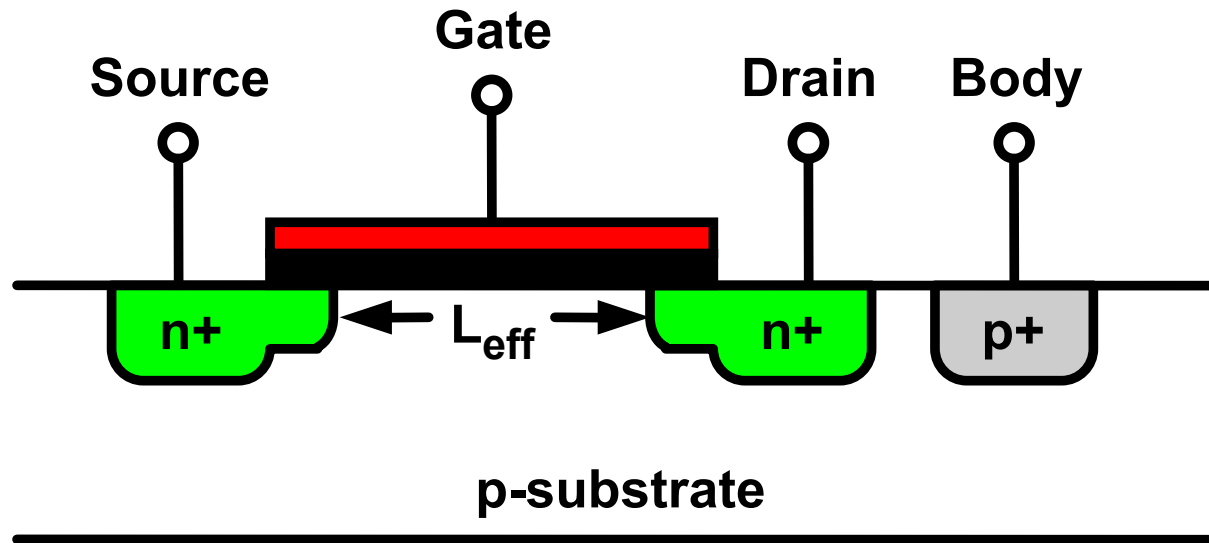

- Transistor's dimensions at design and simulation stages are different from fabrication
- Transistor's channel length smaller than its channel width
- CLFEs are crucial on differential RFICs

Oscillator Mismatch Issues

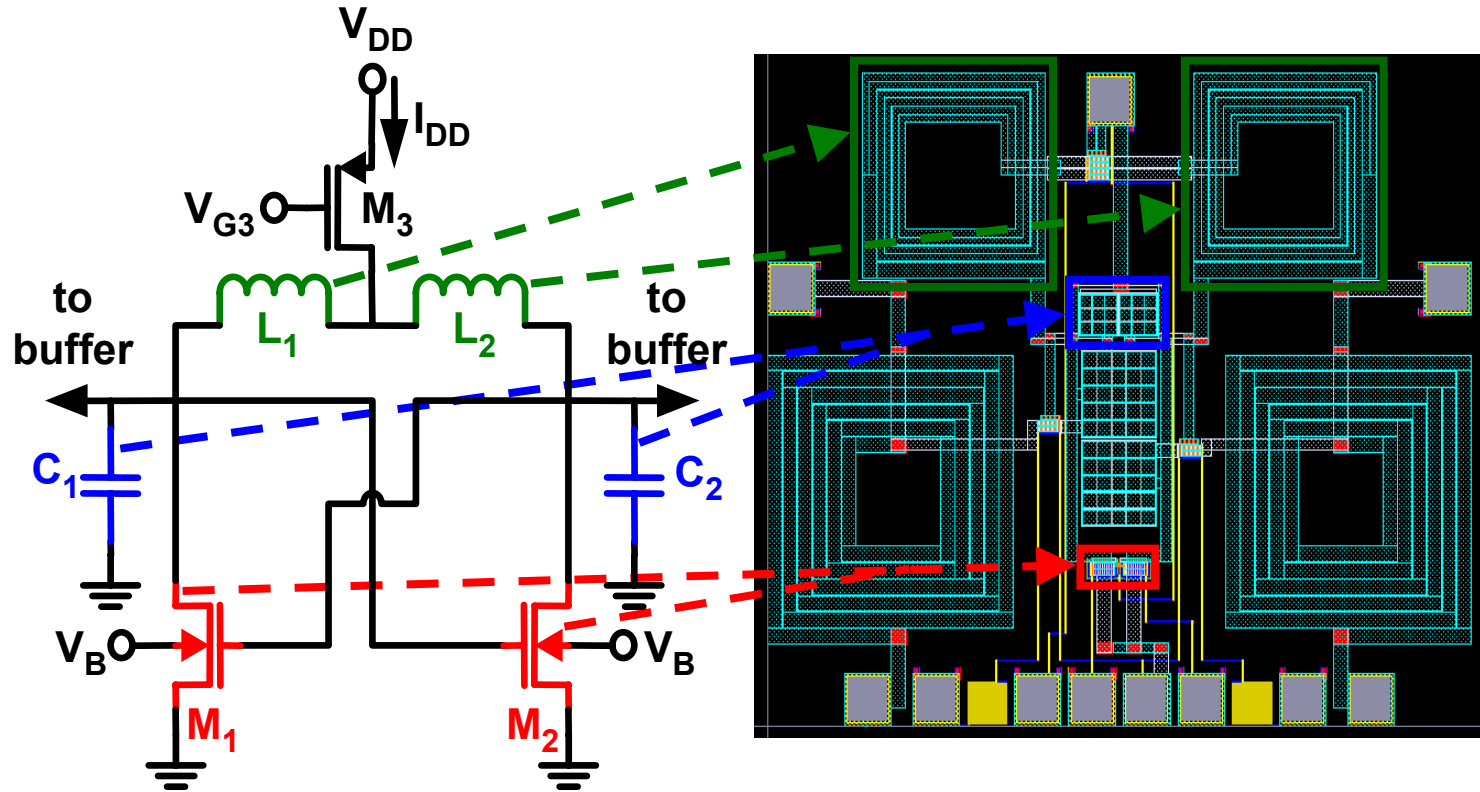


- M_1, M_2 : $L = 0.25\mu\text{m}, 0.28\mu\text{m}, 0.3\mu\text{m}$ (reference), $0.32\mu\text{m}, 0.35\mu\text{m}$
- **Power** = 6.48mW and **Current** $I_{DD} = 3.6\text{mA}$ are approximately constant for all channel length values


CLFEs on Oscillator Frequency

$$\Delta f_0 = \frac{1}{2\pi\sqrt{L}} \left(\frac{1}{\sqrt{2C_t + C_{gs,fab}}} - \frac{1}{\sqrt{2C_t + C_{gs,design}}} \right)$$

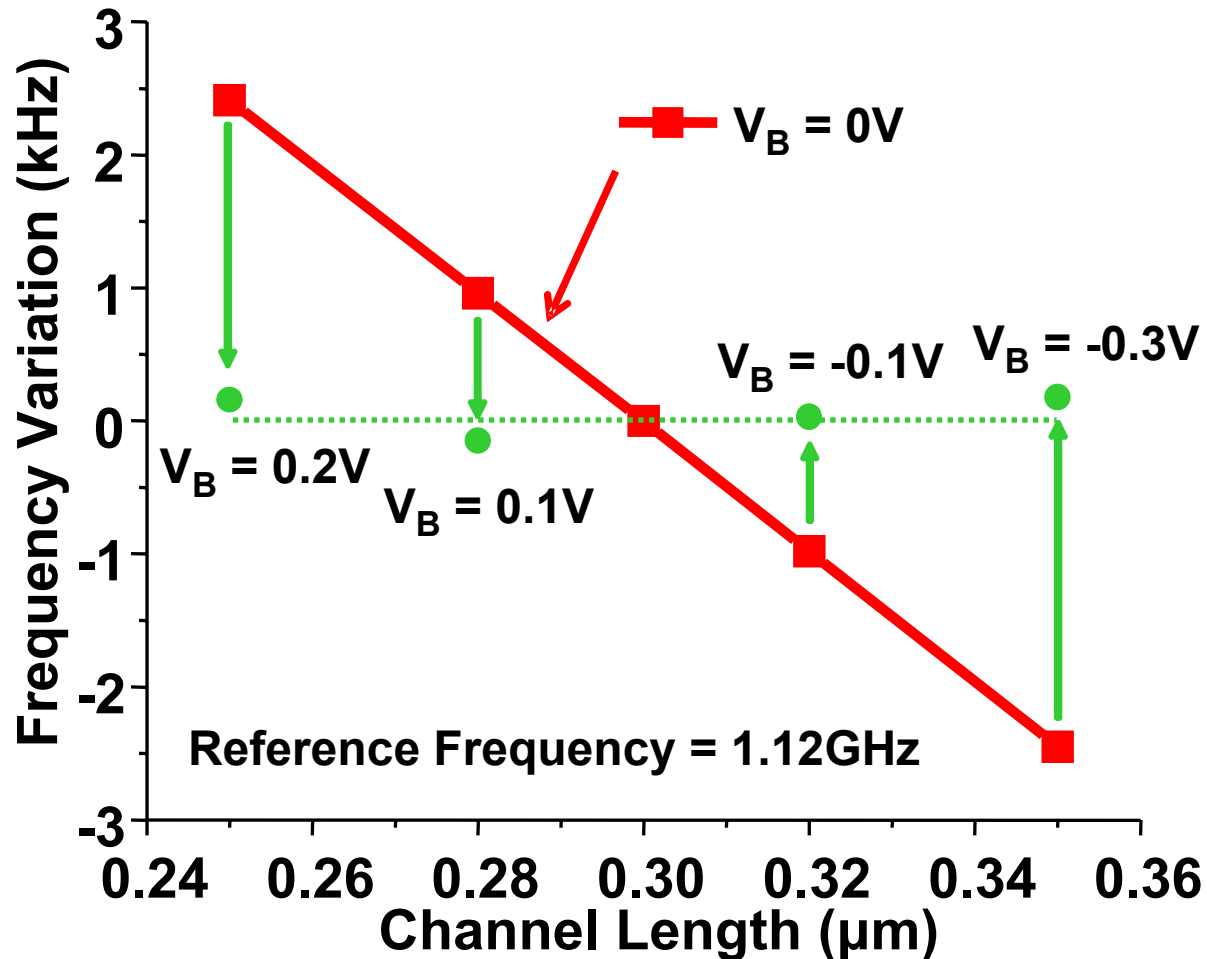
$$C_{gs,fab} = C_{gs,design} \left(\frac{L_{eff,fab}}{L_{eff,design}} \right)$$



CLFEs on Output Power

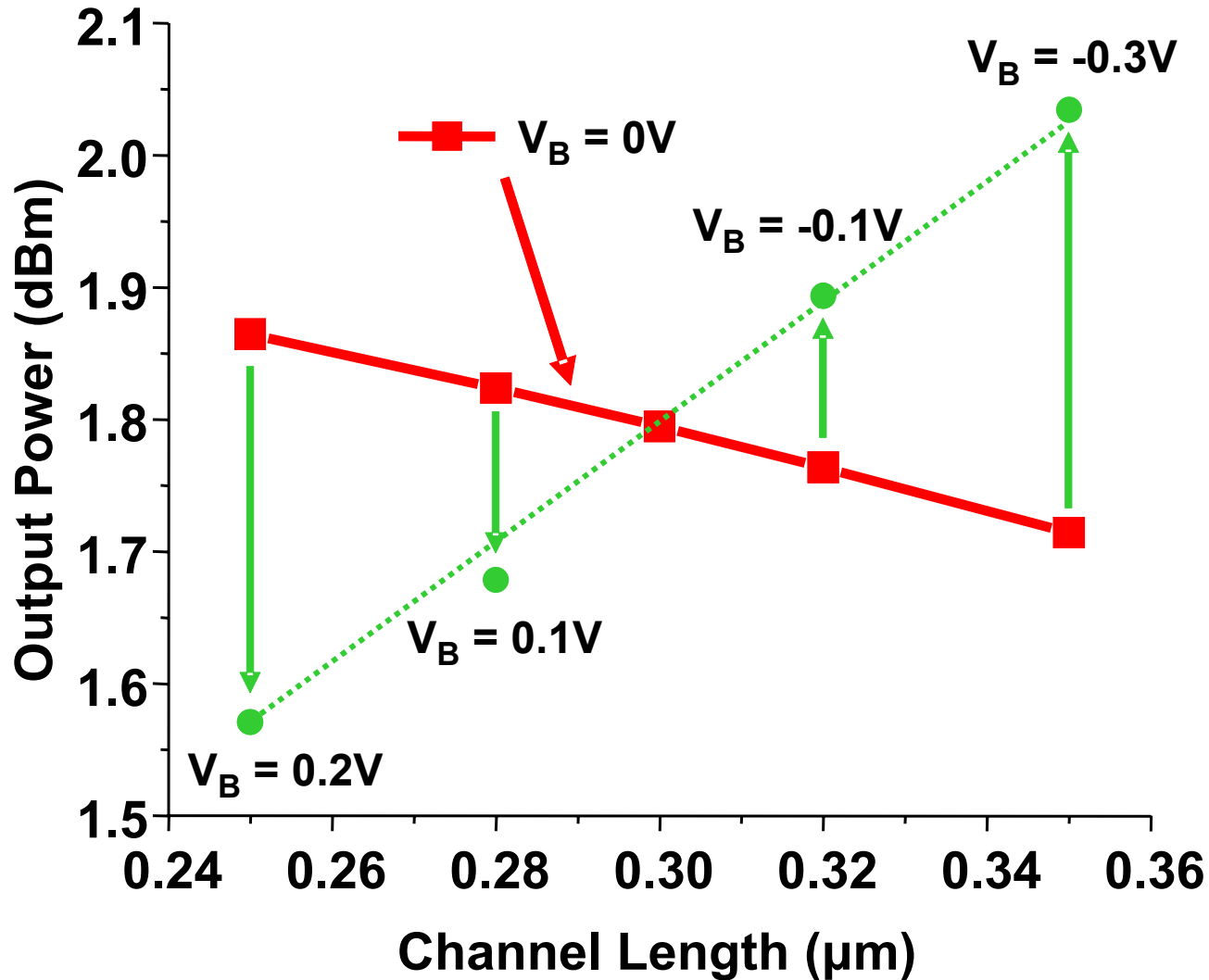

Trend – New Operation Mode

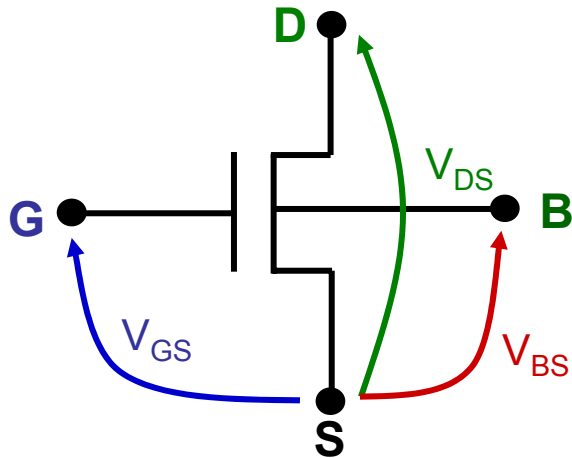


- V_{BS} improves the MOSFET performance

- ◆ **Forward substrate** biasing ($V_{BS} > 0$) reduces the threshold voltage $V_T \rightarrow$ low voltage applications


- ◆ **Forward substrate** biasing ($V_{BS} > 0$) speeds - up the MOSFET \rightarrow RF applications

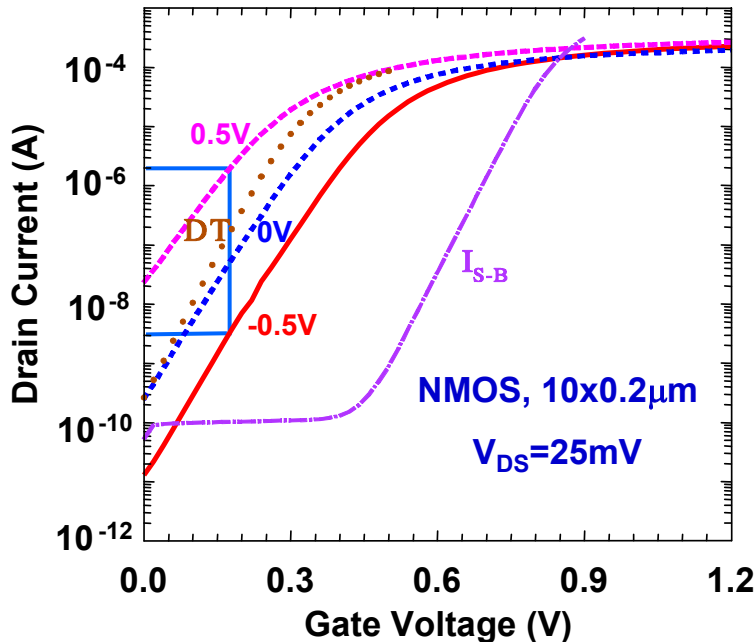- ◆ **Reverse substrate** biasing ($V_{BS} < 0$) reduces the $I_D \rightarrow$ low power applications





Design: Sub-Threshold

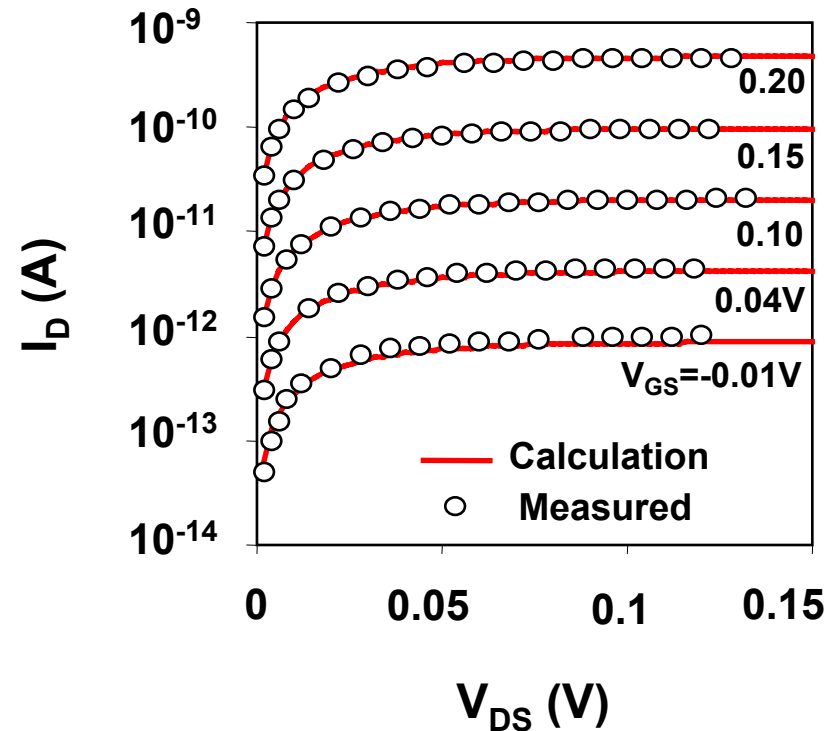- Operate transistor in weak inversion
- Very low V_{DS} required to operate transistor
 - low-voltage applications
- Drain current I_D also very low
 - low-power applications



VTC and Phase noise

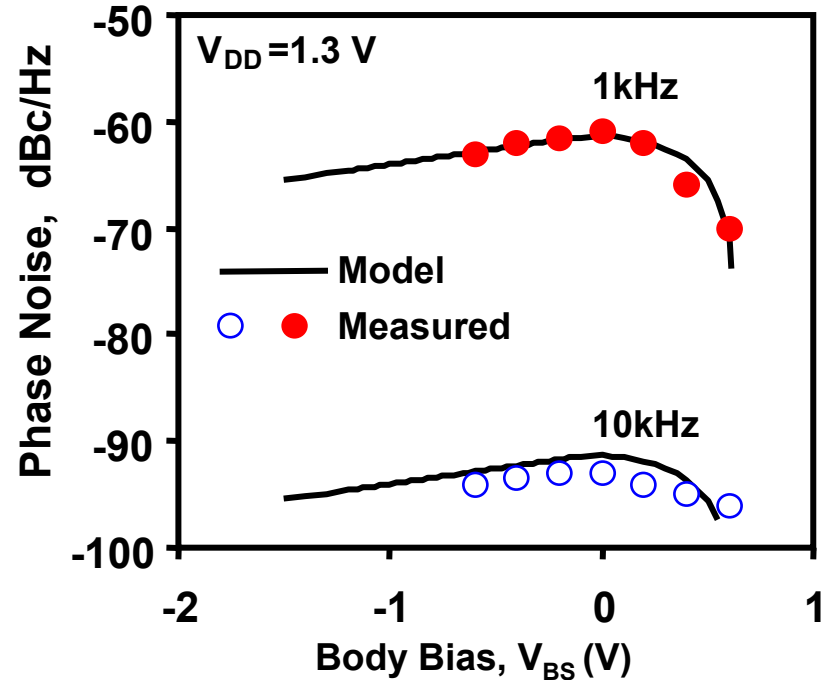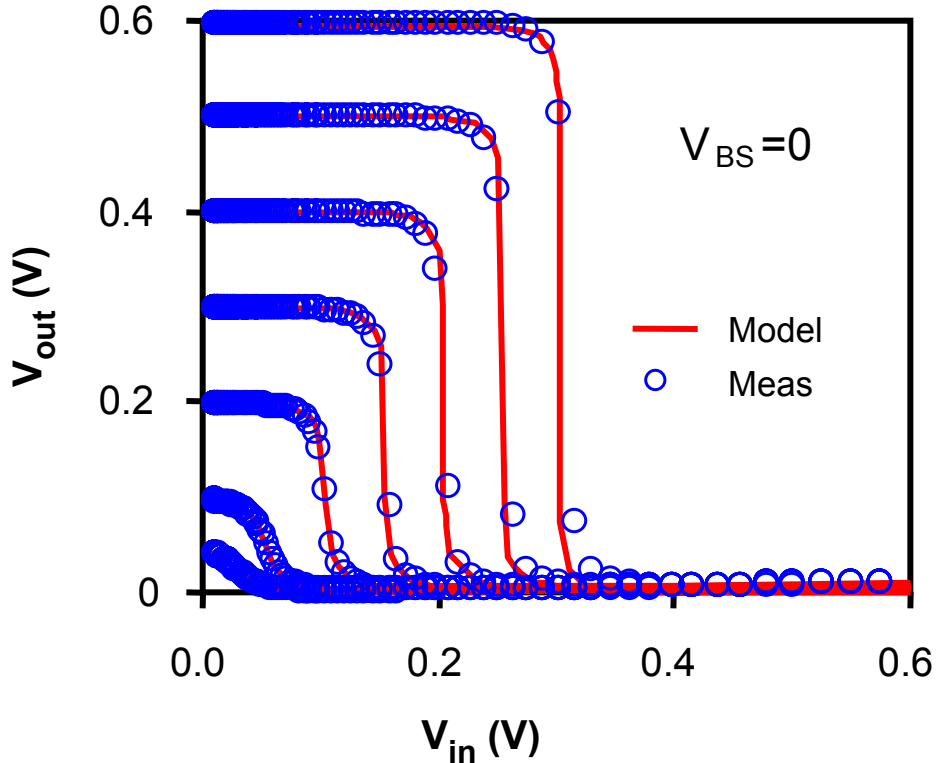

Measurement: RO VCO functional down to **~80 mV** supply voltage.

Body voltage can affect the **phase noise** in ring oscillator

Conclusions

- **Low voltage mixers**

- ◆ Gilbert cell and body-input mixers (0.8V, 0.4mW)

- **Oscillators**

- ◆ VCO with AAC and micro-power VCO (0.4V, 40 μ W)

- **Hot-carrier effects on LNAs**

- ◆ Reduced gain, increased noise figure

- **Mismatch effects on oscillator**

- **Trends- deep subthreshold oscillator**

Thank

You!

