 

SRAM Design




Chapter Overview

- **Memory Classification**
- **Memory Architectures**
- **The Memory Core**
- **Periphery**
- **Reliability**

Semiconductor Memory Classification

RWM		NVRWM	ROM
Random Access	Non-Random Access	EPROM E ² PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		

Memory Architecture: Decoders

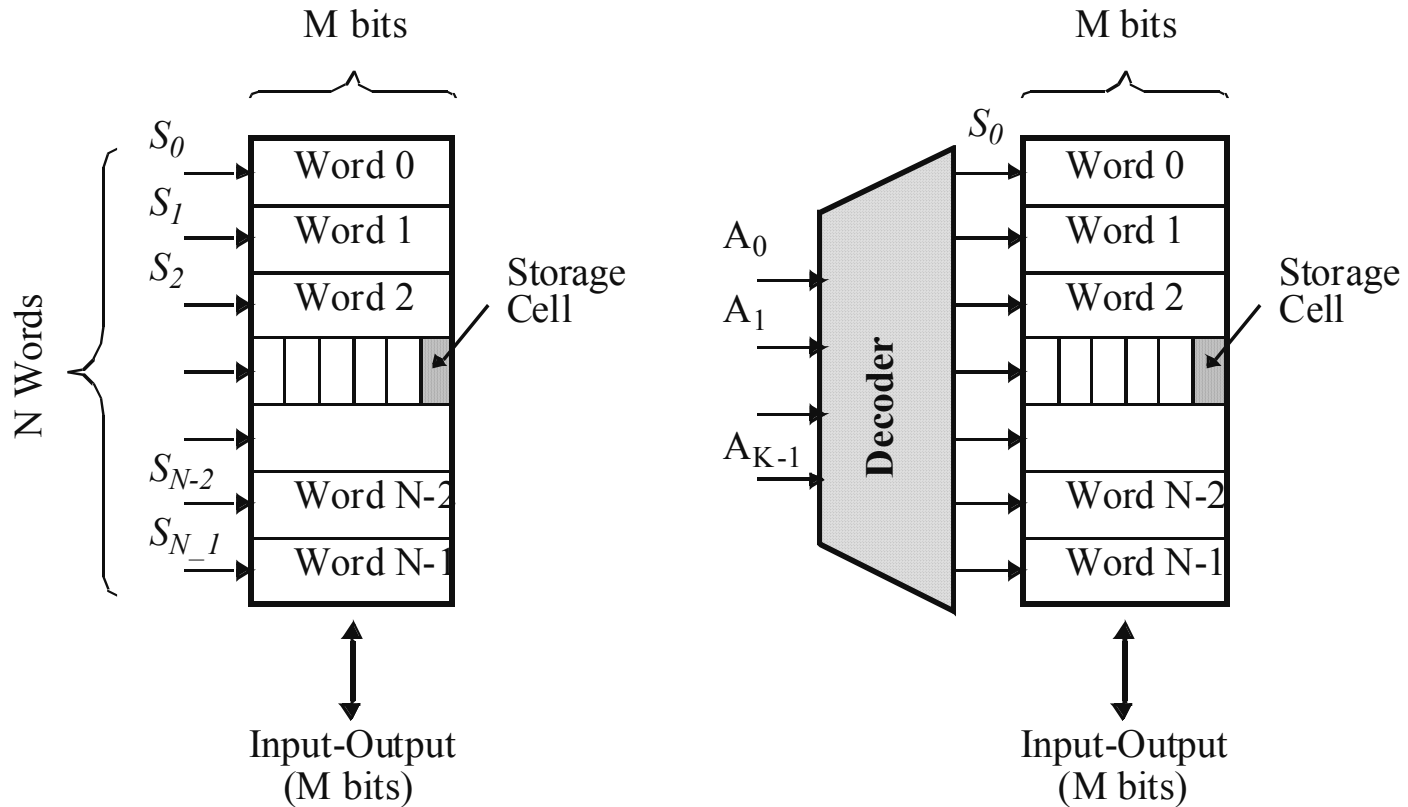


N words $\Rightarrow N$ select signals
Too many select signals


Decoder reduces # of select signals
 $K = \log_2 N$

Array-Structured Memory Architecture

Problem: ASPECT RATIO or HEIGHT >> WIDTH

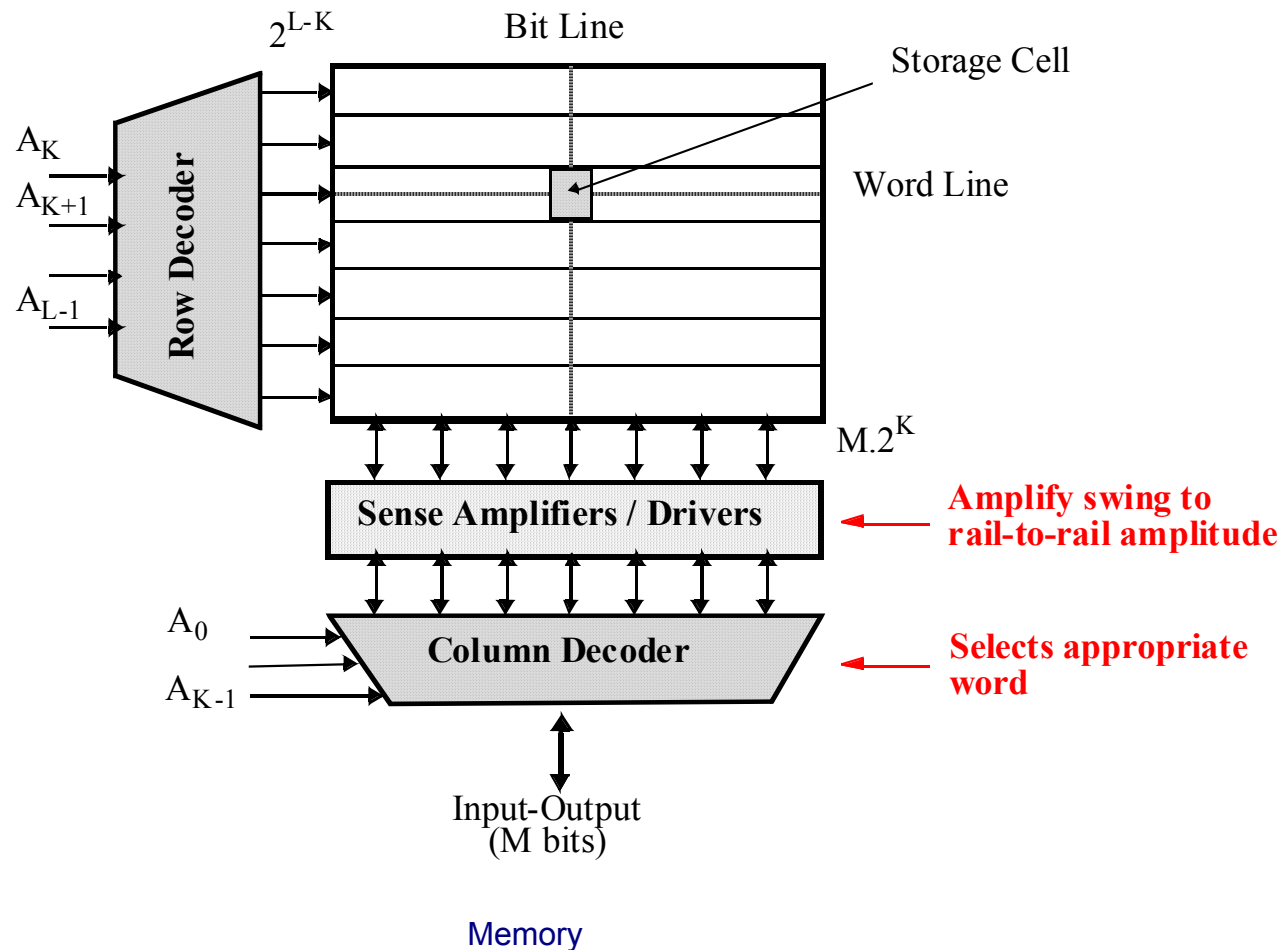


Hierarchical Memory Architecture

 


Advantages:

1. Shorter wires within blocks
2. Block address activates only 1 block => power savings


Memory Timing: Definitions

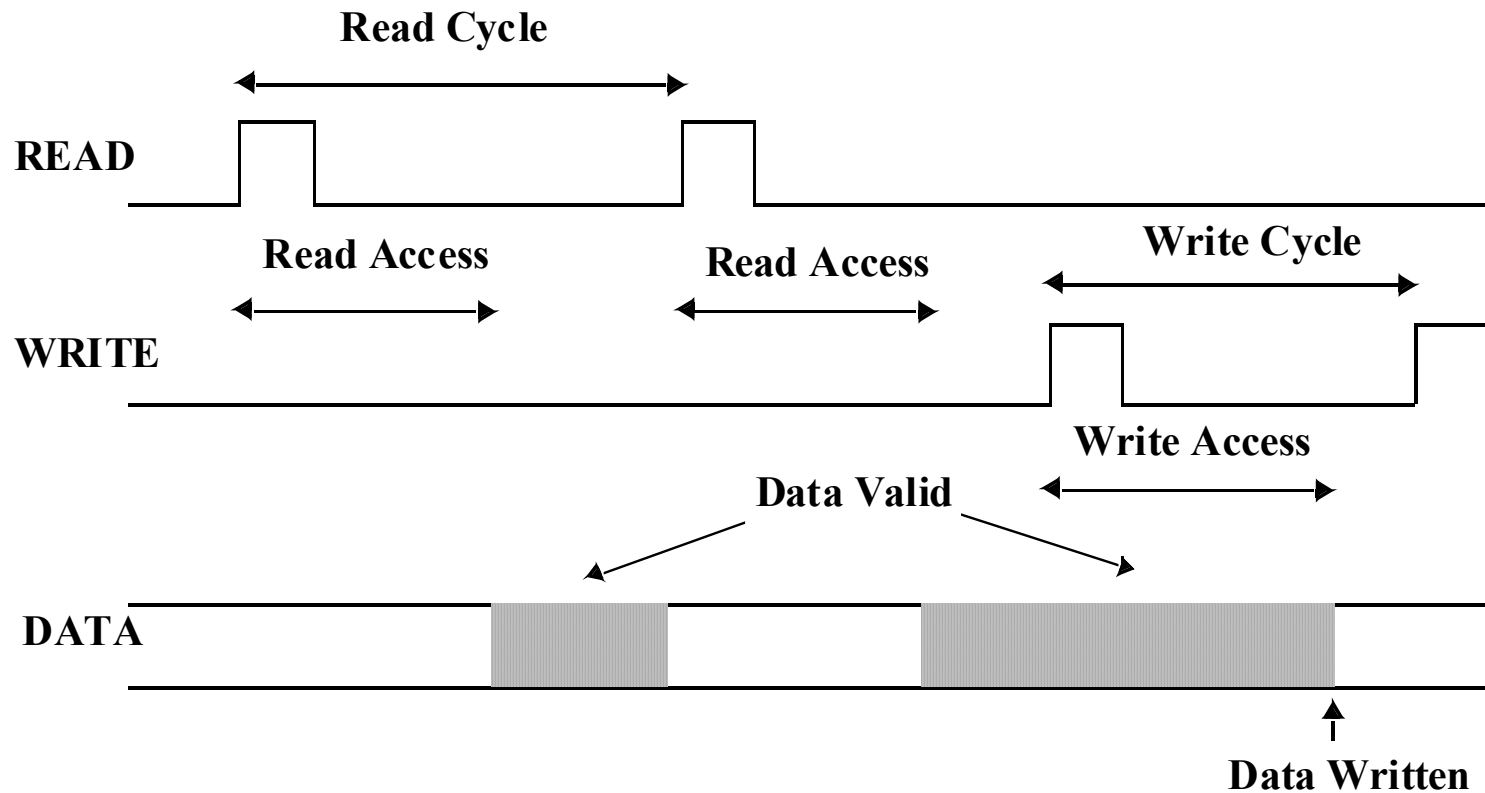

Memory Timing: Approaches

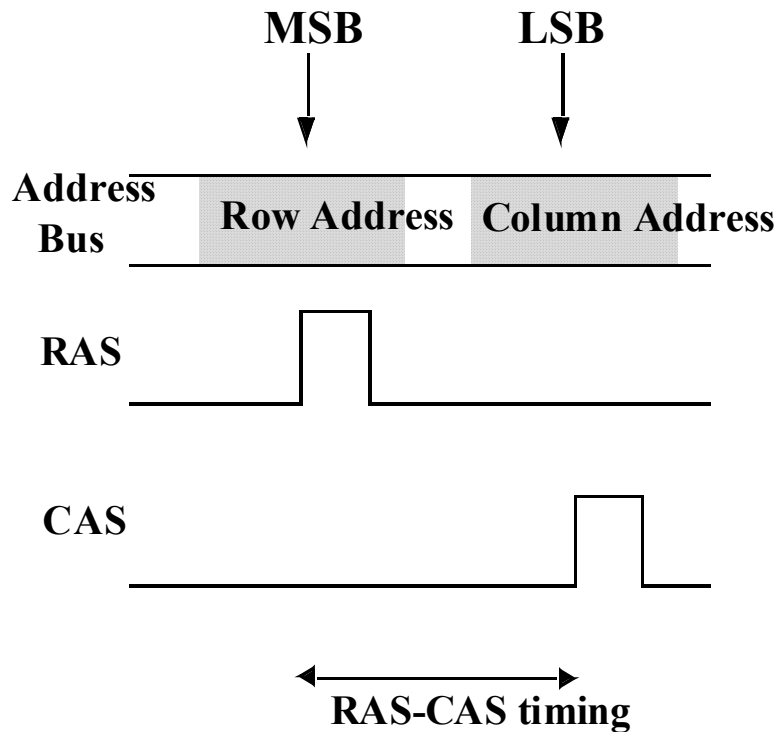

DRAM Timing
Multiplexed Addressing

 

SRAM Timing
Self-timed

Read-Write Memories (RAM)

- **STATIC (SRAM)**

 - Data stored as long as supply is applied**

 - Large (6 transistors/cell)**

 - Fast**

 - Differential**

- **DYNAMIC (DRAM)**


 - Periodic refresh required**

 - Small (1-3 transistors/cell)**

 - Slower**


 - Single Ended**

6-transistor CMOS SRAM Cell

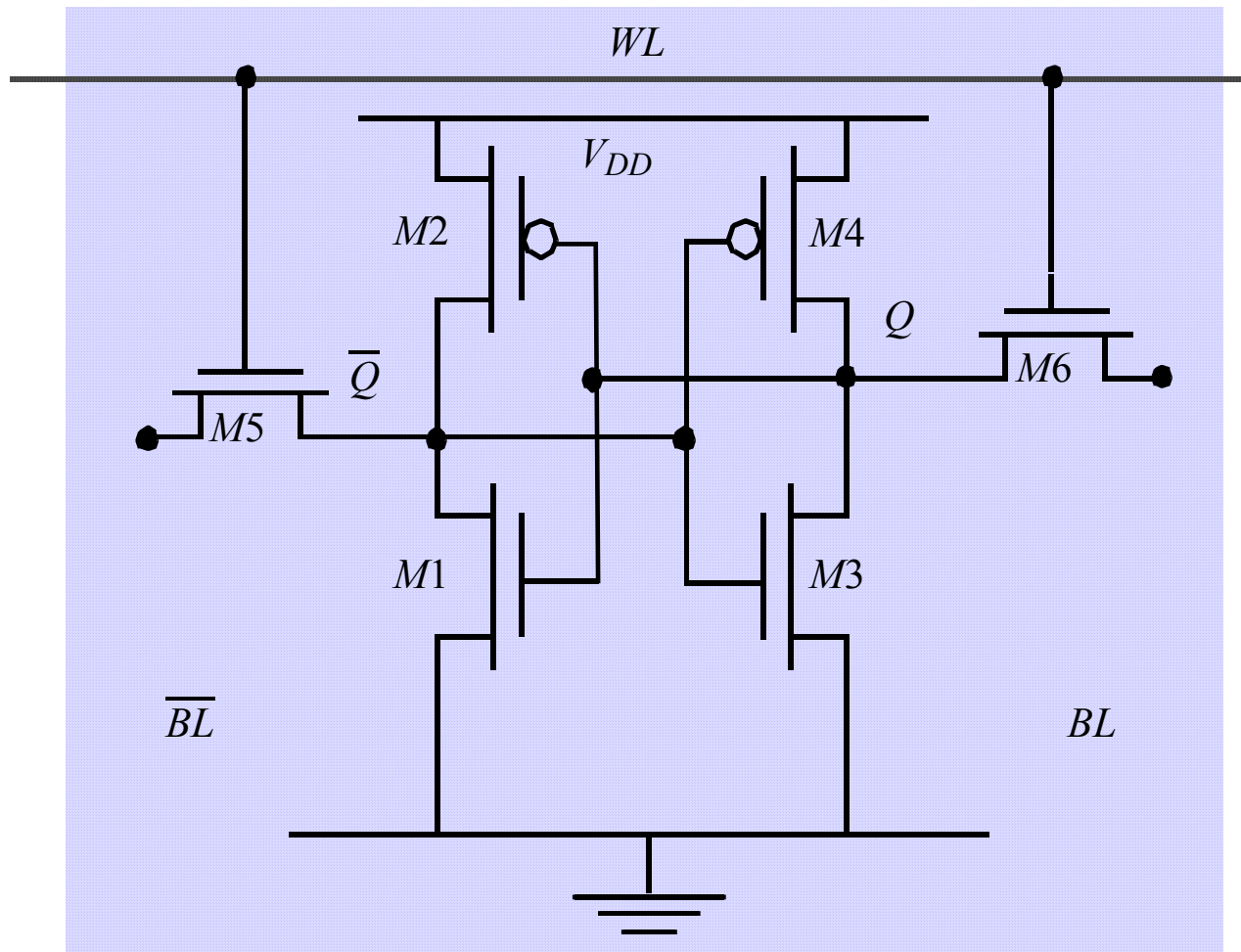

Memory

CMOS SRAM Analysis (Write)

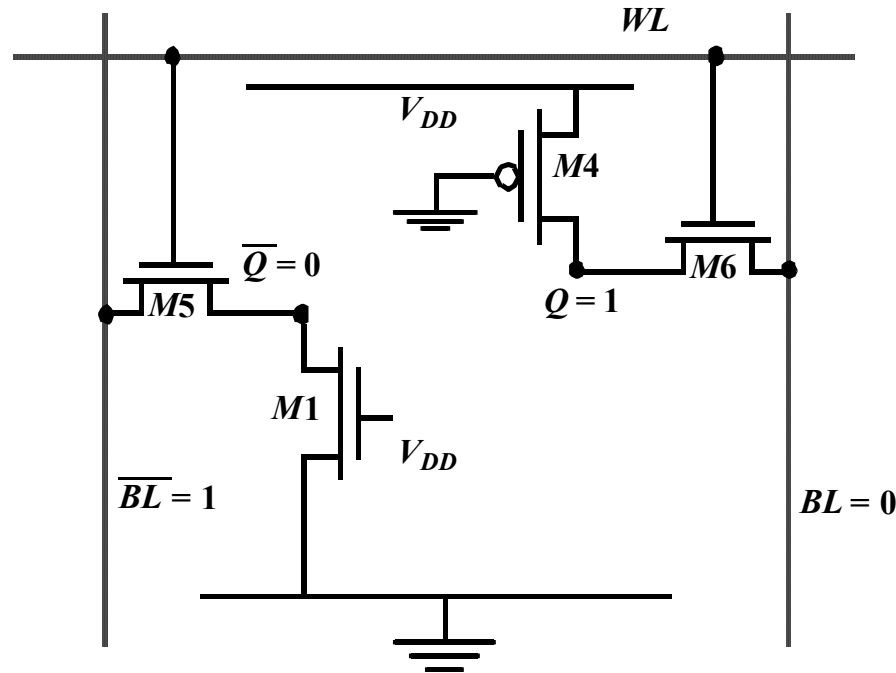


$$k_{n, M6} \left((V_{DD} - V_{Tn}) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{8} \right) = k_{p, M4} \left((V_{DD} - |V_{Tp}|) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{8} \right)$$

$$(W/L)_{n, M6} \geq 0.33 (W/L)_{p, M4}$$

$$\frac{k_{n, M5}}{2} \left(\frac{V_{DD}}{2} - V_{Tn} \left(\frac{V_{DD}}{2} \right) \right)^2 = k_{n, M1} \left((V_{DD} - |V_{Tn}|) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{8} \right)$$

$$(W/L)_{n, M5} \geq 10 (W/L)_{n, M1}$$


CMOS SRAM Analysis (Read)

 

$$\frac{k_{n,M5}}{2} \left(\frac{V_{DD}}{2} - V_{Tn} \left(\frac{V_{DD}}{2} \right) \right)^2 = k_{n,M1} \left((V_{DD} - |V_{Tn}|) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{8} \right)$$


$(W/L)_{n,M5} \leq 10 (W/L)_{n,M1}$ (supercedes read constraint)

6T-SRAM – Layout

 

Memory

Resistance-load SRAM Cell

 

Static power dissipation -- Want R_L large
Bit lines precharged to V_{DD} to address t_p problem

Periphery

- **Decoders**
- **Sense Amplifiers**
- **Input/Output Buffers**
- **Control / Timing Circuitry**

Row Decoders

Collection of 2^M complex logic gates
Organized in regular and dense fashion

(N)AND Decoder

$$WL_0 = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$


$$WL_{511} = \bar{A}_0 \bar{A}_1 \bar{A}_2 \bar{A}_3 \bar{A}_4 \bar{A}_5 \bar{A}_6 \bar{A}_7 \bar{A}_8 \bar{A}_9$$

NOR Decoder

$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$


$$WL_{511} = \overline{A_0 + \bar{A}_1 + \bar{A}_2 + \bar{A}_3 + \bar{A}_4 + \bar{A}_5 + \bar{A}_6 + \bar{A}_7 + \bar{A}_8 + \bar{A}_9}$$

Dynamic Decoders

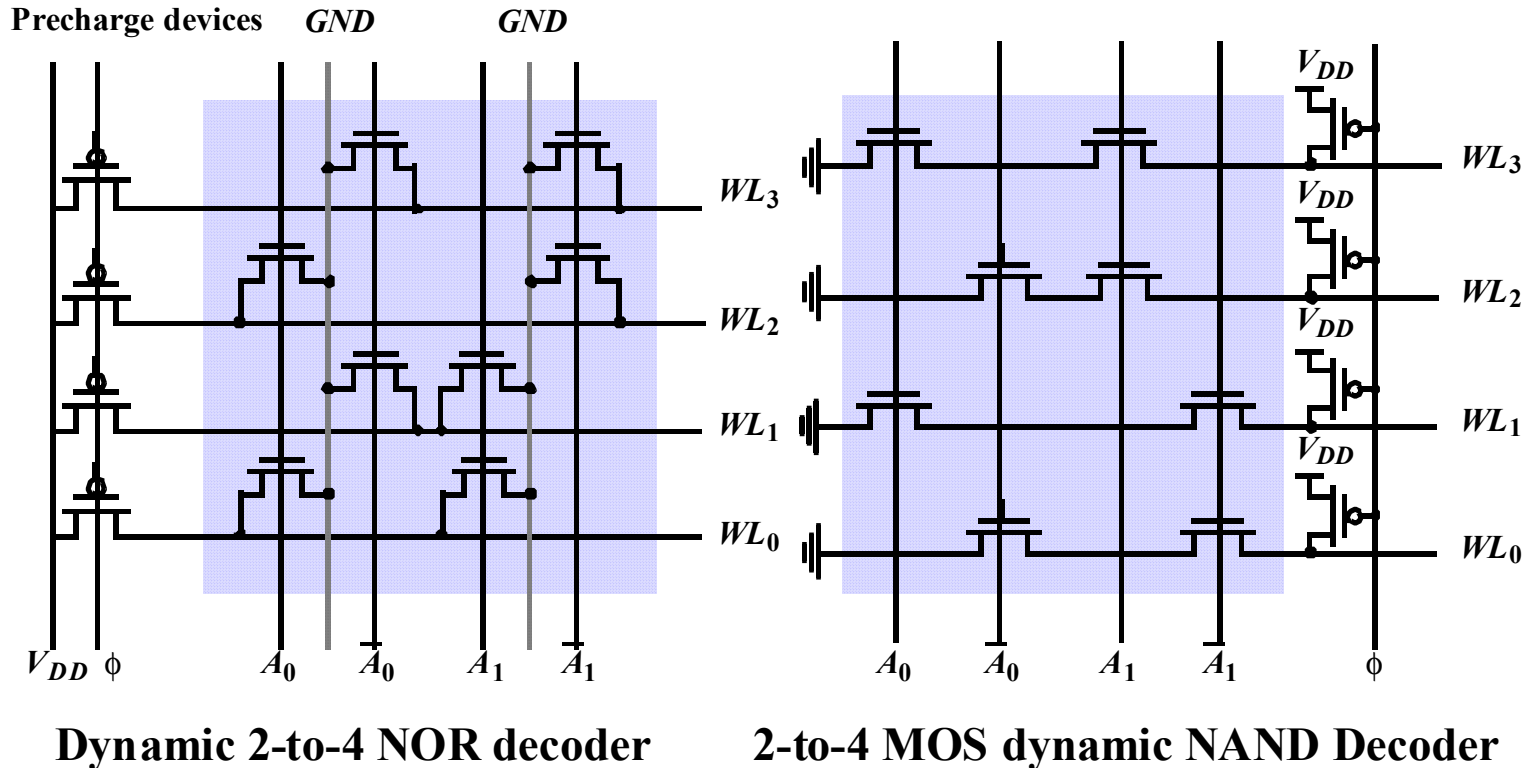


Propagation delay is primary concern

 A NAND decoder using 2-input pre-decoders



Splitting decoder into two or more logic layers produces a faster and cheaper implementation

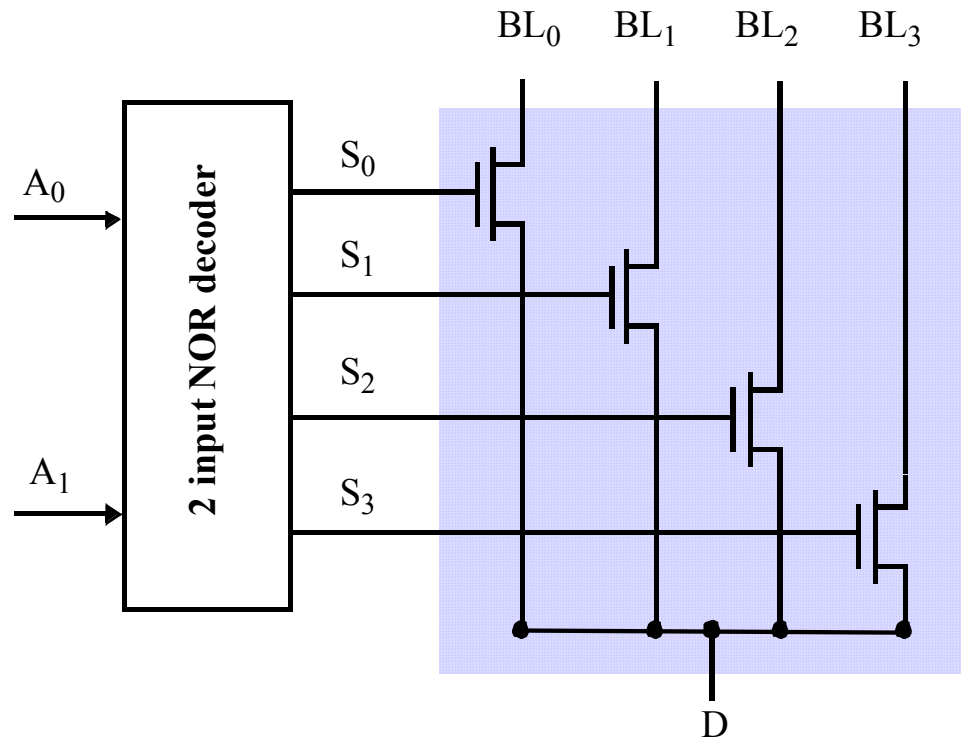
4 input pass-transistor based column decoder



Advantage: speed (t_{pd} does not add to overall memory access time)
only 1 extra transistor in signal path

Disadvantage: large transistor count

4-to-1 tree based column decoder

 

Number of devices drastically reduced


Delay increases quadratically with # of sections; prohibitive for large decoders

Solutions: buffers

progressive sizing

combination of tree and pass transistor approaches

Decoder for circular shift-register

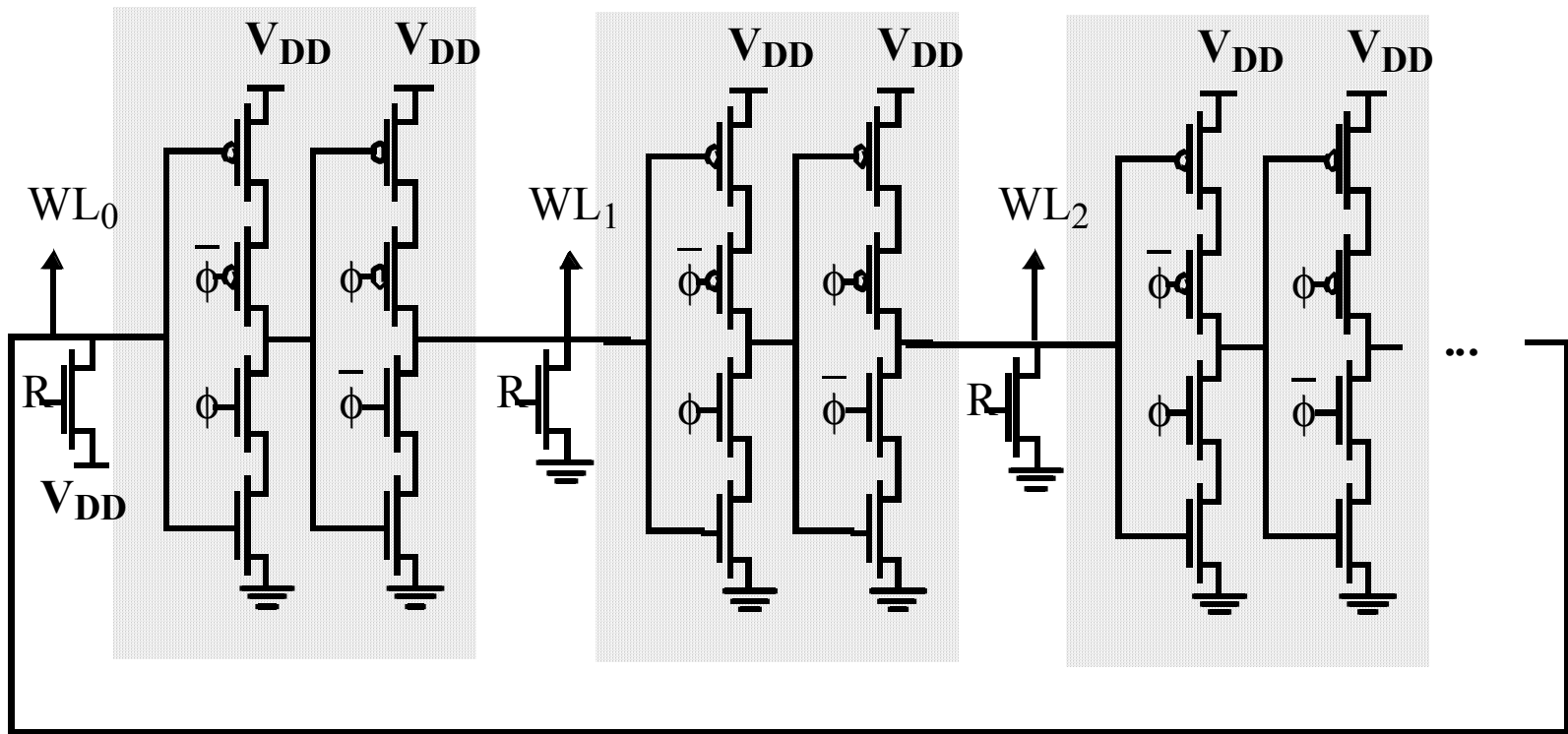

Sense Amplifiers


$$t_p = \frac{C \cdot \Delta V}{I_{av}}$$

make ΔV as small as possible


large

small


Idea: Use Sense Amplifier

 


Differential Sensing - SRAM

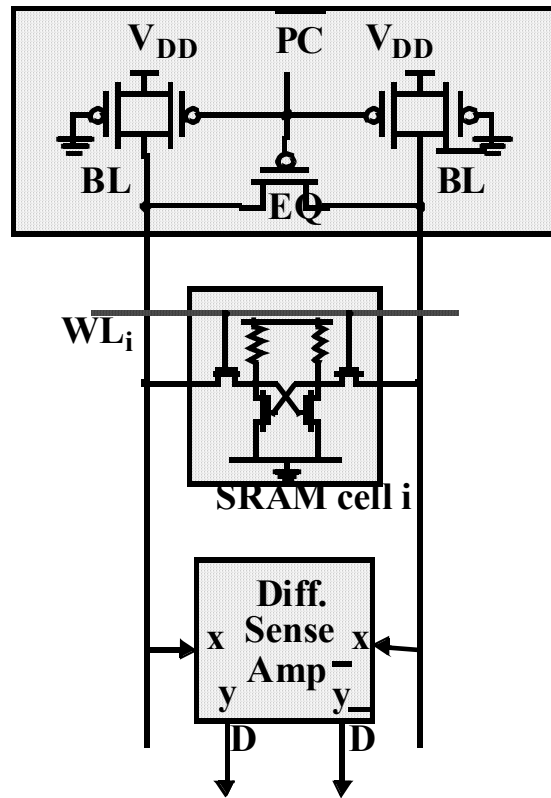

(a) SRAM sensing scheme.

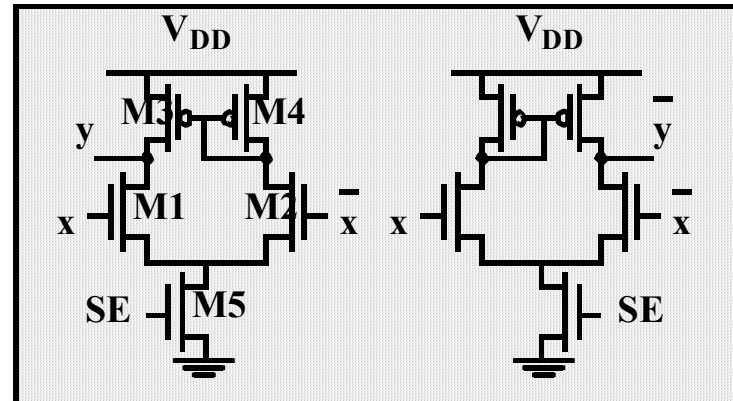


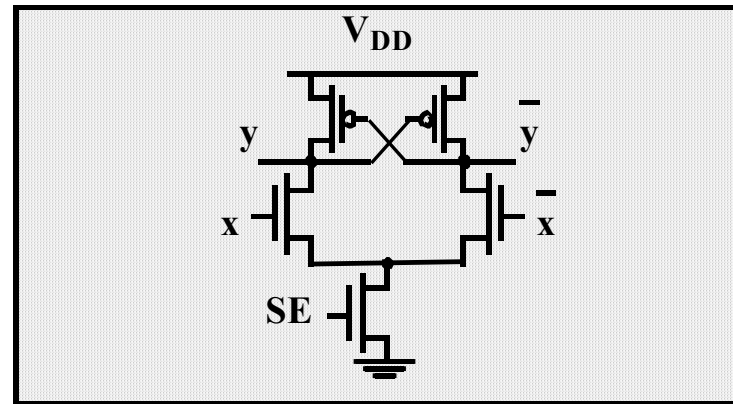(b) Doubled-ended Current Mirror Amplifier




(c) Cross-Coupled Amplifier

Latch-Based Sense Amplifier

 


Initialized in its meta-stable point with EQ
Once adequate voltage gap created, sense amp enabled with SE
Positive feedback quickly forces output to a stable operating point.

Single-to-Differential Conversion

 


How to make good V_{ref} ?

Address Transition Detection

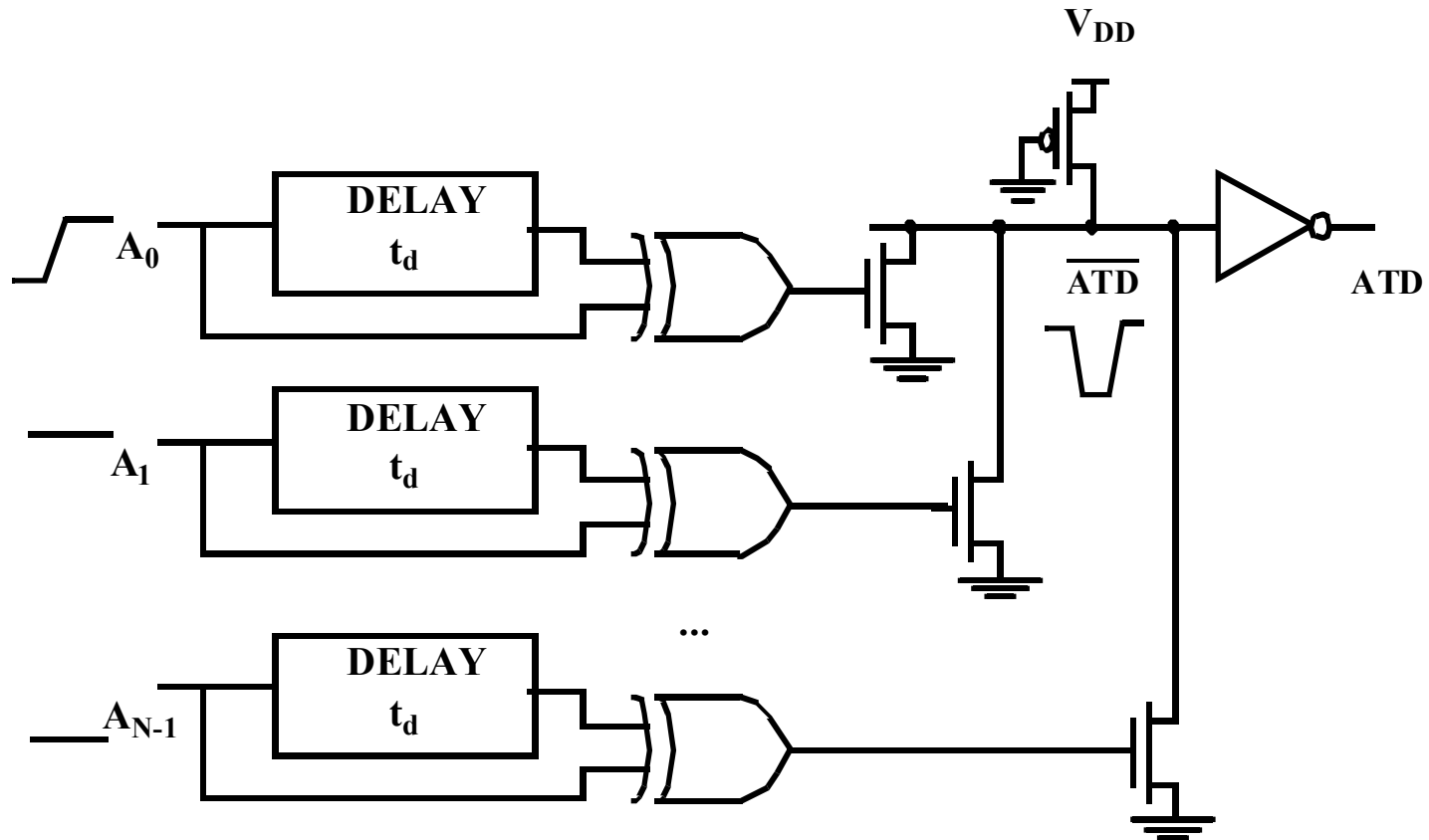

Reliability and Yield

 - Semiconductor memories trade off noise-margin for density and performance



Highly Sensitive to Noise (Crosstalk, Supply Noise)


- High Density and Large Die size cause Yield Problems

$$Y = 100 \frac{\text{Number of Good Chips on Wafer}}{\text{Number of Chips on Wafer}}$$


$$Y = \left[\frac{1 - e^{-AD}}{AD} \right]^2$$

Increase Yield using Error Correction and Redundancy

 
Open Bit-line Architecture – Cross Coupling




Folded-Bitline Architecture

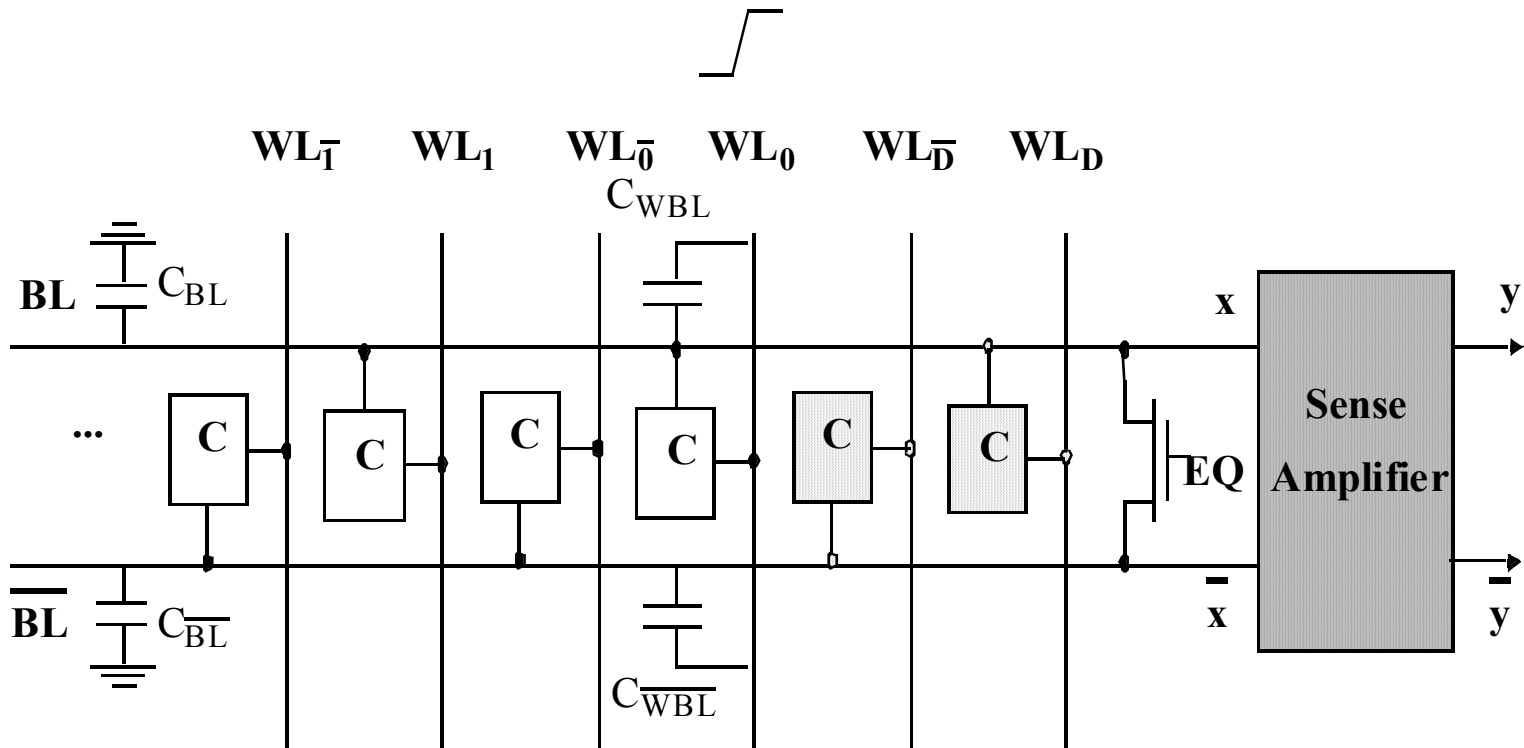

Transposed-Bitline Architecture

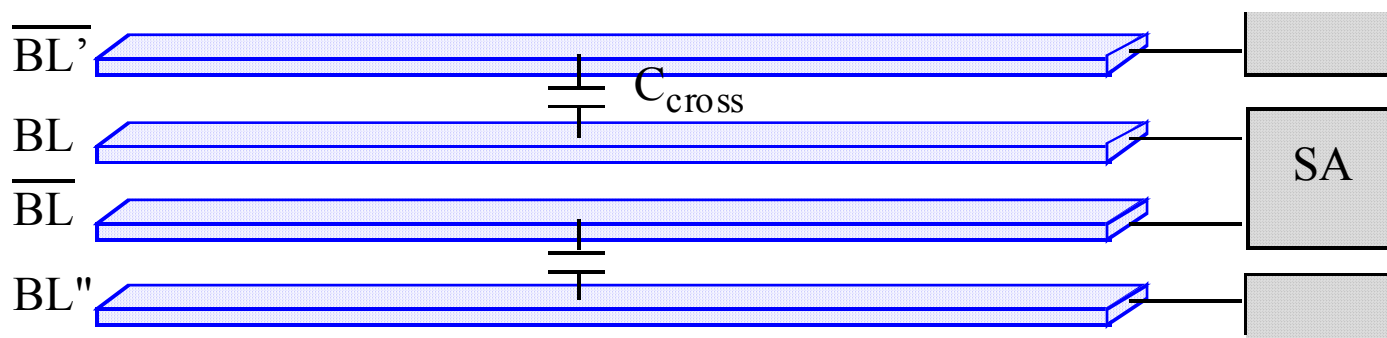


(a) Straightforward bitline routing.

 


(b) Transposed bitline architecture.

Alpha-particles

 


1 particle ~ 1 million carriers

Yield

 


Yield curves at different stages of process maturity
(from [Veendrick92])

Redundancy

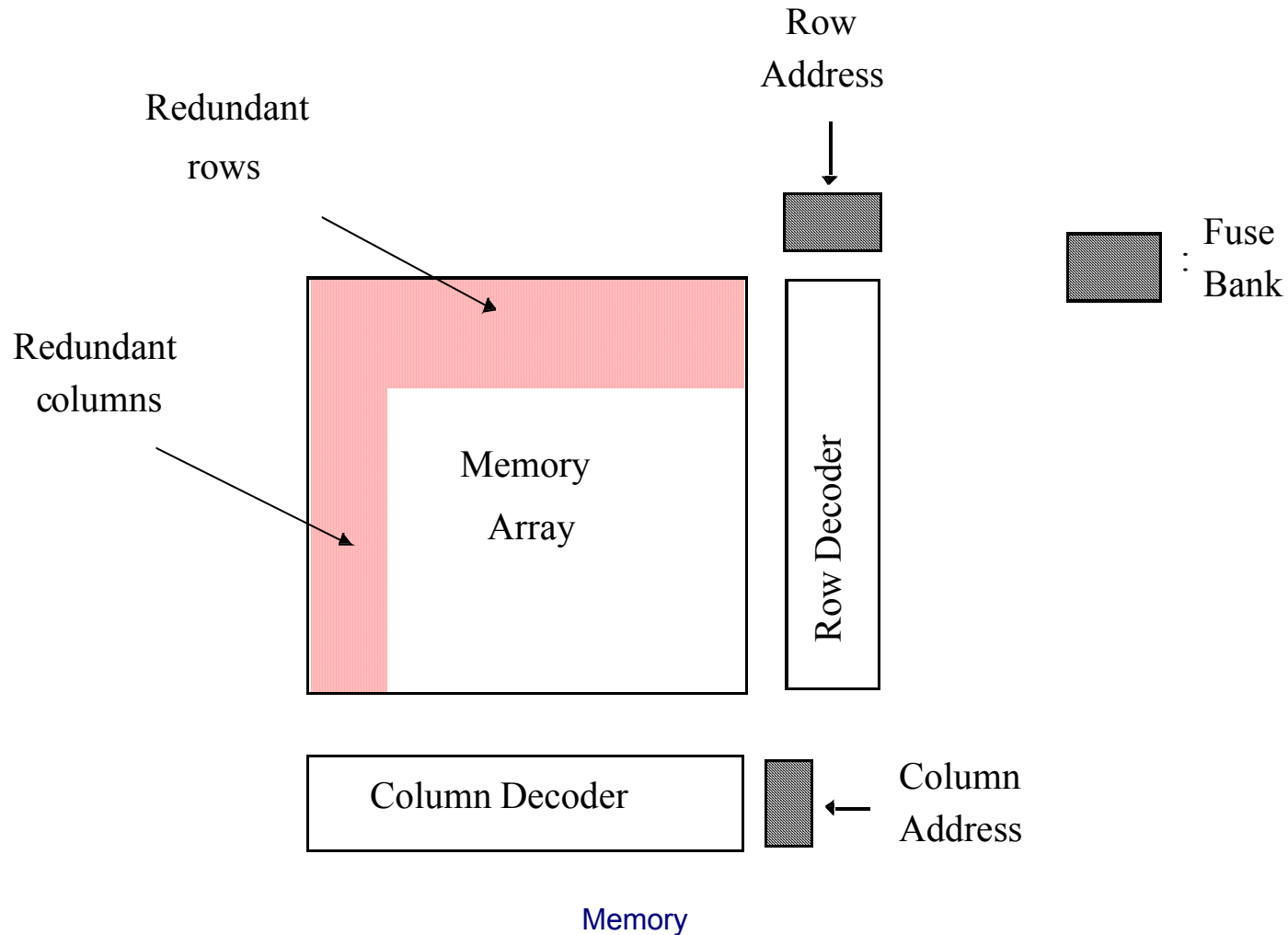


Semiconductor Memory Trends

 


Memory Size as a function of time: x 4 every three years

Semiconductor Memory Trends

 

Increasing die size
factor 1.5 per generation
Combined with reducing cell size
factor 2.6 per generation

Semiconductor Memory Trends

 

Technology feature size for different SRAM generations

Memory