

ECE-223, Assignment #3

Chapter 3, Digital Design, M. Mano, 3rd Edition

3.3) Simplify the following Boolean functions, using three-variable maps:

- a) $xy + x'y'z' + x'yz'$
- b) $x'y' + yz + x'yz'$
- c) $A'B + BC' + B'C'$

3.5) Simplify the following Boolean functions, using four-variable maps:

- a) $F(w, x, y, z) = \sum (1, 4, 5, 6, 12, 14, 15)$
- b) $F(A, B, C, D) = \sum (0, 1, 2, 4, 5, 7, 11, 15)$
- c) $F(w, x, y, z) = \sum (2, 3, 10, 11, 12, 13, 14, 15)$
- d) $F(A, B, C, D) = \sum (0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$

3.12) Simplify the following Boolean functions in products of sums:

- a) $F(w, x, y, z) = \sum (0, 2, 5, 6, 7, 8, 10)$
- b) $F(A, B, C, D) = \prod (1, 3, 5, 7, 13, 15)$

3.13) Simplify the following expressions in (1) sum of the products and (2) products of sums:

- a) $x'z' + y'z' + yz' + xy$
- b) $AC' + B'D + A'CD + ABCD$
- c) $(A' + B' + D')(A + B' + C')(A' + B + D')(B + C' + D')$

3.15) Simplify the following Boolean function F , together with the don't-care conditions d , and then express the simplified function in sum of minterms:

- a) $F(x, y, z) = \sum (0, 1, 2, 4, 5)$, $d(x, y, z) = \sum (3, 6, 7)$
- b) $F(A, B, C, D) = \sum (0, 6, 8, 13, 14)$, $d(A, B, C, D) = \sum (2, 4, 10)$
- c) $F(A, B, C, D) = \sum (1, 3, 5, 7, 9, 15)$, $d(A, B, C, D) = \sum (4, 6, 12, 13)$

3.16) Simplify the following expressions, and implement them with two-level NAND gate circuits:

- a) $ABZ + ABD + ABD' + A'C'D' + A'BC'$
- b) $BD + BCD' + AB'C'D'$

3.28) Derive the circuits for a three-bit parity generator and four-bit parity checker using odd parity bit.

3.29) Implement the following four Boolean expressions with three half adders

- a) $D = A \oplus B \oplus C$
- b) $E = A'BC + AB'C$
- c) $F = ABC' + (A' + B')C$
- d) $G = ABC$