



Assignment #4 E & CE 223

E&CE 223
Assignment 4 - Solutions

1. Mano 4.1, 4.19


Mano 4.1

xyz	F
000	1
001	1
010	1
011	0
100	0
101	0
110	0
111	0

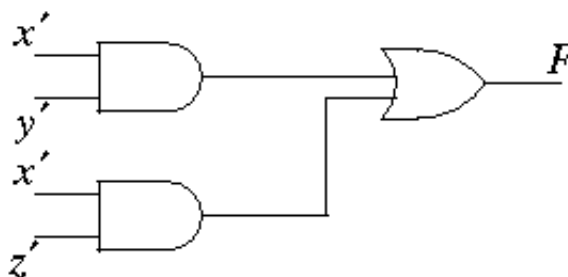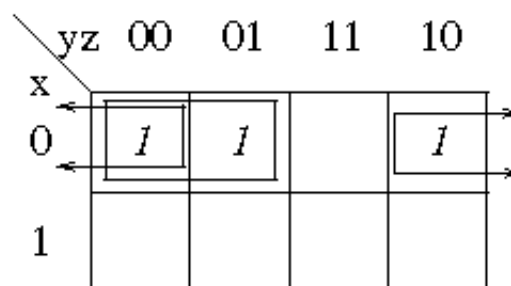


Mano 4.19

(a) $F = (A'B + CD)E + BC(A+B)$

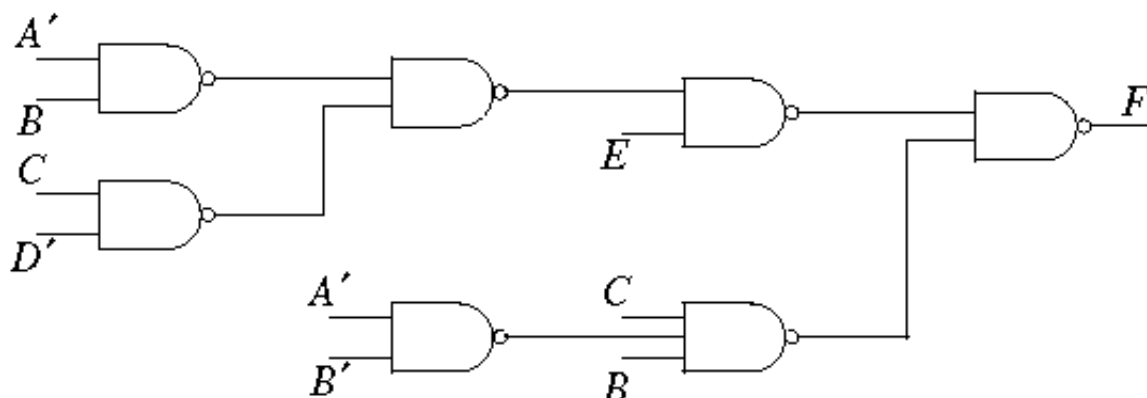

(b) $F = w(x+y+z) + xyz$

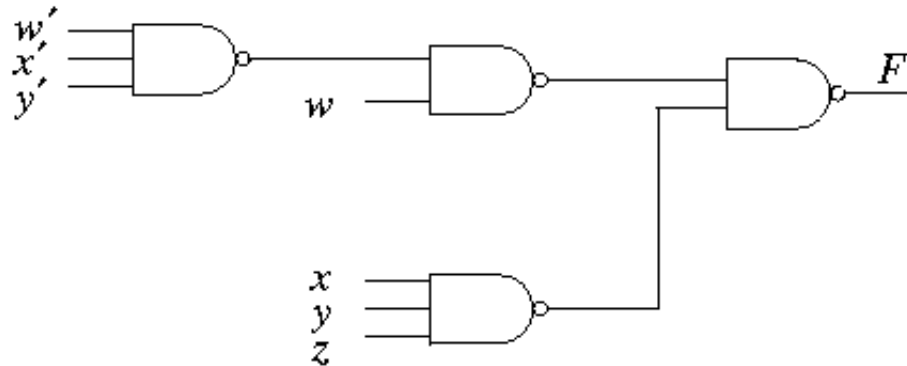


2. Using AND and OR gates find the circuit that minimizes the number of gate inputs for the function:

$$f(u,w,x,y,z) = uy + uw' + xyz + x'yz' + w'x'z'$$


[2 levels, 6 gates, 18 inputs]

$$\begin{aligned} f(u,w,x,y,z) &= w'(u + x'z') + y(u+x'z') + xyz \\ &= w'(u+x'z') + y(u+x'z') + xy(y+w')z \\ &= w'(u + x'z'+xyz) + y(u+x'z'+xyz) \\ &= (w'+y)(u+x'z'+xyz) \end{aligned}$$

[3 levels, 5 gates 12 inputs]

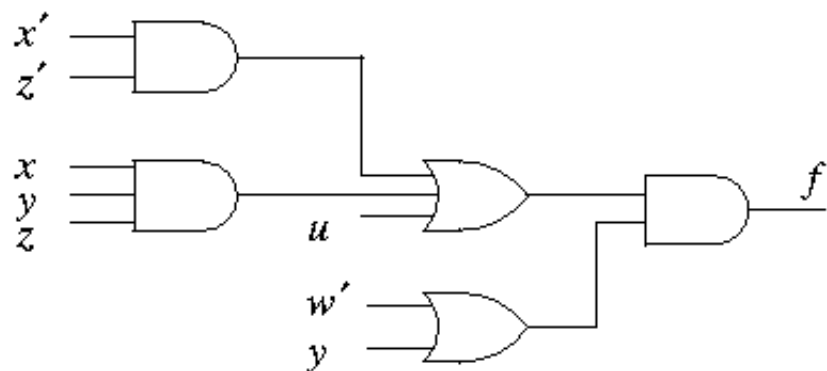

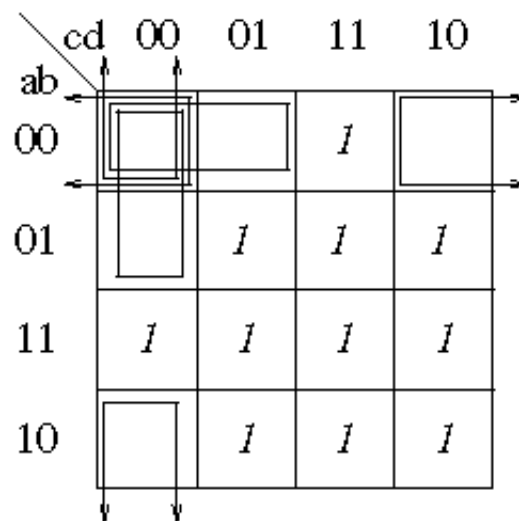3. A function $F(a,b,c,d)$ is 1 if more than one of its inputs is 1.
 (a) Write the maxterm expression for $F(a,b,c,d)$



$$F(a,b,c,d) = \prod(0, 1, 2, 4, 8)$$


- (b) Find the minimum gate three level (AND-OR-AND) circuit.
 Start with product-of-sums

$$F' = a'b'c' + a'b'd' + a'c'd' + b'c'd'$$

$$F = (a+b+c)(a+b+d)(a+c+d)(b+c+d)$$

$$= ([a+b]+c)([a+b]+d)(a+[c+d])(b+[c+d])$$

$$= ([a+b]+cd)(ab+[c+d])$$

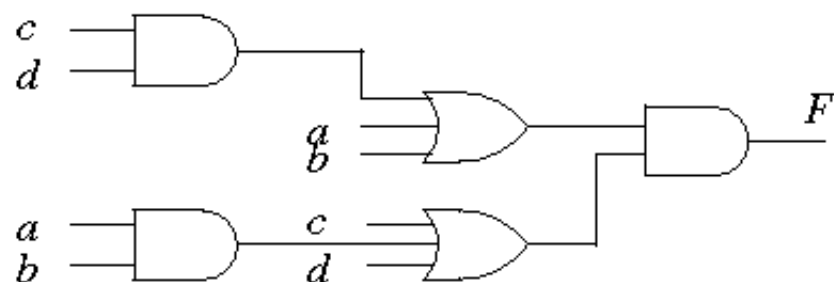

[3 levels, 5 gates, 12 inputs]

4. Realize the following functions using only 2-input NAND gates. Repeat for 2-input NOR gates.


NAND

$$\begin{aligned} \text{(a) } f(w,x,y,z) &= w'y' + wyz + x'y'z' + xz \\ &= y'(w'+x'z') + z wy + x \end{aligned}$$


[now using DeMorgan's theorem]

$$= (\{y'(w[x'z']')\}'\{z([wy]'x')'\})'$$

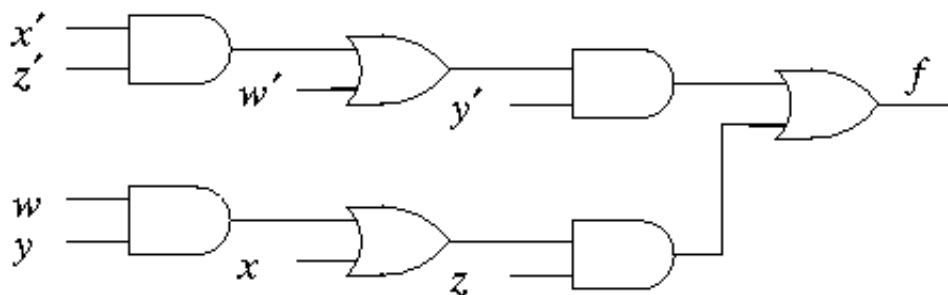from which the NAND circuit below can be drawn or (more simply) draw AND-OR circuit



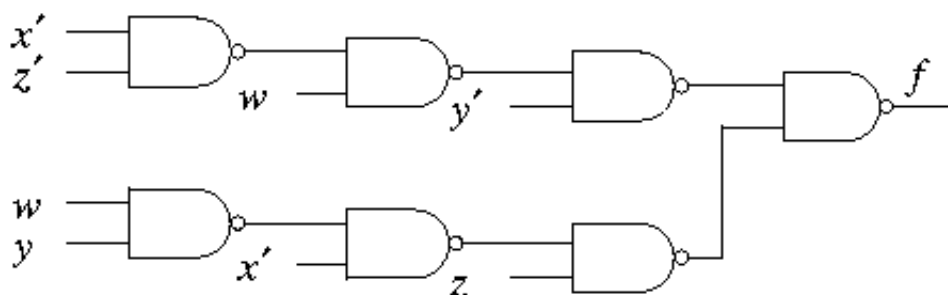insert inverter bubbles and replace with NANDs




NB: Note inputs to third level have been complemented compared to AND-OR-AND-OR circuit.

(b) A straight forward factoring would proceed as follows:


$$\begin{aligned}
 f(w,x,y,z) &= w'x'z + w'xyz' + wxy' + y'z \\
 &= w'[x'z + xyz'] + y'[wx+z] \\
 &= w'[x'z+x(yz')] + y'[wx+z]
 \end{aligned}$$

Note: 3-input AND was split into two 2-input ANDS

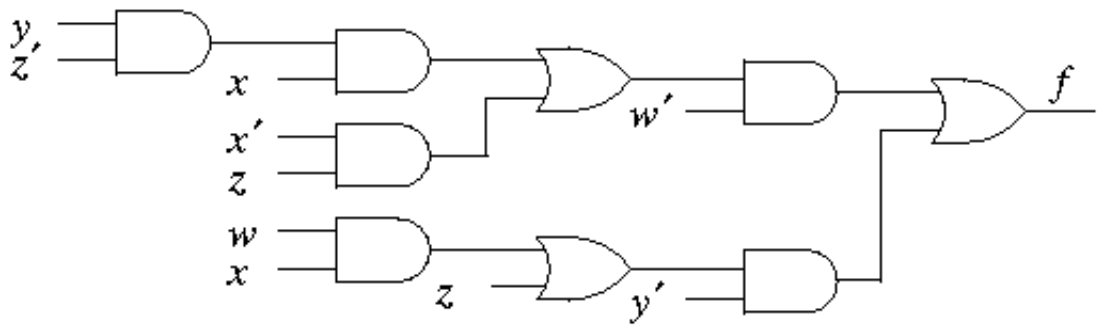

Nine 2-input ANDs required (5 levels).

Insert inverter bubbles and replace gates with NAND. An extra gate is required in the AND-AND sequence.

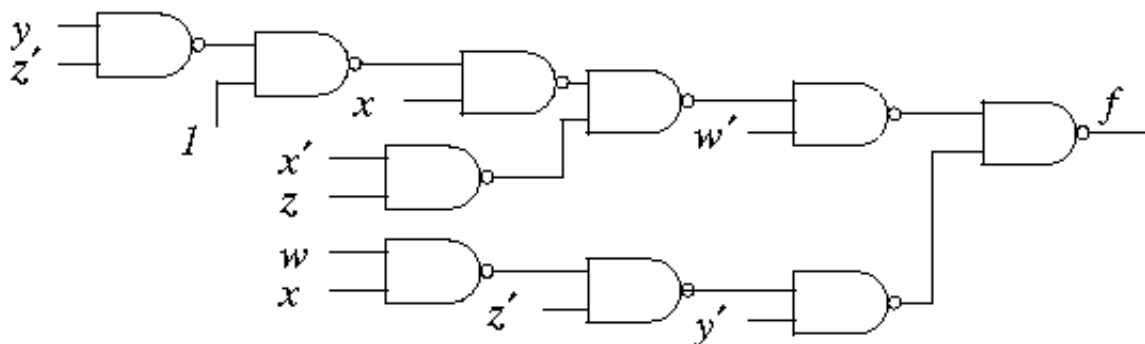

Ten 2-input NAND gates required (6 levels).

A better factoring is suggested by inspecting the Karnaugh map.

	yz	00	01	11	10
wx	00		1	1	
	01		1		1
	11	1	1		
	10		1		

There are four minterms in XOR patterns. The following algebra obtains those XOR expressions.

$$\begin{aligned}
 f(w,x,y,z) &= w'x'z + w'xyz' + wxy' + y'z \\
 &= w'x'z(y+y') + w'xyz' + wxy'(z+z') + y'z \\
 &= w'x'yz + w'xyz' + wxy'z' + wx'y'z + y'z \\
 &= w'y(x'z+xz') + wy'(xz'+x'z) + y'z \\
 &= (w'y+wy')(xz'+x'z) + y'z
 \end{aligned}$$

The above factoring can be visualized by "factoring" the Karnaugh map:


		1	1		
		1	1		
1	1				
1	1				

•

		1	1		
1				1	
1				1	
		1	1		


+

		1			
		1			
		1			
		1			

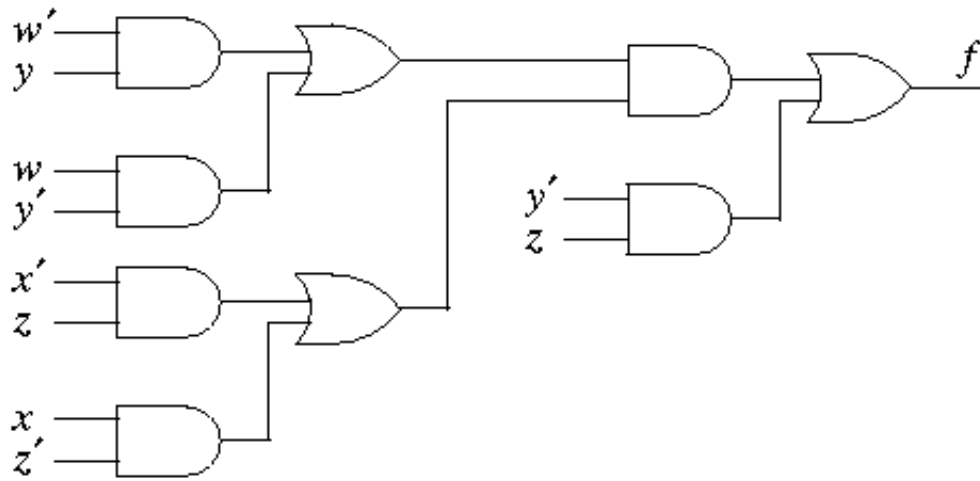

Nine 2-input gates required (4 levels).

Inserting inverter bubbles and converting to NAND gates yields:

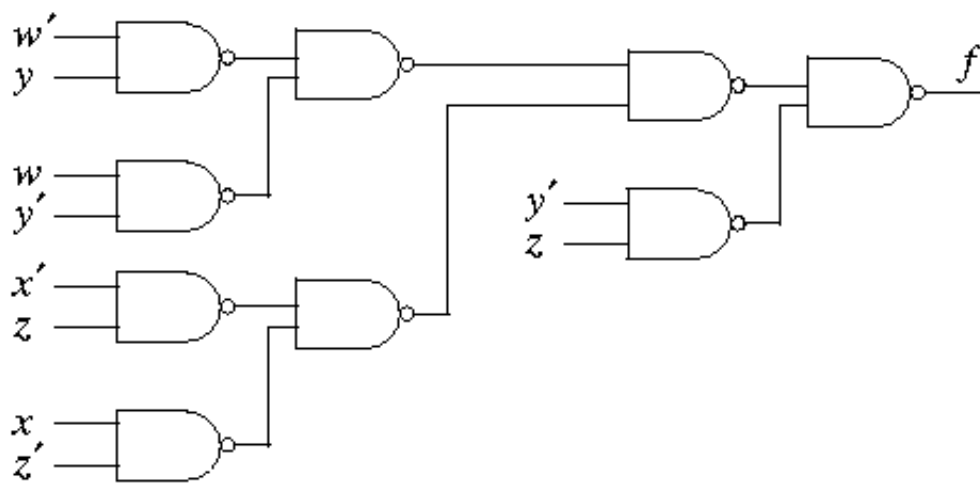

Nine 2-input NAND gates required.

NOR

(a) $f(w,x,y,z) = w'y' + wyz + x'y'z' + xz$

	yz	00	01	11	10
wx	00	1	1		
01		1	1	1	
11			1	1	
10		1		1	

$$f'(w,x,y,z) = yz' + w'x'y + wxz' + wx'y'z$$

$$f(w,x,y,z) = (y'+z)(w+x+y')(w'+x'+z)(w'+x+y+z')$$

$$= (y'+z)(w+x+y'+z')(w+x+y'+z)$$

$$(w'+x'+z+y')(w'+x'+z+y)(w'+x+y+z')$$


$$= (y'+z)(w+x+y'+z')(w'+x'+z+y)(w'+x+y+z')$$

$$= (y'+z)(x+z'+[w+y'] [w'+y])(w'+x'+z+y)$$


$$= (y'+z)(x+z'+[w+y'] [w'+y])(w'+x'+z+y)(w+x'+z+y')$$

$$= (y'+z)(x+z'+[w+y'] [w'+y])(x'+z+[w+y'] [w'+y])$$
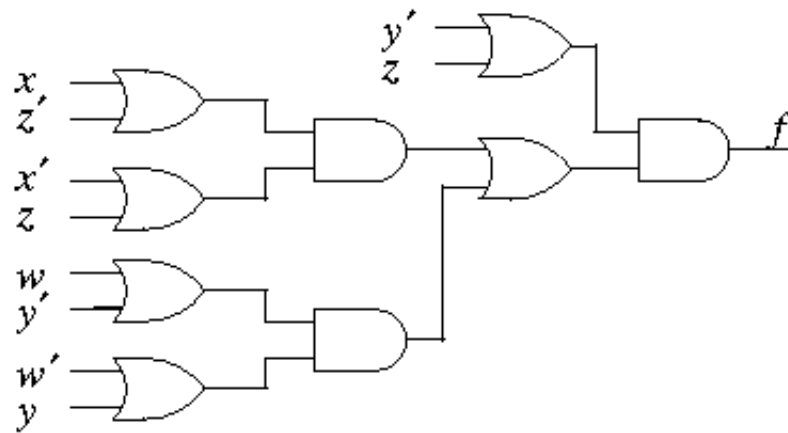
$$= (y'+z)([x+z'] [x'+z] + [w+y'] [w'+y])$$



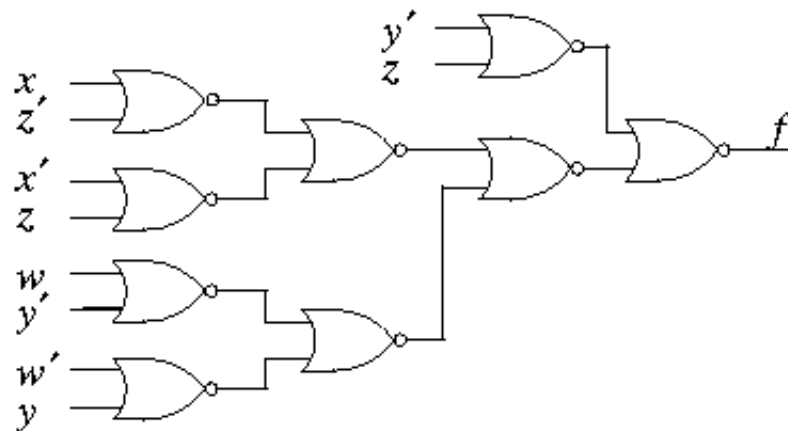Insert inverter bubbles and convert to NOR gates:




(b) $f(w,x,y,z) = w'x'z + w'xyz' + wxy' + y'z$

wx \ yz	00	01	11	10
00		1	1	
01		1		1
11	1	1		
10		1		

$$f'(w,x,y,z) = wy + x'z' + w'y'z' + xyz$$

$$f(w,x,y,z) = (w'+y')(x+z)(w+y+z)(x'+y'+z')$$

$$= [w'(x'+z')+y'] [x(w+y)+z]$$

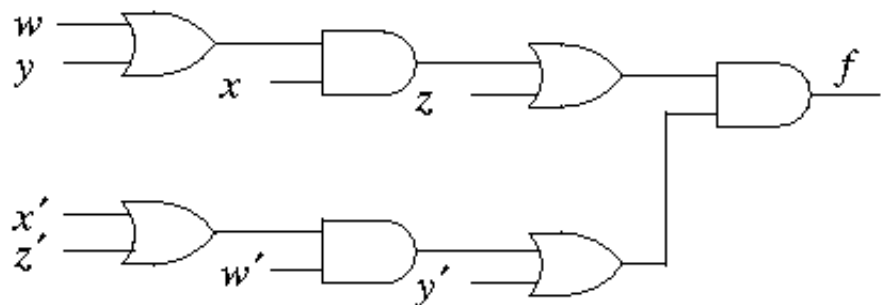

Insert inverter bubbles and convert to NOR gates:

