

**E&CE 223**  
**Assignment 7 - Solutions**

1. A sequential circuit has two inputs  $x_1$  and  $x_2$  and one output  $z$ . Whenever an  $x_1=1$  is observed, the output becomes 1 provided  $x_2=1$  has been observed exactly twice since the last time  $x_1=1$  was observed. The output remains 1 until  $x_2=1$  is observed. Draw the state diagram as (a) a Mealy machine, and (b) as a Moore machine.

(b) Moore machine - five states are required:

$q_0$  - have seen  $x_1=1$ , waiting for  $x_2=1$ ;  $z=0$


$q_1$  - have seen  $x_2=1$  once since last time  $x_1=1$ ;  $z=0$

$q_2$  - have seen  $x_2=1$  twice since last time  $x_1=1$ ;  $z=0$

$q_3$  - remain in this state until  $x_2=1$ ;  $z=1$


$q_4$  - wait for  $x_1=1$ ;  $z=0$

inputs:  $x_2x_1$

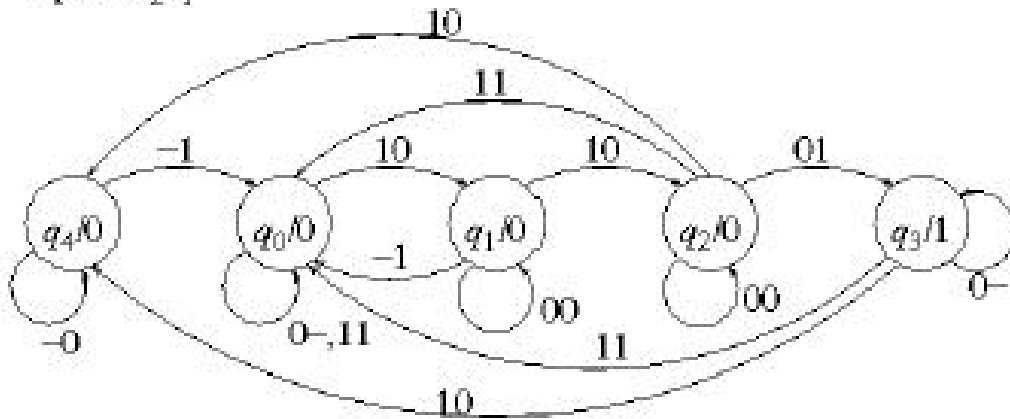

- (a) Mealy machine - same five states. However the output is associated with the transitions between states at the clock pulse. Output  $z$  is zero except for transitions to state  $q_3$ .

inputs/outputs:  $x_2x_1/z$

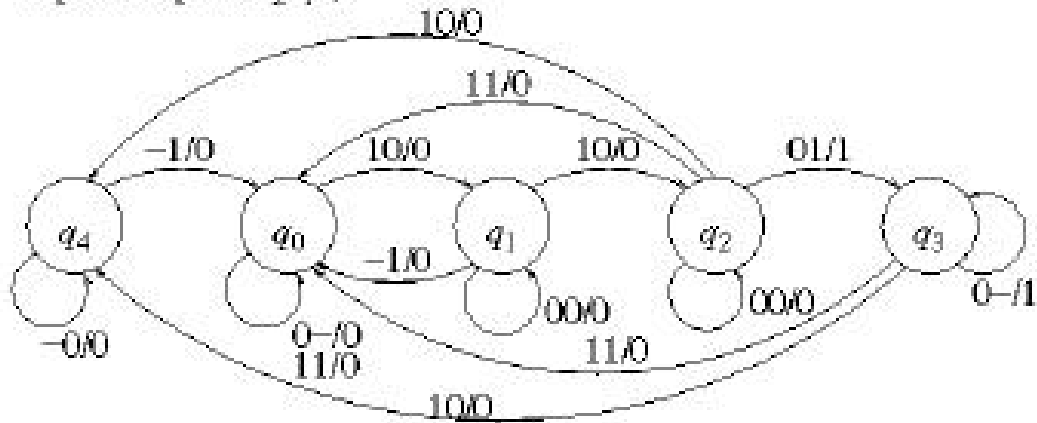


2. Mano 7.4

ROM table

inputs				outputs			
1	2	3	4	1	2	3	4
A	B	C	x	A	B	C	y
0	0	0	0	0	0	1	0
0	0	0	1	0	1	0	0
0	0	1	0	0	0	1	0
0	0	1	1	0	1	0	0
0	1	0	0	0	1	1	0
0	1	0	1	1	0	0	0
0	1	1	0	0	0	1	0
0	1	1	1	1	0	0	0
1	0	0	0	1	0	1	0
1	0	0	1	1	0	0	1
1	0	1	0	0	0	1	0
1	0	1	1	1	0	0	1
1	1	0	0	1	1	1	0
1	1	0	1	1	0	0	1
1	1	1	0	0	0	1	0
1	1	1	1	1	0	0	1

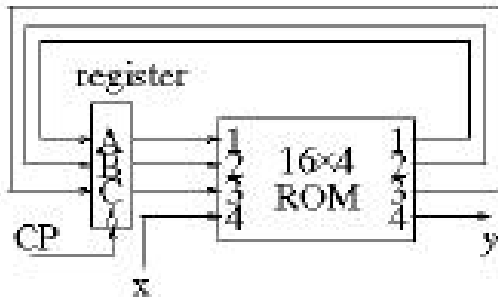The state diagram in Mano, page 247 was developed from the state table given in Mano, page 243. Hence the ROM program for states 001-101 follows directly from that table. The state 000, 110, and 111 are error states, and as discussed in Mano, page 246, are self-correcting.





	$A_2A_4$	$A_2A_4$	$A_2A_4$	$A_2A_4$
$A_8A_4$	00	01	11	10
00	$\phi$	$\phi$	$\phi$	$\phi$
01	$\phi$	$\phi$	$\alpha$	$\phi$
11	X	X	X	X
10	I	$\beta$	X	X

$A_8$  transitions

$$J_8 = A_4A_2A_1$$

$$K_8 = A_1$$

	$A_2A_4$	$A_2A_4$	$A_2A_4$	$A_2A_4$
$A_8A_4$	00	01	11	10
00	$\phi$	$\phi$	$\alpha$	$\phi$
01	I	I	$\beta$	I
11	X	X	X	X
10	$\phi$	$\phi$	X	X

$A_4$  transitions

$$J_4 = K_4 = A_2A_1$$

	$A_2A_4$	$A_2A_4$	$A_2A_4$	$A_2A_4$
$A_8A_4$	00	01	11	10
00	$\phi$	$\alpha$	$\beta$	I
01	$\phi$	$\alpha$	$\beta$	I
11	X	X	X	X
10	$\phi$	$\phi$	X	X

$A_2$  transitions

$$J_2 = K_2 = A_8A_1$$

$$\text{or } K_2 = A_1$$

	$A_2A_4$	$A_2A_4$	$A_2A_4$	$A_2A_4$
$A_8A_4$	00	01	11	10
00	$\alpha$	$\beta$	$\beta$	$\alpha$
01	$\alpha$	$\beta$	$\beta$	$\alpha$
11	X	X	X	X
10	$\alpha$	$\beta$	X	X

$A_1$  transitions

$$J_1 = K_1 = 1$$

All the error states 1010-1111 are self-correcting.

## 6. Mano 7.27

The key is to connect the 'carry out' of one counter to the 'count' input of the next. This makes the second counter increment each time the first counter hits 16. To stop at 64, the 'A<sub>7</sub>' output needs to be fed back to the first counter to stop the counting process. Also, both counters should be cleared at the start so that the counting begins at 0.

