

ECE 223 Digital Circuits and Systems

Combinational Logic




M. Sachdev,
Dept. of Electrical & Computer Engineering
University of Waterloo

1

Combinational Circuits

 - consists of logic gates with outputs that are determined entirely by the present value of the inputs (no memory)
 - Combinatorial circuits might be 2-level logic (SOP,POS) or multi-level



- Two important procedure
 - **Analysis** – Given circuit schematic, explain its behavior
 - **Design** – Given the specifications, build it

2

Analysis Procedure

1. Label all logic gate outputs and primary inputs
2. Starting from primary inputs, represent outputs in terms of their input variables
3. Repeat 2, till you reach output
4. Represent primary output(s) in terms of primary inputs

$$F_2 = AB + AC + BC$$

$$T_1 = A + B + C$$

$$T_2 = ABC$$

$$T_3 = F_2' T_1$$

$$F_1 = T_2 + T_3$$

Simplify the F_1

 


Fig. 4.2 Logic Diagram for Analysis Example

3

Design Procedure

1. From Specifications, determine the required number of inputs and outputs
2. Assign a variable to each input and output
3. Derive a truth Table that defines the required relationship between inputs and outputs
4. Perform logic minimization
5. Draw the logic diagram

4





Design Procedure - Example

- Given input bits in BCD, design a circuit to convert inputs to Excess-3 code outputs

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

5

Example – K maps

    

$$z = D'$$

$$y = CD + C'D'$$

$$= CD + (C + D)'$$

$$x = B'C + B'D + BC'D'$$

$$= B'(C + D) + B(C + D)'$$

$$w = A + BC + BD$$

$$= A + B(C + D)$$

Fig. 4-3 Maps for BCD to Excess-3 Code Converter

6

Example – Schematic

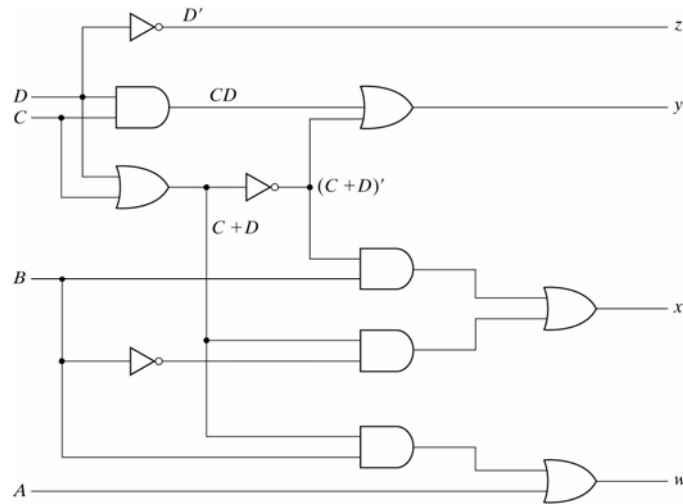


Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter

7

Binary Adder

- Adder is an important component in many logic circuits


- Half Adder

$(CS)_2 = x \text{ plus } y$

$$S = x'y + xy' = x \oplus y$$

$$C = xy$$

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

8

Full Adder

$(CS)_2 = x \text{ plus } y \text{ plus } z$

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

9



Full Adder – K Maps & Schematics

x \ yz	00	01	11	10
0	0	1	0	1
1	1	0	1	0

S

x \ yz	00	01	11	10
0	0	0	1	0
1	1	1	1	1

C

  


$$S = x'y'z + x'y'z' + xy'z' + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

10

Implementation with 2 Half Adders

 

11


Half Subtractor

- Produces $x - y$
 - D – difference
 - B – Borrow

x	y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

$$D = x'y + xy' = S \text{ of half adder}$$

$$B = x'y$$

 

12

Full Subtractor

$(x - y) - z$; where z represents a borrow

x	y	z	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$D = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z = S$ of full adder

$B = x'y + x'z + yz$ (same as C of full adder except x is inverted)


13

Parallel Adder

- Often, we must add $2n$ bit numbers and carry
- Classical approach
 - $(2n + 1)$ inputs and $(n+1)$ outputs
 - Design a $(n+1)$ output, 2-level (e.g. SOP) design
- Problems
 - Too many gates
 - Fan-in is too large
 - Not practical for $n > 3$
- Use iterative circuit, reduced complexity

14

Parallel Adder – 4 Bit Adder

 


- For $n = 4$
 - Inputs 9
 - Outputs 5
 - Power, Gnd 2
- A 4 bit adder is accommodated in 16 pin package (MSI)

15

Parallel Adder - Issues

 - Fewer gates than 2-level implementation, however significantly slower → Rippling effect of carry
- For an n bit adder
 - Propagation delay = $(2 \times \text{Average gate delay}) \times (\text{number of bits})$
 - = $2nxd$, where d = Average gate delay



16

Carry Lookahead Logic

- Define:

- Carry Propagate

$$P_i = a_i \oplus b_i \text{ for } i = 0, \dots, n-1$$

- Carry Generate

$$G_i = a_i b_i$$

- Now

$$s_i = a_i \oplus b_i \oplus c_i$$

$$= P_i \oplus c_i$$

$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i$$

$$= a_i b_i + a_i b_i' c_i + a_i' b_i c_i$$

$$= G_i + c_i P_i$$

17

Carry Lookahead Logic

- Observation

- All carries can be generated simultaneously

$$c_2 = G_1 + P_1 c_1$$

$$c_3 = G_2 + P_2 c_2 = G_2 + P_2 G_1 + P_2 P_1 c_1$$

$$c_4 = G_3 + P_3 c_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 c_1$$

- Delay

- P, G → 2 gate delay
- c → 2 gate delay (2-level circuit)
- S → XOR (2-level circuit)

- 6 gate delays; independent of n

- Practically, n is limited by # of connections and gate loading

18

BCD Adder

Binary Sum					BCD Sum					#
k	Z8	Z3	Z2	Z1	C	S8	S4	S2	S1	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	1	0	0	1	1
0	0	0	1	0	0	1	0	1	0	2
0	0	0	1	1	0	1	0	1	1	3
0	0	1	0	0	0	1	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15

Binary Sum					BCD Sum					#
k	Z8	Z3	Z2	Z1	C	S8	S4	S2	S1	
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19


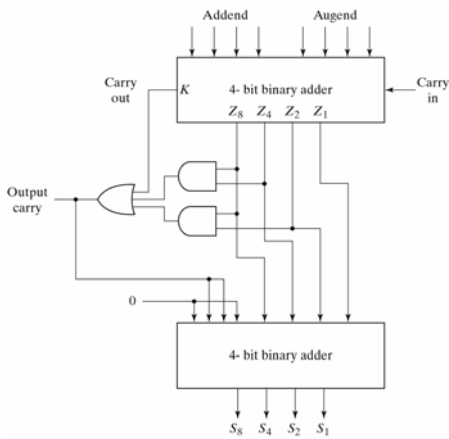


Fig. 4-14 Block Diagram of a BCD Adder

Magnitude Comparator

 

- Classical approach
 - 3 outputs and 2n inputs
 - Large logic complexity, if $n > 3$
- Alternative Approach
- 2-step process

23

Magnitude Comparator

- 2-step process
 1. Define

$$x_i \equiv (A_i \odot B_i) = A_i B_i + A_i' B_i', \quad 0 < i < 3$$

$$2. \quad F_1 = (A = B) = x_3 x_2 x_1 x_0$$

$$\begin{aligned} F_2 = (A > B) &= (A_3 > B_3) \\ &+ (A_3 = B_3) \cdot (A_2 > B_2) \\ &+ (A_3 = B_3) \cdot (A_2 = B_2) \cdot (A_1 > B_1) \\ &+ (A_3 = B_3) \cdot (A_2 = B_2) \cdot (A_1 = B_1) \cdot (A_0 > B_0) \\ &= A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0' \end{aligned}$$

$$\begin{aligned} F_3 &= A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0 \\ &= (F_1 + F_2)' \end{aligned}$$

24

Magnitude Comparator

 



Fig. 4-17 4-Bit Magnitude Comparator

25

Decoders

- Code of n bits can represent 2^n decode outputs
 - One output is true at a time

x	y	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 


26

Decoders with Enable

- If $E = 0 \rightarrow$ all outputs are disabled
 - Outputs are active low

E	x	y	Y_0	Y_1	Y_2	Y_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	0	1	0	1	1
0	0	1	1	1	0	1
0	0	1	1	1	1	0

 

27

Larger Decoders

- Larger decoders are built with smaller ones

 


Fig. 4-20 4 × 16 Decoder Constructed with Two 3 × 8 Decoders

- Special decoders (other than n to 2^n)
 - BCD to 7 segment display

28

Function implementation using Decoders

- Adder $S = \Sigma(1,2,4,7)$; $C = \Sigma(3,5,6,7)$

 


Fig. 4-21 Implementation of a Full Adder with a Decoder

29

Encoders

- Does reverse operation to decoder
- Constraint – only one input is active at a time
- Example, Octal to Binary Encoder
 $Z = D1 + D3 + D5 + D7$; $y = D2 + D3 + D6 + D7$; $x = D4 + D5 + D6 + D7$

Inputs								Outputs		
D0	D1	D2	D3	D4	D5	D6	D7	x	y	z
1	0	0	0	0	0	1	0	0	0	0
0	1	0	0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0	0	1	0
0	0	0	1	0	0	1	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	1	0	0	0	0	0	1	1	1	1

Priority Encoders

- Encoder with priority function
 - Multiple inputs may be true simultaneously
 - Higher priority input gets the precedence

Inputs				Outputs		
D ₀	D ₁	D ₂	D ₃	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	0	1	1	1

- Valid bit, V, indicates two inputs are true at the same time
 - Higher priority input gets the precedence

31

Priority Encoders - Circuit

 



Fig. 4-22 Maps for a Priority Encoder

$$\begin{aligned}
 x &= D_2 + D_3 \\
 y &= D_3 + D_1 D_2' \\
 V &= D_0 + D_1 + D_2 + D_3
 \end{aligned}$$

32

Multiplexers

 - A Multiplexer has n inputs, one output, and S ($2^S = n$) select (control) inputs



s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

Passes (selects) an input depending on S

Fig. 4-25 4-to-1-Line Multiplexer


33

Function Implementation with Multiplexers

- Let $F(x,y,z) = \Sigma(1,2,6,7)$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(a) Truth table

 

(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

34

Multiplexers with Tri-stated Gates

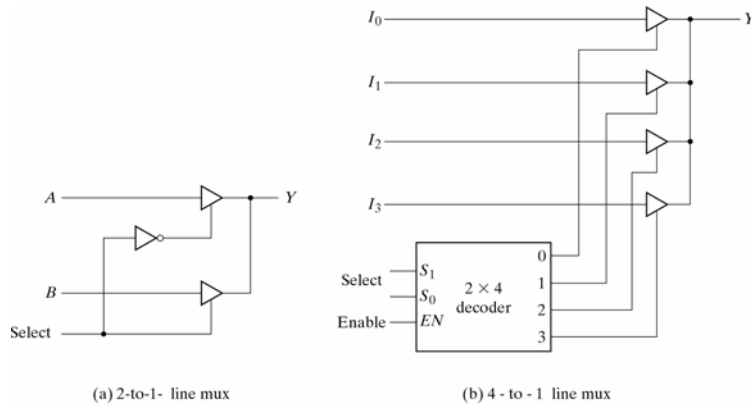


Fig. 4-30 Multiplexers with Three-State Gates

35

Book Sections – Combination Circuits

- Material is covered in Sections 4.1 – 4.5, 4.7 – 4.10

36