

ECE 223

Digital Circuits and Systems

Logic Minimization



M. Sachdev,
Dept. of Electrical & Computer Engineering
University of Waterloo

1

Karnaugh Maps - Introduction

- 2-Level Logic implementation using SOP or POS is not the most economical in terms of #gates & #inputs
- A Karnaugh map is a graphical representation of a truth table
 - The map contains one cell for each possible minterm
 - Adjacent cells differ in only one literal; i.e. x (or x')
 - Function is plotted by placing 1 in cells corresponding to minterms
 - Put 0 in rest of the cells

2

K Map with 2 Variables

- $F = f(x,y)$

x	y	F
0	0	m0
0	1	m1
1	0	m2
1	1	m3

		y	
		0	1
x	0	m0	m1
	1	m2	m3

- Example, $F1 = x'y$

		y	
		0	1
x	0		
	1		

3

K Map with 3 Variables

- 3 Variable, $F = f(x,y,z)$;
- Given $F2 = \sum(2,3,4,5)$
 - Represent it on the K map
 - minimize the function

		yz			
		00	01	11	10
x	0				
	1				

		yz			
		00	01	11	10
x	0	m0	m1	m3	m2
	1	m4	m5	m7	m6

		yz			
		00	01	11	10
x	0	$x'y'z'$	$'x'y'z$	$x'yz$	$x'yz'$
	1	$xy'z'$	$xy'z$	xyz	xyz'

4

K Map with 3 Variables

- 3 Variable, $F = f(x,y,z)$;
 - Given $F3 = \sum(3,4,6,7)$
 - Minimize the function using K map
- Function minimization
- Find maximum size groups that *cover all 1s* in the map
(Comment – a group should not be a subset of other group)
 - 4 cell group \rightarrow 2 literals can be removed
 - 2 cell group \rightarrow 1 literal can be removed
- Guidelines for logic synthesis (SOP)
 - Fewer groups \rightarrow fewer AND gates, and fewer inputs to the OR gate
 - Fewer literals (larger group) \rightarrow fewer inputs to an AND gate
 - *Synthesis Objective: Fewest # of gates and # of inputs*

		yz			
		00	01	11	10
x	0				
	1				

5

K Map with 4 Variables

- 4 Variable, $F = f(w,x,y,z)$
- Given, $F4 = \sum(3,4,5,7,9,13,14,15)$
 - represent it on the map
 - Minimize the logic
- Clues
 - Make all possible groups
 - Do we need “the group of 4”?

$$F4 = w'xy' + wxy + w'yz + wy'z$$

		yz			
		00	01	11	10
wx	00	m0	m1	m3	m2
	01	m4	m5	m7	m6
	11	m12	m13	m15	m14
	10	m8	m9	m11	m10

		yz			
		00	01	11	10
wx	00	0	0	1	0
	01	0	1	1	0
	11	1	1	1	1
	10	0	1	0	0

6

Implicants & Prime Implicants, ...

- **Implicant:** A group of one or more k map cell
- **Prime implicant:** an implicant that is not a subset of another implicant
- **Essential Prime Implicant:** a prime implicant that covers at least one cell not covered by another prime implicant
- Example, $F5(w,x,y,z) = \sum(0,1,2,5,6,7,9,13,14)$

wx \ yz	00	01	11	10
00	1	1	0	1
01	0	1	1	1
11	0	1	0	1
10	0	1	0	0

wx \ yz	00	01	11	10
00	1	1	0	1
01	0	1	1	1
11	0	1	0	1
10	0	1	0	0

7

Product of Sum Expression

- Let F be the function $\rightarrow F' = \sum(\text{all minterms not in } F)$
- $F = \pi(\text{all minterms not in } F)'$ (de Morgan's theorem)
- Therefore, one can obtain POS expression by
 1. Group all 0s on K map
 2. Use de Morgan's theorem to obtain POS expression
- $F6 = x'z' + x'y' + w'y'z$ (SOP) = $(w' + x')(y' + z')(x' + z)$ (POS)
- *One is often simpler than the other \rightarrow Check both*

wx \ yz	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	1	1	0	1

wx \ yz	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	1	1	0	1

Plotting Product of Sum Expression

- Given, $F7 = (w + x)(x + y' + z)(y + z)$

$$\begin{aligned} F7' &= [(w + x)(x + y' + z)(y + z)]' \\ &= (w + x)' + (x + y' + z)' + (y + z)' \\ &= w'x' + x'y'z' + y'z' \end{aligned}$$

- $F7'$ is plotted by putting 0s in appropriate cells

- Can $F7'$ be simplified further?

$$\begin{aligned} F7' &= w'x' + x'z' + y'z' \\ F7 &= (w + x)(x + z)(y + z) \end{aligned}$$

wx \ yz	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	0	1	1	1
10	0	1	1	0

9

Don't care Conditions

- Some time, not all values of a function are defined
 - Some inputs conditions will never occur
 - We don't care what the output is for that input condition
- In these cases, we can choose the output to be wither 0 or 1, whichever simplifies the circuit
- Example – A circuit to produce output 1 if a BCD digit is multiple of 3
 - BCD – Four inputs (wxyz) 0 (0000) \rightarrow 9 (1001)
 - Values of wxyz 10 (1010) \rightarrow 15 (1111) don't care
- The function $F8 = \sum(3,6,9) + d(10,11,12,13,14,15)$

10

Don't Care - Plotting

- Don't care are plotted as X in the K map
- SOP expression → Treat X as 1 if it allows a larger group
- POS expression → Treat x as 0 if it allows a larger group
- $F8_1 = wz + xyz' + x'yz$ (SOP)
- $F8'_2 = xz + w'y' + x'z'$ { $F' = \sum(\text{all minterms not in } F)$ }
- $F8_2 = (x' + z')(w + y)(x + z)$ de Morgan's theorem

Is $F8_1 = F8_2$??

wx \ yz	00	01	11	10
00	0	0	1	0
01	0	0	0	1
11	X	X	X	X
10	0	1	X	X

wx \ yz	00	01	11	10
00	0	0	1	0
01	0	0	0	1
11	X	X	X	X
10	0	1	X	X ₁₁

Simplest 2-Level Expression

- Example, $F(w,x,y,z) = \sum(0,1,2,5,6,7,9,14) + d(13)$
 - Determine essential and prime implicants

wx \ yz	00	01	11	10
00	1	1	0	1
01	0	1	1	1
11	0	X	0	1
10	0	1	0	0

Essential prime implicants

wx \ yz	00	01	11	10
00	1	1	0	1
01	0	1	1	1
11	0	X	0	1
10	0	1	0	0

Prime implicants

Simplest 2-Level Expression

- Example, $F(w,x,y,z) = \sum(0,1,2,5,6,7,9,14) +d(13)$
 - Determine essential and prime implicants

	0	1	2	5	6	7	9	14	
$y'z$ (1,5,9,13)		√		√			√		⊗
xyz' (6,14)					√			√	⊗
$w'x'y'$ (0,1)	√	√							A
$w'x'z'$ (0,2)	√		√						B
$w'xz$ (5,7)				√		√			C
$w'xy$ (6,7)					√	√			D
$w'yz'$ (2,6)			√		√				E

- All minterms must be covered
 - i.e., essential prime implicants must be included
 - Different choices for prime implicants
 $B + C$; or $B + D$; or $A + C + E$; or $A + D + E$

13

Tabulation (Quine-McCluskey) Method

- The map method of simplification is convenient if # of variables ≤ 4
 - Tabulation method is preferred for function with large # of variables
- For $F(w,x,y,z)$ consider adjacent minterms

let $a = m_4 + m_5 = w'xy'z' + w'xy'z = w'xy'$
 or $= 0100 + 0101 = 010-$
 Similarly, $b = m_{12} + m_{13} = wxy'z' + wxy'z = wxy' = 110-$
- Let $c = a + b = m_4 + m_5 + m_{12} + m_{13}$
 $w'xy' + wxy' = xy' = -10-$
- Adjacent terms differ by a single bit in their representation
- Tabulation method consists of grouping of minterms and systematically checking for single bit differences

14

Tabulation (Quine-McCluskey) Method

- Example, $F(w,x,y,z) = \sum(0,3,4,6,7,8,10,11,15) + d(5,9)$
 - Place minterms in different Sections according to # of 1's in their binary representation
 - Each member of each Section is compared with each member of Sections below; all reduction are recorded in next column
 - Mark terms that combine
 - All unmarked terms are prime implicants

15

Tabulation Method - Example

- Example

16

NAND & NOR Implementation

- In digital logic families NAND & NOR implementations are cheaper compared to AND & OR implementations
 - Hence, NAND & NOR are preferred
- NAND and NOR are universal gates
 - Can mimic any logic gate
 - Example, NAND gate can implement:
 - NOT \rightarrow short inputs
 - AND $\rightarrow \{(xy)'\}'$
 - OR $\rightarrow (x'y)' = x + y$
- Similarly for NOR gate, one can show its universality

17

NAND – 2-level Implementation

- Can implement any arbitrary logic
Example, $F = AB + CD$

 


Fig. 3-20 Three Ways to Implement $F = AB + CD$

18

NAND – 2-level Implementation

- Given, $F_9(x,y,z) = \sum(1,2,3,4,5,7)$
Minimize the function, and implement it with NAND gates

 
 


Fig. 3-21 Solution to Example 3-10

19

NAND – 2-level Implementation Procedure

- Simplify the function and express it in SOP form
 - Draw a NAND gate for each product term
 - Draw a single gate using AND-invert or invert-OR symbol for the sum term
 - A term with single literal, complement if needed
- Multi-level NAND Circuits**
 - Convert all AND gates to NAND gates
 - Convert all OR gates to NAND gates with invert-OR symbols
 - Balance all bubbles, insert an inverter if needed

20

NOR – Implementation

- NOR gate is a dual of NAND
 - Same rules and procedures
- Example, $F = (A + B)(C + D)E$

 


Fig. 3-26 Implementing $F = (A + B)(C + D)E$


21

Wired Logic


- Two logic gate outputs are not shorted together
 - May create logical conflicts → Logic is not defined
- In some technologies, it is possible to short O/Ps of some logic gates (*wired logic*)

$$F1 = (AB)'(CD)' = (AB + CD)' \quad (\text{wired AND})$$
 
$$F2 = (A + B)' + (C + D)' = [(A + B)(C + D)]' \quad (\text{wired OR})$$



 (a) Wired-AND in open-collector
TTL NAND gates.
(AND-OR-INVERT)



(b) Wired-OR in ECL gates
(OR-AND-INVERT)

Fig. 3-28 Wired Logic

22

Exclusive-OR Function

- XOR gate is expensive to implement in silicon
 - XOR = $xy' + x'y$
 - XNOR = $(xy' + x'y)' = xy + x'y'$
- But they are useful in
 - Parity checking
 - Arithmetic circuits (adders, subtractors)

x	y	XOR	XNOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

23

Exclusive-OR Function

- XOR gate properties
 - Commutative
 - Associative
- Odd and Even Functions

		BC		B	
		00	01	11	10
A	0		1		1
	1	1		1	

(a) Odd function
 $F = A \oplus B \oplus C$

		BC		B	
		00	01	11	10
A	0	1		1	
	1		1		1

(a) Even function
 $F = (A \oplus B \oplus C)'$

Fig. 3-33 Map for a Three-variable Exclusive-OR Function

24

Exclusive-OR Function

- 4 Variable XOR

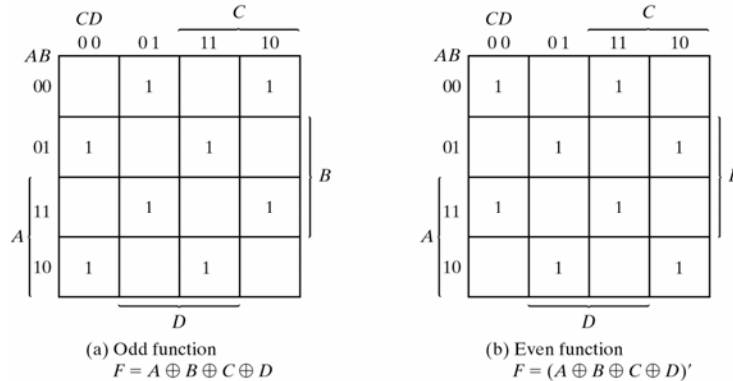


Fig. 3-35 Map for a Four-variable Exclusive-OR Function

25

Parity Generation and Checking

- Parity checking is useful for detecting and correcting errors when transmitting binary data
 - We can always append a parity bit to the end of the data bits (e.g. 32) so that the number of 1s in the packet is always even or odd
- If we lose a bit in transmission, we can use the parity bit to tell us there has been a problem

 



Fig. 3-36 Logic Diagram of a Parity Generator and Checker

26



Book Sections – Logic Minimization

- Material is covered in Sections 3.1 – 3.8