

# ECE 223 Digital Circuits and Systems

## Registers & Counters



M. Sachdev

Dept. of Electrical & Computer Engineering  
University of Waterloo

1

## Registers

- Register is a group of flip-flops
  - $n$ -bit register has  $n$  flip-flops
  - Can hold  $n$  bits of binary data
  - Register may also contain combinational logic

 


Fig. 6-1 4-Bit Register

2

## Register with Parallel Load

- Specific control signal to load n-bit data
  - Load = 0, register retains the data
  - Load = 1, register accepts new data

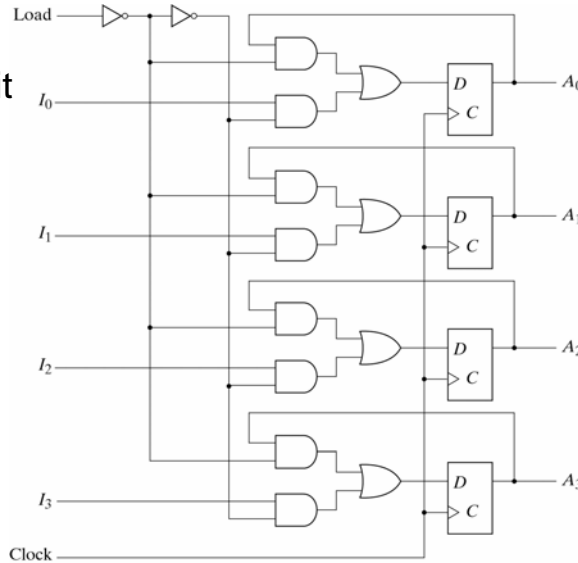


Fig. 6-2 4-Bit Register with Parallel Load

## Shift Register

- Capable of shifting data in one or both directions
  - Clock controls the shift operation
- Figure shows a simple shift register with left to right data shifting capability

 


Fig. 6-3 4-Bit Shift Register

## Serial Data Transfer

- Serial mode → Data is transferred one bit at a time

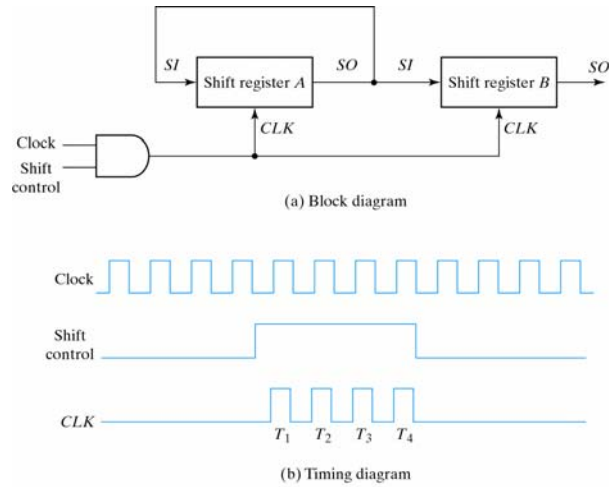


Fig. 6-4 Serial Transfer from Register A to register B

5

## Serial Addition

- Parallel adders
  - Faster,
  - cost more logic
- Serial adders
  - Slower
  - n-bit addition → n clock cycles
  - Less hardware

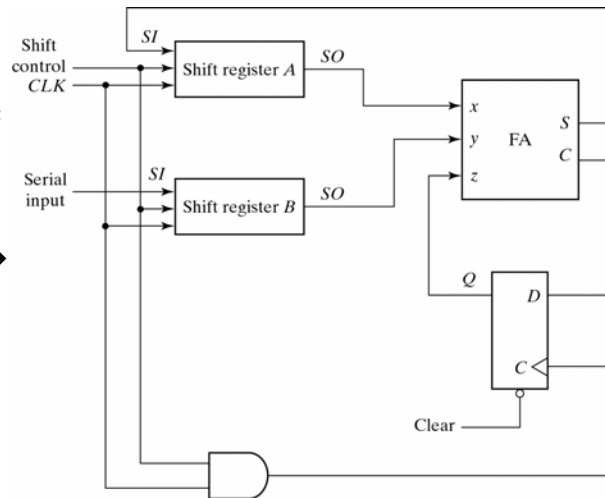


Fig. 6-5 Serial Adder

6

# Universal Shift Register

Mode Control		Operation
S1	S0	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Para load

 


Fig. 6-7 4-Bit Universal Shift Register

# Ripple (Asynchronous) Counter

- Counts the binary sequence
  - Negative edge triggered
  - Output of one flip-flop → Clock to the next
  - Clock skew adds up

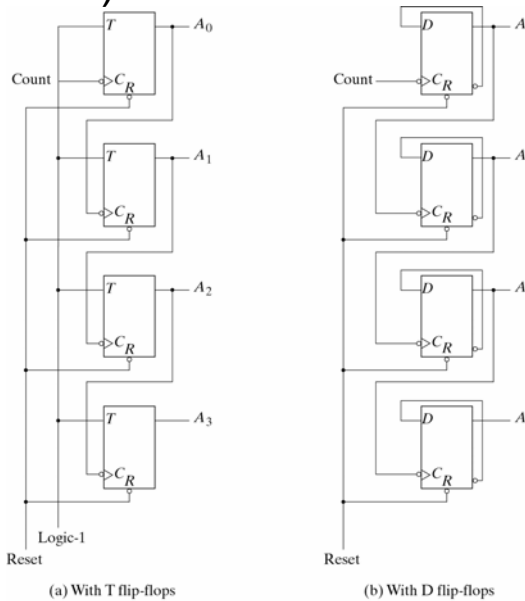


Fig. 6-8 4-Bit Binary Ripple Counter

## BCD Ripple Counter

- Counter must reset itself after counting the terminal count

 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

 


Fig. 6-10 BCD Ripple Counter

9

## Synchronous Counters

- A common clock is applied to all flip-flops
  - Clock skew does not add up
  - Faster than ripple counters
- Synchronous counters can be designed using **sequential circuit procedure**
- Synchronous binary counter

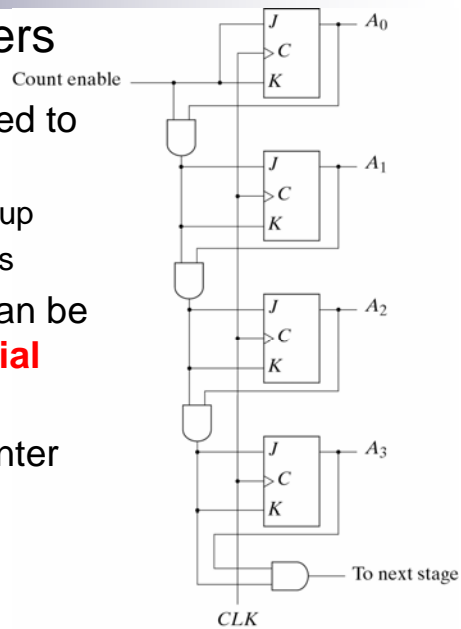


Fig. 6-12 4-Bit Synchronous Binary Counter

## Up-Down Binary Counter

- Can count up (0000 → 1111) or down (1111 → 0000) binary sequence

 


Fig. 6-13 4-Bit Up-Down Binary Counter

11

## Synchronous BCD Counter

- Design a synchronous BCD counter with T flip-flops

Present State				Next State				Out	Flip-flop inputs			
Q8	Q4	Q2	Q1	Q8	Q4	Q2	Q1	y	TQ8	TQ4	TQ2	TQ1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

12

## Binary Counter with Parallel Load

 


Fig. 6-14 4-Bit Binary Counter with Parallel Load

13

## BCD Counter & Modulo-N Counter

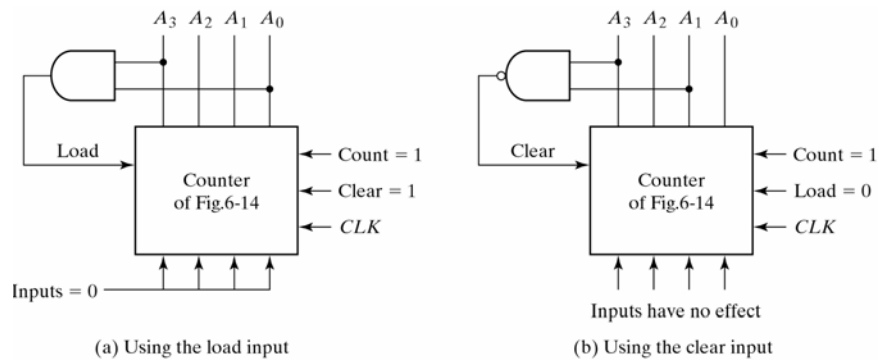


Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load

- **Home work** - Suppose we want to design a counter with 1,2,3,4,5,6,7,8,9 sequence (mod-9 counter)?

14

## Counter with Unused States

- A circuit with  $n$  flip-flops has  $2^n$  states
  - We may have to design a counter with a given sequence (unused states)
  - Unused states may be treated as don't care or assigned specific next state
  - Outside noise may cause the counter to enter unused state
    - Must ensure counter eventually goes to the valid state

Present State			Next State			Flip-flop Inputs					
A	B	C	A	B	C	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

15

## Counter with Unused States



 


Fig. 6-16 Counter with Unused States

16

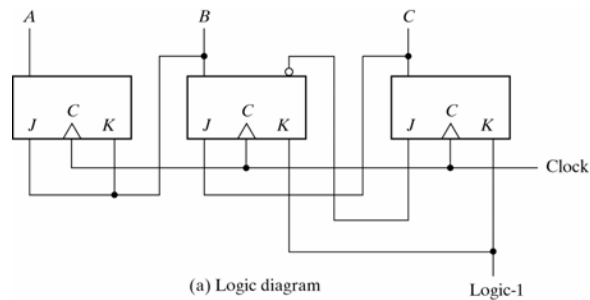

# Ring Counter

 

Capable of generating different timing signals


 


Fig. 6-17 Generation of Timing Signals
 
# Johnson Counter

- Number of states of a ring counter can be doubled



Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	$AB'$
3	1	1	0	0	$BC'$
4	1	1	1	0	$CE'$
5	1	1	1	1	$AE$
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding

Fig. 6-18 Construction of a Johnson Counter



## Book Sections – Registers & Counters

- Material is covered in Sections 6.1 – 6.5