

ECE 223 Digital Circuits and Systems

Synchronous Logic




M. Sachdev

Dept. of Electrical & Computer Engineering
University of Waterloo

1

Sequential Circuits

 
- Combinational circuits
 - Output = f (present inputs)
- Sequential circuits
 - Output = f (present inputs and past inputs)
 - Circuit remembers past history
 - Must contain memory



2

Synchronous Sequential Circuits

 - A synchronizing, periodic signal, Clock, facilitates the transition from present state to next state
 - Memory is provided by flip-flops



(a) Block diagram




(b) Timing diagram of clock pulses

Fig. 5-2 Synchronous Clocked Sequential Circuit

3

SR (Set Reset) Latches

 - NOR Latch
- SR = 11 is avoided
 - Outputs are not complementary
 - Input transition from 11 → 00 may cause circuit to: (i) fall into either state, or become meta-stable



(a) Logic diagram


(b) Function table

Fig. 5-3 SR Latch with NOR Gates

4

SR (Set Reset) Latches

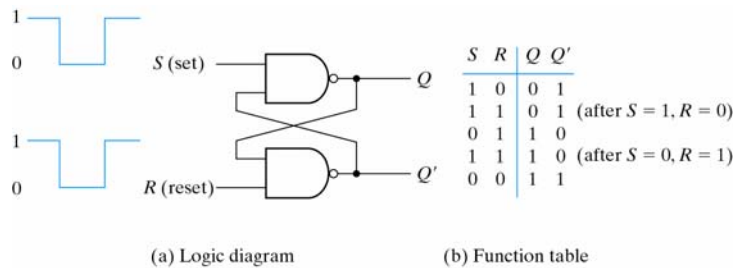- NAND Latch
- $SR = 00$ is avoided
 - Outputs are not complementary
 - Input transition from $00 \rightarrow 11$ may cause circuit to: (i) fall into either state, or become meta-stable



(a) Logic diagram


(b) Function table

Fig. 5-4 SR Latch with NAND Gates

5

SR Latch with control Input

 - $C = 0$
 - Latch retains its state
- $C = 1$
- Allows propagation of SR inputs



(a) Logic diagram


(b) Function table

Fig. 5-5 SR Latch with Control Input

6

Data (D) Latch

 - Data latch eliminate, the need for complementary inputs
 - Outputs are also complementary



(a) Logic diagram

(b) Function table

Fig. 5-6 D Latch

7

Flip-flop

- Latch is level sensitive to the control signal
 - Multiple data transition may cause problem while $C = 1$
- Flip-flop is edge triggered
 - Flip-flop samples the data on Clock transition

 


Fig. 5-9 Master-Slave D Flip-Flop

8

Edge Triggered Flip-flop

- Efficient implementation
 - Multiple data transitions do not affect the output


 


Fig. 5-10 *D*-Type Positive-Edge-Triggered Flip-Flop

9

J-K Flip-flop

 - Versatile flip-flop
 - Can be Set, Reset, or Complement (toggle) its output



(a) Circuit diagram

(b) Graphic symbol

Fig. 5-12 *JK* Flip-Flop

10

J-K Flip-flop

$$Q_{n+1} = JQ_n' + K'Q_n = D$$



| | | | | | |
|-----------|------|-------|----|----|----|
| Q_{n+1} | JK | 00 | 01 | 11 | 10 |
| | | Q_n | | | |
| 0 | | | | 1 | 1 |
| 1 | | 1 | | | 1 |

| J | K | Q_n | Q_{n+1} |
|-----|-----|-------|-----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

11

Asynchronous Inputs

  - Ability to Reset (or Set) irrespective of Clock state
- Often needed in computation



| R | C | D | Q | Q' |
|-----|-----|-----|-----|------|
| 0 | X | X | 0 | 1 |
| 1 | ↑ | 0 | 0 | 1 |
| 1 | ↑ | 1 | 1 | 0 |

(b) Function table

Fig. 5-14 D Flip-Flop with Asynchronous Reset

Analysis of Clocked Sequential Circuits

■ Procedure

- Determine **state equations** (transition equations)
- Determine the **state table** (transition table)
- Determine **state diagram**

■ Example – Analysis with D flip-flop

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = A'(t)x(t)$$

Or

$$A(t+1) = Ax + Bx$$

$$B(t+1) = A'x$$

$$\text{Similarly, } y = (A+B)x'$$

 


Fig. 5-15 Example of Sequential Circuit

13

State Table

| Present State | | Input | Next State | | Output |
|---------------|---|-------|------------|---|--------|
| A | B | x | A | B | y |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 |

14

State Table, State Diagram

| Present State | Next State | | Output | |
|---------------|------------|-------|--------|-------|
| | x = 0 | x = 1 | x = 0 | x = 1 |
| AB | AB | AB | y | y |
| 00 | 00 | 01 | 0 | 0 |
| 01 | 00 | 11 | 1 | 0 |
| 10 | 00 | 10 | 1 | 0 |
| 11 | 00 | 10 | 1 | 0 |

 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

Analysis with JK Flip-flop

 


Fig. 5-18 Sequential Circuit with JK Flip-Flop

$$\begin{aligned}
 J_A &= B, & K_A &= Bx' \\
 J_B &= x', & K_B &= A'x + Ax' = A \oplus x
 \end{aligned}$$

State Table

| Present State | | Input | Next State | | Flip-flop Inputs | | | |
|---------------|---|-------|------------|---|------------------|----|----|----|
| A | B | x | A | B | JA | KA | JB | KB |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |

$$A(t+1) = JA' + K'A$$

$$B(t+1) = JB' + K'B$$

17

State Diagram

 


Fig. 5-19 State Diagram of the Circuit of Fig. 5-18


18

Analysis with Toggle Flip-flop

- The Characteristic Equation

$$Q(t+1) = T \oplus Q$$

$$= T'Q + TQ'$$

 

(a) Circuit diagram

(b) State diagram

Fig. 5-20 Sequential Circuit with T Flip-Flops

Analysis with Toggle Flip-flop

| Present State | | Input x | Next State | | Output y |
|---------------|---|--------------|------------|---|---------------|
| A | B | | A | B | |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 |

Mealy and Moore Models (Machine)

- Most general model of a sequential circuit has inputs, outputs, and internal states
 - Two different models – (i) Mealy model, (ii) Moore Model
- Difference is how output is generated

Mealy Model – Output is a function of present state & input

Moore Model – Output is only a function of present state


 


Fig. 5-2 Synchronous Clocked Sequential Circuit

21


Mealy Machine

 

- Observation
 - Output can change asynchronous to the clock
 - The output delay with respect to clock is **unpredictable**
 - Difficult to do the timing analysis

22

Moore Machine

 

- Observation
 - Output changes synchronously to the clock
 - The output delay with respect to clock is **predictable**
 - Easier timing analysis

23

State Reduction



- Sequential circuit analysis
 - Circuit diagram → state table (or state diagram)
- Sequential circuit design
 - State diagram (state table) → circuit diagram
- Redundant state may exist in a state diagram (or table)
 - By eliminating them → reduce the # of logic gates and flip-flops
 - “Two states are equivalent if for each member of the set of inputs, they give exactly same state or an equivalent state
 - When two states are equivalent, one of them can be removed

24

State Reduction - Example

| Present State | Next State | | Output |
|---------------|------------|-----|--------|
| | X=0 | X=1 | |
| A | D | C | 1 |
| B | A | E | 0 |
| C | D | A | 1 |
| D | B | D | 0 |
| E | C | B | 0 |

| Present State | Next State | | Output |
|---------------|------------|-----|--------|
| | X=0 | X=1 | |
| P (A,C) | D | P | 1 |
| Q (B,E) | P | Q | 0 |
| D | Q | D | 0 |

  

25

State Reduction – Home Work

- Reduced the shown state diagram
(Page 199 in the text book)

 


Fig. 5-22 State Diagram

26

State Assignment

- States must be assigned coded binary values
 - In order to realize with physical components

| Present State | Next State | | Output | |
|---------------|------------|-----|--------|-----|
| | X=0 | X=1 | X=0 | X=1 |
| a | a | b | 0 | 0 |
| b | c | d | 0 | 0 |
| c | a | d | 0 | 0 |
| d | e | d | 0 | 1 |
| e | a | d | 0 | 1 |

| State | Assignment 1 Binary | Assignment 2 Gray code | Assignment 3 One-hot |
|-------|------------------------|---------------------------|-------------------------|
| a | 000 | 000 | 00001 |
| b | 001 | 001 | 00010 |
| c | 010 | 011 | 00100 |
| d | 011 | 010 | 01000 |
| e | 100 | 110 | 10000 |

27

Sequential Circuits – Design Procedure

- Procedure
 1. Words or timing diagram
 2. Draw state transition diagram
 3. Make state table
 4. Reduced state table (if possible)
 5. Assign binary values to states
 6. Choose flip-flop type
 7. Derive simplified flip-flop input equations and output equations
 8. Draw the logic diagram

28

Synthesis using D Flip-flops

- Given the state diagram, design the circuit using D flip-flops

 


Fig. 5-24 State Diagram for Sequence Detector

| Present State | | Input x | Next State | | Output y |
|---------------|---|------------|------------|---|-------------|
| A | B | | A | B | |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 |

29

Synthesis using D Flip-flops

| | | | | | |
|---|----|----|----|----|----|
| | Bx | 00 | 01 | 11 | 10 |
| A | 0 | | | 1 | |
| | 1 | | 1 | 1 | |

$$D_A = Ax + Bx$$

| | | | | | |
|---|----|----|----|----|----|
| | Bx | 00 | 01 | 11 | 10 |
| A | 0 | | 1 | | |
| | 1 | | 1 | 1 | |

$$D_B = Ax + B'x$$

| | | | | | |
|---|----|----|----|----|----|
| | Bx | 00 | 01 | 11 | 10 |
| A | 0 | | | | |
| | 1 | | | 1 | 1 |

$$y = AB$$

30

Synthesis using JK Flip-flop

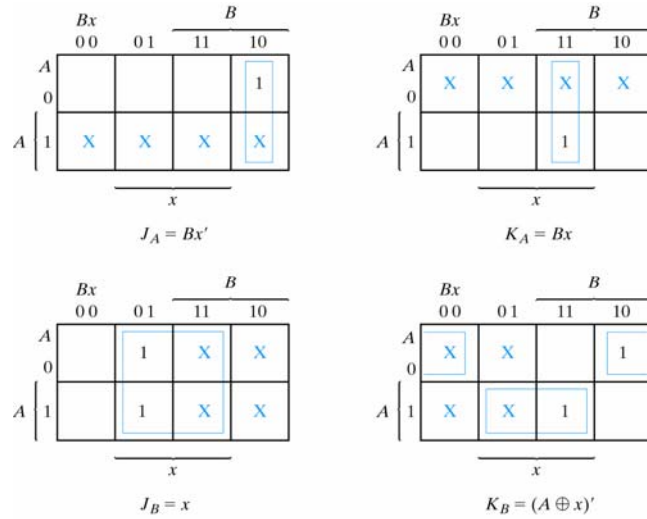


Fig. 5-27 Maps for J and K Input Equations

33

Synthesis using JK Flip-flop

 


Fig. 5-28 Logic Diagram for Sequential Circuit with JK Flip-Flops

34



Book Sections – Sequential Circuits

- Material is covered in Sections 5.1 – 5.4, 5.6 – 5.7