 




## Problem Set 6

- 6-1** Construct a  $D$  flip-flop that has the same characteristics as the one shown in Fig. 6-5, but instead of using NAND gates, use NOR and AND gates. (Remember that a one-input NOR gate is equivalent to an inverter.)
- 6-2** Construct a  $D$  flip-flop that has the same characteristics as the one shown in Fig. 6-5, but instead of using NAND gates, use NOR gates.



(a) Logic diagram

$Q$	$D$	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

  

(b) Characteristic table


(c) Characteristic equation

(d) Graphic symbol

**FIGURE 6-5**  
 $D$  flip-flop

- 6-4** Draw the logic diagram of a master-slave  $D$  flip-flop. Use NAND gates.

- 6-9** Derive the state table and the state diagram of the sequential circuit shown in Fig. P6-9. Explain the function that the circuit performs.

 


**FIGURE P6-9**

- 6-12** A sequential circuit has two *JK* flip-flops, *A* and *B*; two inputs, *x* and *y*; and one output, *z*. The flip-flop input functions and the circuit output function are as follows:

$$\begin{aligned}
 JA &= Bx + B'y' & KA &= B'xy' \\
 JB &= A'x & KB &= A + xy' \\
 z &= Axy + Bx'y'
 \end{aligned}$$

- Draw the logic diagram of the circuit.
  - Tabulate the state table.
  - Derive the next-state equations for *A* and *B*.
- 6-21** Design a sequential circuit with two *JK* flip-flops, *A* and *B*, and two inputs, *E* and *x*. If *E* = 0, the circuit remains in the same state regardless of the value of *x*. When *E* = 1 and *x* = 1, the circuit goes through the state transitions from 00 to 01 to 10 to 11 back to 00, and repeats. When *E* = 1 and *x* = 0, the circuit goes through the state transitions from 00 to 11 to 10 to 01 back to 00, and repeats.

- 6-22** A sequential circuit has three flip-flops,  $A, B, C$ ; one input,  $x$ ; and one output,  $y$ . The state diagram is shown in Fig. P6-22. The circuit is to be designed by treating the unused states as don't-care conditions. The final circuit must be analyzed to ensure that it is self-correcting.
- Use  $D$  flip-flops in the design.
  - Use  $JK$  flip-flops in the design.

 

**FIGURE P6-22**

- 6-25** Design the following nonbinary sequence counters as specified in each case. Treat the unused states as don't-care conditions. Analyze the final circuit to ensure that it is self-correcting. If your design produces a nonself-correcting counter, you must modify the circuit to make it self-correcting.
- Design a counter with the following repeated binary sequence: 0, 1, 2, 3, 4, 5, 6. Use  $JK$  flip-flops.
  - Design a counter with the following repeated binary sequence: 0, 1, 2, 4, 6. Use  $D$  flip-flops.
  - Design a counter with the following repeated binary sequence: 0, 1, 3, 5, 7. Use  $T$  flip-flops.
  - Design a counter with the following repeated binary sequence: 0, 1, 3, 7, 6, 4. Use  $T$  flip-flops.