

Problem Set 7

1. A sequential circuit has two inputs x_1 and x_2 and one output z . Whenever an $x_1=1$ is observed, the output becomes 1 provided $x_2=1$ has been observed exactly twice since the last time $x_1=1$ was observed. The output remains 1 until $x_2=1$ is observed. Draw the state diagram as (a) a Mealy machine, and (b) as a Moore machine.

- 7-4** Design a sequential circuit whose state diagram is given in Fig. 6-31 using a 3-bit register and a 16×4 ROM.

 


FIGURE 6-31
State diagram for the circuit of Fig. 6-30

7-9 Draw the logic diagram of a 4-bit register with four *D* flip-flops and four 4×1 multiplexers with mode-selection inputs s_1 and s_0 . The register operates according to the following function table:

s_1	s_0	Register Operation
0	0	No change
0	1	Complement the four outputs
1	0	Clear register to 0 (synchronous with the clock)
1	1	Load parallel data

7-17 How many flip-flops will be complemented in a 10-bit binary ripple counter to reach the next count after the following count:

- (a) 1001100111;
- (b) 0011111111.

7-23 Design a synchronous BCD counter with *JK* flip-flops.

7-27 Using two circuits of the type shown in Fig. 7-19, construct a binary counter that counts from 0 through binary 64.

 


FIGURE 7-19
4-bit binary counter with parallel load