

University of Waterloo
Department of Electrical and Computer Engineering
ECE 223 Digital Circuits and Systems

Midterm Examination

Instructor: M. Sachdev
Total Marks = 100

Date Feb 16, 2000

Name:..... Student id:.....								
1.		2.	3.	4.		5.		Total:

Attempt all problems. If information appears to be missing make a reasonable assumption, state it and proceed. Calculators are not needed and are not allowed

Problem 1

(A): Convert following number from one radix to another [12]

(i) $(212.785)_{10}$ to radix 7

(ii) $(0110\ 1111)_2$ to radix 8

Name:..... Student id:.....

(B): How many different ways signed numbers can be represented in computers? Name them. Explain why in modern computers signed binary numbers are represented in “2’s complement” format? [8]

Name:..... Student id:.....

Problem 2

Given the following Boolean function, $F = xy'z + x'y'z + w'xy + wx'y + wxy$

- (i) Draw a corresponding Karnaugh map of the function
- (ii) Give minterm and maxterm expressions
- (iii) Simplify the function and implement it by NAND gates only [20]

Name:..... Student id:.....

Problem 3

Given the function $F(w, x, y, z) = \sum(0, 2, 3, 5, 7, 8, 10, 11, 14)$ [20]


- (i) Find all prime implicants
- (ii) Find all essential prime implicants
- (iii) Represent the function in the simplest “sum of products” form

Name:.....

Student id:.....

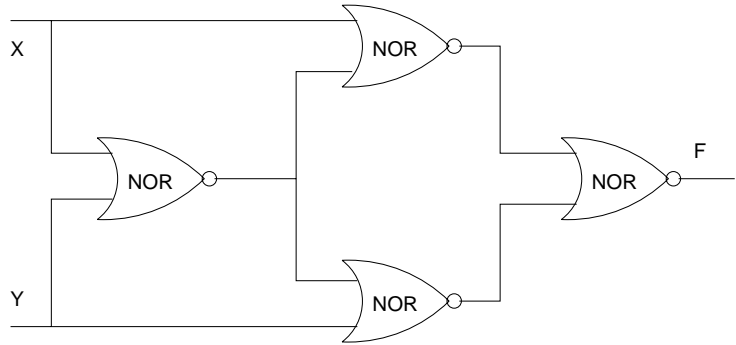Problem 4

(A): Verify algebraically that the circuit shown below generates the “exclusive-NOR” function [10]



(B): A “full subtractor” performs $[(x-y) - z]$ operation. [10]

- (i) Generate the truth table of the full subtractor
- (ii) Implement the function with logic gates

Name:..... Student id:.....

Problem 5

(A): Draw a gate level diagram of a 2-to-4 decoder [8]

(B): Redefine the carry propagate and carry generate as follows: [12]

$$\mathbf{P_i = A_i + B_i \quad \text{and} \quad G_i = A_i \cdot B_i}$$

Show that the output carry and output sum of a full adder becomes

$$\mathbf{C_{i+1} = (C_i' G_i' + P_i)'} = \mathbf{G_i + P_i \cdot C_i}$$

$$\mathbf{S_i = (P_i G_i') \oplus C_i}$$