

# E&CE 437

## Integrated VLSI Systems

### The Inverter

**M. Sachdev**

1 of 29

Department of Electrical & Computer Engineering, University of Waterloo

## Inverter: Introduction

- **The inverter is the simplest of all digital logic gates**
  - However, building understanding for its properties and operation is crucial for the design and analysis of larger/complexer logic gates
  - We will discuss,
  - General properties of an inverter (and logic gates)
  - Inverter implementation issues in MOS and bipolar technologies

2 of 29


Department of Electrical & Computer Engineering, University of Waterloo

## General Properties: Area and Complexity

- **Small area is a desirable property for a digital logic gate**
  - Larger packing density
  - Small parasitic capacitances
  - Shorter interconnects,
  - smaller chip area, hence higher number of devices per wafer (lower cost)
- **Fewer transistors for a logic gate usually results into smaller area**
  - Hence, minimum possible number of transistors for a give gate are important

3 of 29

## Inverter: Static Behavior

 


- **Static behavior of an inverter can be described by voltage transfer characteristics**
  - $V_{OL}$  and  $V_{OH}$  are low and high logic values of an inverter
  - $V_M$  is the logic (gate, or switching) threshold of an inverter

4 of 29
 
## Noise Margin

- In real life applications, output voltage of a gate may not have the nominal value
  - Owing to load, high switching speed, etc.
  - Hence, it is desirable to define an acceptable voltage range for logic 1 and logic 0, respectively



5 of 29

## Noise Margin, Regenerative Property & Fan-in, Fan-out

- For logic robustness large noise margin is desirable
- $NM_L = V_{IL} - V_{OL}$
- $NM_H = V_{OH} - V_{IH}$
- Logic gates have the property to restore the proper output logic values despite of non-ideal input levels (regenerative action)
- Fan-out is the number of logic gates that can be driven from a given logic gate (maximum fan-out)
- Fan-in is the number of inputs to a logic gate, large fan-in results in poorer performance

6 of 29

## Dynamic Behavior

- **Performance is an important attribute to any logic gate and determines its dynamic behavior**
  - Performance is measured by propagation delay through the logic gate ( $t_{plh}$  and  $t_{phl}$ ) and its rise and fall times
- **Performance is a strong function of the output load**
  - Often ring oscillator is used to compare different technologies objectively
  - However, ring oscillator performance has little correlation to actual logic gate or IC performance
- **Exercise**
  - *Simulate a 21 stage CMOS ring oscillator and measure its frequency*


7 of 29

## Power & Energy Consumption

- **Power consumption of a gate conveys how much heat it dissipates and how much energy is consumed per cycle**
  - Power consumption influence many critical decisions in the design of an IC (e.g., packaging, cooling, long term reliability, etc.)
  - $P_{peak} = i_{peak} V_{supply}$
  - $$P_{av} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_{supply}}{T} \int_0^T i_{supply}(t) dt$$
- **Power consumption has dynamic as well as static components**
  - Dynamic part is associated with charging and discharging of capacitance and is proportional to frequency
  - Static part is owing to sub-threshold leakage


8 of 29

## CMOS Inverter: Static Behavior


 


- A transistor has on resistance,  $R_{On}$ , when conducting, otherwise almost infinite resistance
  - In steady state, either PMOS or NMOS provides a low impedance path from output to VDD or GND
  - Infinite input impedance for the inverter

## Voltage Transfer Characteristics

 

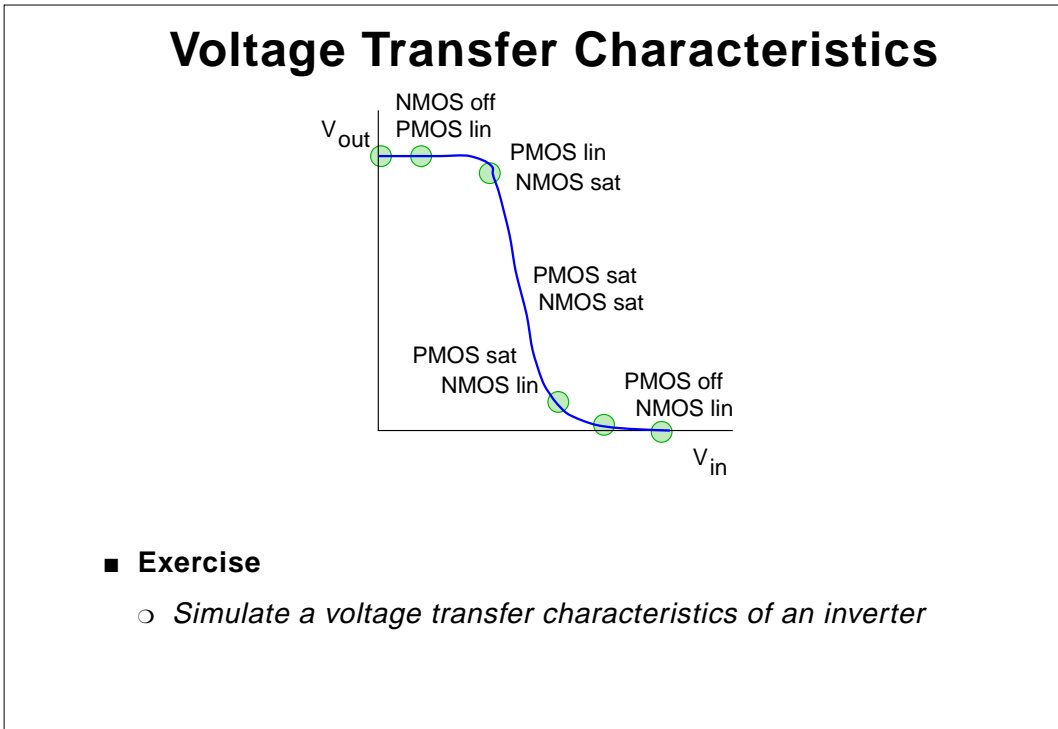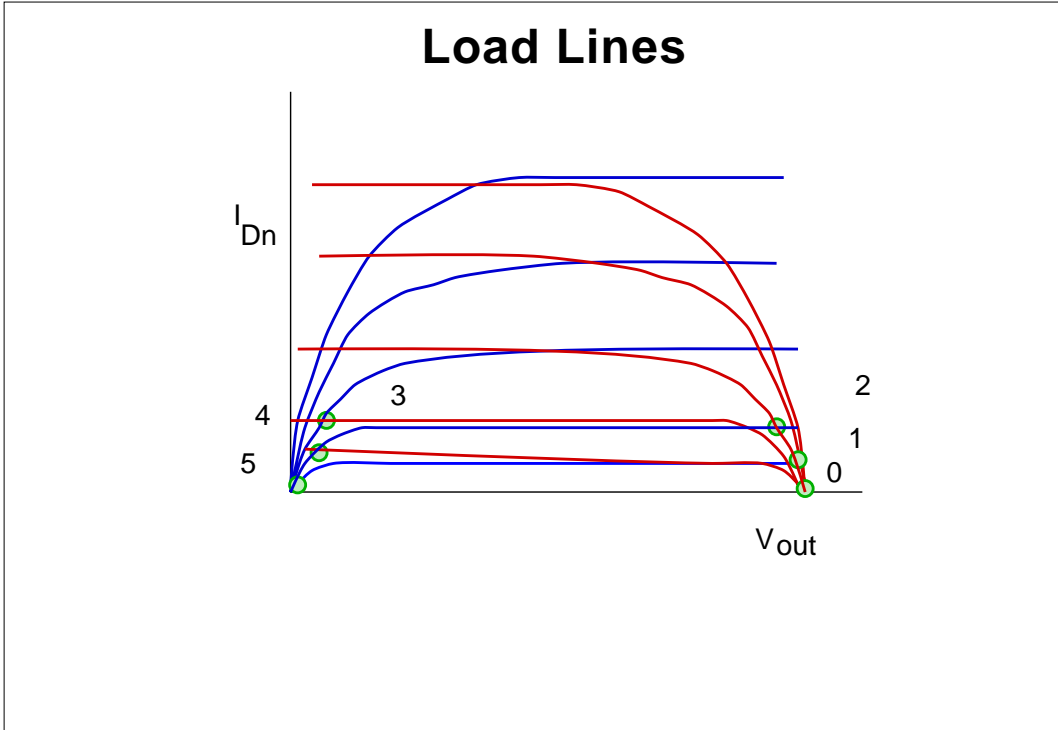- Voltage transfer characteristics for an inverter can be deduced from the load lines
  - Current characteristics of PMOS and NMOS should be superimposed on each other
  - I-V characteristics of PMOS should be transformed




# CMOS Inverter: An Amplifier

- In VTC of inverter, VOL and VOH were defined where

$$\frac{\partial V_{out}}{\partial V_{in}} = -1$$

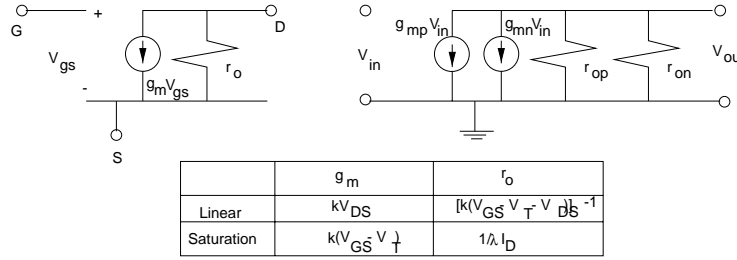- At this point, small signal gain, g, of the amplifier (inverter) is equal to -1



- Gain, g, is  $g = \frac{V_{out}}{V_{in}} = -(g_{mn} + g_{mp})(r_{on} \parallel r_{op}) = -1$  when  $V_{in} = V_{IH}$  and  $V_{IL}$
- At  $V_{in} = V_{IH}$ , PMOS and NMOS transistors can be assumed to be in saturation and linear regions, respectively
- $g_{mn} = k_n V_{out}$  and  $g_{mp} = k_p (V_{DD} - V_{IH} - |V_{Tp}|)$
- $\lambda_p = 0$ , ignoring the channel length modulation
- $r_{on} = \frac{1}{k_n (V_{IH} - V_{out} - V_{Tn})}$  and  $r_{op} = \infty$

■ **Putting these formulas in equation**

$$g = -(k_n V_{out} + k_p (V_{DD} - V_{IH} - |V_{Tp}|)) \left( \frac{1}{k_n (V_{IH} - V_{out} - V_{Tn})} \right) = -1$$

■ **Also, the static current through PMOS and NMOS should be the same**


$$k_n \left[ (V_{IH} - V_{Tn}) V_{out} - \frac{V_{out}^2}{2} \right] = \frac{k_p}{2} (V_{DD} - V_{IH} - |V_{Tp}|)^2$$

■ **With these two equations, equations for  $V_{out}$  and  $V_{IH}$  can be found**

- Similarly, equations can be derived for  $V_{in} = V_{IL}$
- In the same fashion we can find out an analytical expression for the inverter threshold ( $V_M$ )
  - $V_M$  is the point where  $V_{out} = V_{in}$ ; in this region both transistors are in saturation
  - Equating their currents
  - $$\frac{k_n}{2} [ (V_M - V_{Tn})^2 ] = \frac{k_p}{2} [ (V_{DD} - V_{IH} - |V_{Tp}|)^2 ]$$
  - Or
  - $V_M = \frac{r(V_{DD} - |V_{Tp}|) + V_{Tn}}{1 + r}$  where  $r = \sqrt{\frac{k_p}{k_n}}$
- If threshold voltages are equal and  $k_p = k_n$ , then  $V_M = V_{DD}/2$ 
  - Under these conditions, both PMOS and NMOS have equal strength and the inverter is balanced
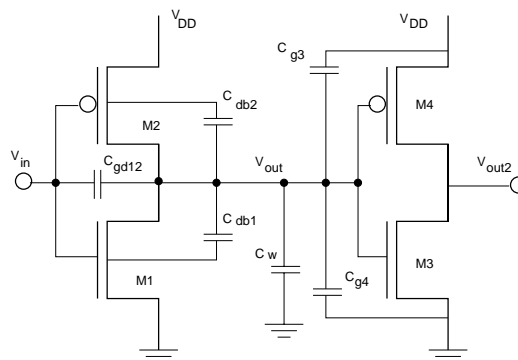
## CMOS Inverter: Dynamic Behavior

- Dynamic behavior (delay) of an inverter is determined by the time it takes to (dis)charge output capacitance



- We are interested in determining transient response of  $V_{out}$  assuming  $V_{in}$  is driven by an ideal voltage source



■ **Several capacitances contribute to overall capacitance**

- **C<sub>gd12</sub>**: M1, M2 in steady state are either in cut-off or in saturation; overlap capacitance of M1, M2 contributes to this capacitance; the gate capacitance is either between gate and bulk (cut-off) or gate and source (saturation)
- **C<sub>db1</sub> and C<sub>db2</sub>**: Capacitance between drain and bulk is due to reverse biased pn-junction. This is a non-linear capacitance which is approximated as linear
- **C<sub>w</sub>**: This is the capacitance due to interconnect
- **C<sub>g3</sub> and C<sub>g4</sub>**: We assume that the gate capacitance of loading gates is between V<sub>out</sub> and V<sub>DD</sub> (GND). Overlap and gate capacitances are clustered into a single component

## Propagation Delay

■ **The propagation delay can be computed by integrating the capacitor (dis)charge current**

$$t_p = C_L \int_{v_1}^{v_2} \frac{1}{i(v)} (dv) = \frac{C_L(V_2 - V_1)}{I_{av}}$$

■ **Propagation delay is defined as time between input reaching 50% to output reaching 50% of full value**

$$t_p = \frac{C_L(V_{OH} - V_{OL})/2}{|I_{av}|}$$

- This equation holds for both t<sub>plh</sub> and t<sub>phl</sub> transitions
- Assuming that the input transition (V<sub>DD</sub> -> 0) is abrupt then only PMOS contributes to the current
- The PMOS is in saturation so long V<sub>out</sub> < |V<sub>Tp</sub>| and after that it is in linear mode, therefore currents in respective regions

- $I(V_{out} = 0) = \frac{k_p}{2} \langle V_{DD} - |V_{Tp}| \rangle^2$
- and
- $I\left(V_{out} = \frac{V_{DD}}{2}\right) = k_p \langle (V_{DD} - |V_{Tp}|) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{8} \rangle$
- 
- The average current,  $I_{av}$ , can be computed as

$$I_{av} = \left( \frac{I(V_{out} = 0) + I\left(V_{out} = \frac{V_{DD}}{2}\right)}{2} \right) = \frac{k_p}{2} \left\langle \frac{7V_{DD}^2}{8} + \frac{|V_{Tp}|^2}{2} - \frac{3V_{DD}|V_{Tp}|}{2} \right\rangle$$

- A simpler equation is arrived at if we assume that PMOS remains in saturation from  $V_{out} = 0$  to  $V_{DD}/2$ ; In this case

$$t_{plh} = \frac{C_L(V_{DD})}{k_p \langle V_{DD} - |V_{Tp}| \rangle^2} \approx \frac{C_L}{k_p V_{DD}} \quad \text{If } V_{DD} \gg V_{Tp}$$

- Similarly for  $t_{phl}$

$$t_{phl} = \frac{C_L(V_{DD})}{k_n \langle V_{DD} - V_{Tn} \rangle^2} \approx \frac{C_L}{k_n V_{DD}}$$

- therefore,

$$t_p = \frac{1}{2}(t_{plh} + t_{phl}) = \frac{C_L}{2V_{DD}} \left( \frac{1}{k_p} + \frac{1}{k_n} \right)$$

■ **Design Challenges, how to reduce  $t_p$ ?**

- Increase  $k_p$  and  $k_n$
- Reduce  $C_L$
- Increase  $V_{DD}$
- .....

## Second Order Performance Issues

- **Previously, we assumed that input transition is abrupt and only one transistor is on during (dis)charging process**
  - Signals have finite rise/fall times and for a brief period both PMOS and NMOS are on
  - $t_{plh}$  increases as input fall time is increased
  - Smaller rise/fall times are also desirable for low power consumption
- **We assumed that the maximum (dis)charge current is saturation current of transistors (proportional to  $V_{DD}^2$ )**
  - In small geometries, owing to velocity saturation,  $I_{av}$  is proportional to  $V_{DD}$
  - Therefore, if  $V_{DD} \gg V_T$   $t_p \approx \frac{C_L}{2} \left( \frac{1}{k_p} + \frac{1}{k_n} \right)$

21 of 29


- **In the timing analysis, we have so far ignored the source and drain resistance of (dis)charging device**
  - The source resistance affects the performance
    - (i): Effective  $V_{GS}$  is reduced (i.e., lowering the saturation current)
    - (ii): The source is no longer grounded,  $V_T$  of the transistor is increased due to body effect
  - $$I_{n, sat, R} = \frac{k_n}{2} (V_{DD} - V_S - V_S V_{Tn})^2$$
  - where  $V_S = R_S \cdot I_{n, sat, R}$

22 of 29

# Power Consumption and Power-Delay Product
 
## ■ Static power consumption

- Ideally, there should be no static power consumption since both transistors are never on simultaneously




- A small component is contributed by reverse biased diode leakage current

- As mentioned before, at  $V_{GS} = 0$ , the transistor current is not absolutely 0 but a small component (sub-threshold current)
- As we scale the technology,  $V_T$  is also scaled resulting in exponentially higher sub-threshold current
- $P_{stat} = I_{leakage} V_{DD}$

## ■ Majority of power is consumed during switching; two components

 
### ■ 1. Charging of load capacitance, $C_L$



- Energy,  $E_{VDD}$  taken from supply during the transition and  $E_C$  is stored on the capacitor at the end of transition
- $$E_{VDD} = \int_0^{\infty} i_{VDD}(t) V_{DD} dt = V_{DD} \int_0^{\infty} C_L \frac{dv_{out}}{dt} dt = C_L V_{DD} \int_0^{V_{DD}} dv_{out} = C_L V_{DD}^2$$
- $$E_C = \int_0^{\infty} i_{VDD}(t) v_{out} dt = \int_0^{\infty} C_L \frac{dv_{out}}{dt} v_{out} dt = C_L \int_0^{V_{DD}} v_{out} dv_{out} = \frac{C_L V_{DD}^2}{2}$$
- Energy stored on the capacitor is only half of what is drawn from the supply, rest of it dissipated in the PMOS transistor
- Energy dissipation is independent of transistor dimensions
- During the discharge phase, charge is removed from the capacitor and its energy is dissipated in the NMOS transistor
- Hence, in each switching cycle fixed energy  $C_L V_{DD}^2$  is taken from the supply, to compute the power, we must multiply energy by frequency,  $P_{dyn} = C_L V_{DD}^2 f$
 
## ■ 2. Direct-Path Currents

- Owing to finite rise and fall times, both transistors are on for a brief period of time during transitions



- If we assume that the current spikes can be approximated as triangular waveform and  $V_{DD} \gg |V_T|$ ; then energy consumed per period
- $$E_{dp} = V_{DD} \frac{I_{peak} t_r}{2} + V_{DD} \frac{I_{peak} t_f}{2} = V_{DD} I_{peak} \left( \frac{t_r + t_f}{2} \right)$$

## Total Power Dissipation of an Inverter

- Total power is the sum of three components

- $P_{tot} = P_{dyn} + P_{dp} + P_{stat} = C_L V_{DD}^2 f + V_{DD} I_{peak} \left( \frac{t_r + t_f}{2} \right) f + V_{DD} I_{leak}$

- Energy per operation or Power-Delay Product

- Power-Delay Product (PDP) is a quality measure for a logic gate and is defined as amount of energy consumed in each cycle

- Exercise

- Optimize a CMOS inverter for minimum PDP. Also optimize the inverter for minimum power and minimum delay.

27 of 29

## Technology Scaling & CMOS

- Ever since ICs were invented, dimensions are scaled to

- Integrated more transistors in the same area
- Allow higher operational speed

- Scaling has profound impact on many aspects of ICs

- Constant Voltage Scaling

- All device dimensions are scaled by a factor S
- Voltage (i.e.,  $V_{DD}$ ) after the scaling is same as before
- This method of scaling is followed till 0.8 micron
- However for lower geometries, higher electric field resulted in poor device reliability

28 of 29

■ **Therefore, for advanced technologies today Constant Field Scaling is followed**

- All dimensions including power supply is scaled by a factor S

Parameter	Relation	CVS	CFS
$W, L, t_{ox}$		$1/S$	$1/S$
$V_{DD}, V_T$		1	$1/S$
Area	WL	$1/S^2$	$1/S^2$
$C_{ox}$	$t_{ox}$	S	S
$C_L$	$C_{ox}WL$	$1/S$	$1/S$
$k_n, k_p$	$C_{ox}W/L$	S	S
$I_{av}$	$k_{n,p}V^2$	S	$1/S$
$J_{av}$	$I_{av}/Area$	$S^3$	S
$t_p$ (intrinsic)	$C_L V / I_{av}$	$1/S^2$	$1/S$
$P_{av}$	$C_L V^2 / t_p$	S	$1/S^2$
PDP	$C_L V^2$	$1/S$	$1/S^3$