

ELE-B7 Power Systems Engineering


Load Flow (*Gauss-Seidel Method*)

Dr. Ramadan El-Shatshat

Classification of buses:


Different buses at the network can be classified as:

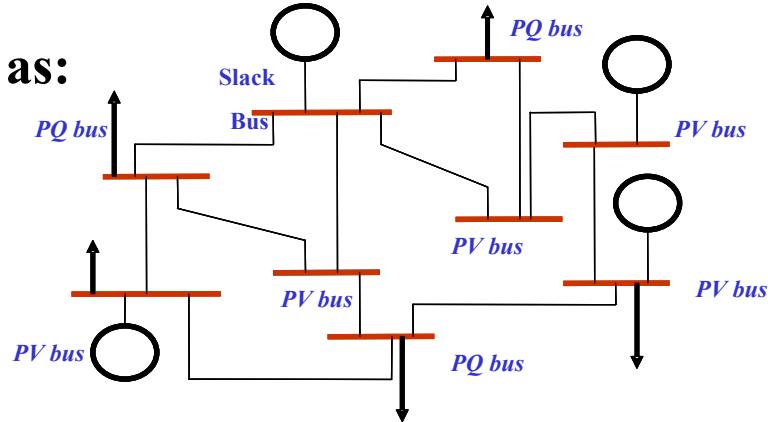1. The Load Buses (**PQ bus**)
2. The Generator Bus (**PV bus**)
3. The Slack or Swing Bus



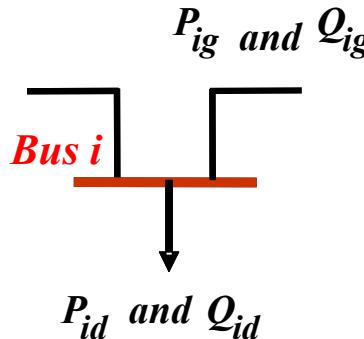1. The Load Buses (**PQ bus**)

A non-generator bus. The active and reactive powers are specified at this bus. The voltage magnitude and phase angle are unknown.



P_i and Q_i are known & $|V_i|$ and δ_i are unknown

Generators Power: $P_{ig} = 0$ and $Q_{ig} = 0$

Delivered Power: P_{id} and Q_{id} are known

In practice, the load real power is known from measurement, load forecasting or historical record and the reactive power is assumed based on 0.85 pf.


$$P_{i,sch} = P_{ig} - P_{id} = -P_{id} \quad \text{and}$$

$$Q_{i,sch} = Q_{ig} - Q_{id} = -Q_{id}$$

2. The Generator Bus (*PV bus*)

The bus is also known as “*Voltage controlled bus*” because the voltage magnitude can be kept constant. At this bus the **net** active power and the voltage magnitude are specified. The reactive power and the voltage phase angle are unknown.

P_i and $|V_i|$ are known & Q_i and δ_i are unknown

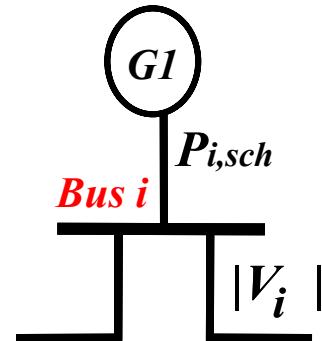

NOTE: There are certain buses without generators may have voltage controlled capability. At these buses the real power generation is zero.

3. The Slack or Swing Bus

Because the system losses are not known precisely before completing the power flow solution, it is not possible to specify the real power injected at every bus. Hence, The real power of one of the generator buses is allowed to swing. The swing bus supplies the slack between the scheduled real power generation and the sum of all loads and system losses. The voltage angle of the slack bus serves as a reference, $\delta_i = 0$

$|V_i|$ and δ_i are known & P_i and Q_i are unknown

NOTE:

Real Power losses = Total generation – Total load

$$P_L = \sum_{i=1}^N P_{gi} - \sum_{i=1}^N P_{di} = \sum_{i=1}^N P_i$$

In the load flow problem, we select the slack bus at which the power Pg is not scheduled.

After solving the load flow problem, the difference (Slack) between the total specified power (P) going into the system at all other buses and the total output (P) plus the losses (I^2R) are assigned to the slack bus.

For this reason a generator bus must be selected as a slack bus.

Voltage of the swing bus is selected as a reference. Generally, the bus of the largest generator is selected as swing bus and numbered as bus 1.

Solution of Non-Linear Equations

The two *load flow equations* are:

$$P_i = |V_i| \sum_{p=1}^n |Y_{ip}| |V_p| \cos(\delta_i - \delta_p - \gamma_{ip})$$

$$Q_i = |V_i| \sum_{p=1}^n |Y_{ip}| |V_p| \sin(\delta_i - \delta_p - \gamma_{ip})$$

These equations provide *the calculated value* of *net* real power and *net* reactive power entering bus ‘*i*’. The equations are non-linear and only a numerical solution is possible. There are different methods could be implemented to solve these equations. Among those is the Gauss-Seidel method.

Gauss-Seidel Method

Consider a system of non-linear equations having “*n*” unknowns x_1, x_2, \dots, x_n

$$f_1(x_1, x_2, \dots, x_n)$$

$$f_2(x_1, x_2, \dots, x_n)$$

..

$$f_n(x_1, x_2, \dots, x_n)$$

Rearranging, then

$$x_i = f_i(x_1, x_2, \dots, x_n) \quad \text{Eq. 1}$$

$$1 \leq i \leq n$$

Assuming initial values,

$$x_1^o, x_2^o, \dots, x_n^o$$

Substituting the initial values in **Eq. 1**, then

first iteration $\overrightarrow{x_1^I} = f_1^I(x_1^o, x_2^o, \dots, x_n^o)$

first variable $\overrightarrow{x_2^I} = f_2^I(x_1^I, x_2^o, \dots, x_n^o)$

All values are initial values
 $x_1^o, x_2^o, \dots, x_n^o$

$x_1 = x_1^I$ from previous step
and all other values are
initial values
 x_2^o, \dots, x_n^o

$$x_3^I = f_3^I(x_1^I, x_2^I, x_3^o, \dots, x_n^o)$$

$x_1 = x_1^I$ & $x_2 = x_2^I$
and
 x_3^o, \dots, x_n^o

Or in general

$$x_i^I = f_i^I(x_1^I, x_2^I, \dots, x_{i-1}^I, x_i^o, \dots, x_n^o)$$

Where x_i^1 is the first approximation of x_i using the initial assumed values.

The k^{th} approximation of x_i is:

$$\xrightarrow{\substack{K^{th} \text{ iteration} \\ i^{th} \text{ variable}}} x_i^k = f_i^1(x_1^k, x_2^k, \dots, x_{i-1}^k, x_i^{k-1}, x_{i+1}^{k-1}, \dots, x_n^{k-1})$$

The changes in the magnitude of each variable x_i^k from its value x_i^{k-1} at the previous iteration is:

$$\Delta x_i = x_i^k - x_i^{k-1}$$

If $\Delta x_i < \varepsilon$ then the solution has converged.

Where, ε is a small value (for example : $\varepsilon = 0.001$)

EXAMPLE:

For the following equation, find an accurate value for x up to 5 decimal places.

$$2x - \log(x) = 7$$

SOLUTION:

Using Gauss-Seidel

$$x = 0.5(7 + \log x)$$

$$x^0 = 1$$

$$x^1 = 0.5(7 + \log 1) = 3.5$$

1st iteration

$$x^1 = 3.5$$

$$x^2 = 0.5(7 + \log 3.5) = 3.772034$$

2nd iteration

$$x^2 = 3.772034$$

$$x^3 = 0.5(7 + \log 3.772034) = 3.788287$$

$$x^3 = 3.788287$$

$$x^4 = 0.5(7 + \log 3.788287) = 3.789221$$

$$x^5 = 3.789274$$

$$x^6 = 3.789278 \quad \varepsilon = 0.000004$$

EXAMPLE:

For the following equations, find an x and y after 4 iterations.

$$x = 0.7 \sin x + 0.2 \cos y \quad & \quad y = 0.7 \cos x - 0.2 \sin y$$

SOLUTION:

Using Gauss-Seidel, assuming initial values

$$x^0 = y^0 = 0.5 \text{ (rad)}$$

$$x^1 = 0.7 \sin x^0 + 0.2 \cos y^0$$

$$x^1 = 0.7 \sin 0.5 + 0.2 \cos 0.5$$

$$x^1 = 0.51111$$

$$y^1 = 0.7 \cos 0.51111 - 0.2 \sin 0.5$$

$$y^1 = 0.51465$$

$$x^2 = 0.516497$$

$$y^2 = 0.510241$$

$$x^3 = 0.520211$$

$$y^3 = 0.509722$$

$$x^4 = 0.522520$$

$$y^4 = 0.509007$$

Gauss-Seidel Method for Load Flow Analysis

Advantages

1. *Simplicity*
2. *Small computer memory requirement*
3. *Less computational time per iteration*

Disadvantages

1. *Slow rate of convergence, and therefore large number of iterations.*
2. *Increase in the number of iterations as the number of system buses increases.*
3. *The speed of convergence is affected by the selected slack bus.*

I - G-S Method when PV buses are absent

Assuming a power system in which the voltage *controlled buses are absent*. If the system has n buses, then; one bus will be considered as a slack bus and the other $n-1$ buses are load buses (**PQ-buses**).

For the Slack or Swing Bus:

$|V_i|$ and $\delta_i = 0$ are known & P_i and Q_i are unknown

The swing bus voltage is taken as a reference. Its voltage magnitude is known and its phase shift angle is set equal to zero.

For $(n-1)$ Load Buses (PQ bus):


P_i and Q_i are known & $|V_i|$ and δ_i are unknown

Using Gauss-Seidel Method, we assume the *initial values* for the magnitude and phase shift angle of $(n-1)$ buses. These values are *updated at each iteration*.

For an ‘ n ’ bus system

$$I_{bus} = Y_{bus} V_{bus} \quad \dots \dots \text{Eq. 1}$$

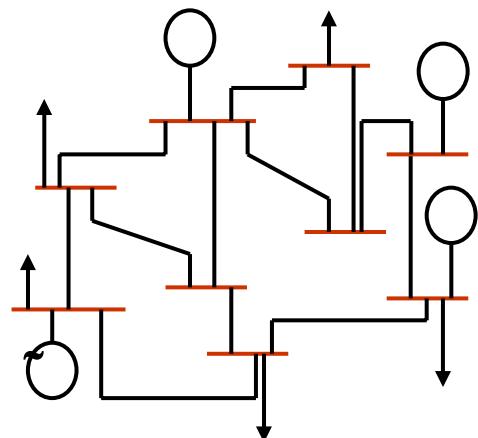For the i^{th} bus of an ‘ n ’ bus system, the current entering this bus is:



$$I_i = Y_{i1} V_1 + Y_{i2} V_2 + \dots + Y_{ii} V_i + \dots + Y_{in} V_n \quad \dots \dots \text{Eq. 2}$$

$$I_i = Y_{ii} V_i + \sum_{\substack{p=1 \\ p \neq i}}^n Y_{ip} V_p \quad \dots \dots \text{Eq. 3}$$

$$V_i = \frac{1}{Y_{ii}} \left(I_i - \sum_{\substack{p=1 \\ p \neq i}}^n Y_{ip} V_p \right) \quad \dots \dots \text{Eq. 4}$$

In power systems, power is known rather than currents. The complex power injected into the i^{th} bus is:

$$S_i = P_i + jQ_i = V_i I_i^* \quad Eq. 5$$

$$S_i^* = V_i^* I_i \quad Eq. 6$$

OR

$$I_i = \frac{P_i - jQ_i}{V_i^*} \quad Eq. 7$$

Substituting in Eq. 4

$$V_i = \frac{1}{Y_{ii}} \left(\frac{P_i - jQ_i}{V_i^*} - \sum_{\substack{p=1 \\ p \neq i}}^n Y_{ip} V_p \right) \quad Eq. 8$$

Rearranging in GS method
“Vi” is moved to the left hand side of the equation.

Since bus 1 is the slack bus “reference”, then V_i represents $n-1$ set of equations for $i = 2, 3, \dots, n$. These equations will be solved using G-S method for the unknowns V_2, V_3, \dots, V_n .

NOTES:

- Eq. 8 can be written as:

NOTE
The values for P and Q
are the scheduled
values for PQ Bus.

$$V_i = \frac{1}{V_i^*} \frac{P_i - jQ_i}{Y_{ii}} - \sum_{\substack{p=1 \\ p \neq i}}^n \frac{Y_{ip}}{Y_{ii}} V_p \quad \dots \dots \text{Eq. 9}$$

$$V_i = \frac{K_i}{V_i^*} - \sum_{\substack{p=1 \\ p \neq i}}^n L_{ip} V_p \quad \dots \dots \text{Eq. 10}$$

$$K_i = \frac{P_i - jQ_i}{Y_{ii}} \quad \text{and} \quad L_{ip} = \frac{Y_{ip}}{Y_{ii}}$$

The values for K_i and L_{ip} are computed once in the beginning and used in every iteration.

- The voltages at all the buses in a power system are close to 1.0 pu. Therefore, we can start the G-S iteration process assuming initial values for the voltages equal to 1.0 and making zero angle.

$$V_2^o = V_3^o = \dots \dots V_n^o = 1 \angle 0$$

- At each step in the iteration process use the **most updated values** for the voltages to compute the new values for the bus voltages.

$$V_i = \frac{K_i}{V_i^*} - \sum_{\substack{p=1 \\ p \neq i}}^n L_{ip} V_p \quad Eq. 11$$

$$V_i = \frac{K_i}{V_i^*} - \sum_{p=1}^{i-1} L_{ip} V_p - \sum_{p=i+1}^n L_{ip} V_p \quad Eq. 12$$

Therefore, for the ($k^{th}+1$) iteration,

$$V_i^{k+1} = \frac{K_i}{(V_i^k)^*} - \sum_{p=1}^{i-1} L_{ip} V_p^{(k+1)} - \sum_{p=i+1}^n L_{ip} V_p^k \quad Eq. 13$$

for $i = 1, 2, \dots, n$

The iteration process is continuous till the convergence occurs, i.e.;

$$| \Delta V_i^{k+1} | = | V_i^{k+1} | - | V_i^k | < \epsilon \quad Eq. 14$$


for $i = 1, 2, \dots, n$

4. The ***current and complex power*** at i^{th} bus are:

$$I_i = Y_{i1} V_1 + Y_{i2} V_2 + \dots + Y_{ii} V_i + \dots + Y_{in} V_n$$

And

$$S_i = P_i + jQ_i = V_i I_i^*$$

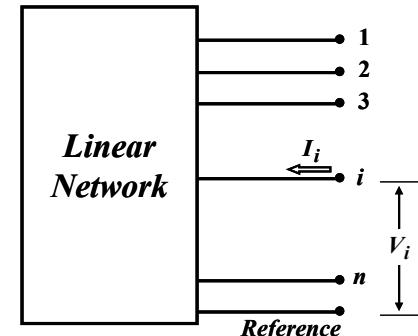

$$S_i^* = P_i - Q_i = V_i^* I_i$$

Or

$$P_i - jQ_i = V_i^* (Y_{i1} V_1 + Y_{i2} V_2 + \dots + Y_{ii} V_i + \dots + Y_{in} V_n)$$

$$P_i = \text{Re}\{V_i^* (Y_{i1} V_1 + Y_{i2} V_2 + \dots + Y_{ii} V_i + \dots + Y_{in} V_n)\}$$

$$Q_i = -\text{Im}\{V_i^* (Y_{i1} V_1 + Y_{i2} V_2 + \dots + Y_{ii} V_i + \dots + Y_{in} V_n)\}$$

The two equations are known as the ***rectangular form*** of the ***load flow equations***. They provide **the calculated value** of ***net*** real power and ***net*** reactive power **entering** bus ' i '.

EXAMPLE:

For the three bus system. Write the expression for the bus voltages using GS method.

SOLUTION:

The system contains 3 buses, ($n=3$).

i- Select bus 1 as a slack bus “reference”.

$$|V_1| = 1 \text{ and } \delta_1 = 0$$


ii- Buses 2 and 3 are load buses.

$P_2, P_3, Q_2 \text{ and } Q_3$ are known

$V_2, V_3, \delta_2 \text{ and } \delta_3$ are unknown

$$V_2 = \frac{K_2}{V_2^*} - \sum_{\substack{p=1 \\ p \neq 2}}^3 L_{2p} V_p$$
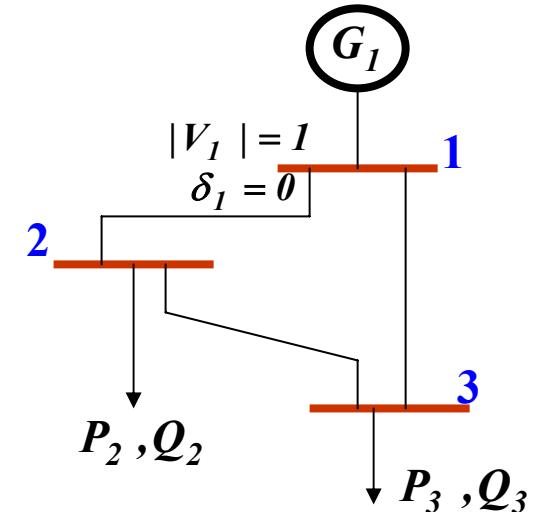
$$V_2 = \frac{1}{V_2^*} \frac{P_2 - jQ_2}{Y_{22}} - \sum_{\substack{p=1 \\ p \neq 2}}^3 \frac{Y_{2p}}{Y_{22}} V_p$$



NOTE

The load flow problem is solved when the mismatch is equal to zero.

Calculated values
=
Scheduled values

NOTE

The values for P and Q
are the scheduled
values

$$V_2 = \frac{1}{V_2^*} \frac{P_2 - jQ_2}{Y_{22}} - \left[\frac{Y_{21}}{Y_{22}} V_1 + \frac{Y_{23}}{Y_{22}} V_3 \right] \quad \dots\dots \text{Eq. 15}$$

$$V_3 = \frac{1}{V_3^*} \frac{P_3 - jQ_3}{Y_{33}} - \left[\frac{Y_{31}}{Y_{33}} V_1 + \frac{Y_{32}}{Y_{33}} V_2 \right] \quad \dots\dots \text{Eq. 16}$$

Using GS method, **select the initial values** for the unknowns as:

$$V_2^o = V_3^o = 1\angle 0$$

Start the first iteration

$$V_2^1 = \frac{1}{(V_2^o)^*} \frac{P_2 - jQ_2}{Y_{22}} - \left[\frac{Y_{21}}{Y_{22}} V_1 + \frac{Y_{23}}{Y_{22}} V_3^o \right] \quad \dots\dots \text{Eq. 17}$$

The most updated voltage value is the initial value

$$V_3^1 = \frac{1}{(V_3^o)^*} \frac{P_3 - jQ_3}{Y_{33}} - \left[\frac{Y_{31}}{Y_{33}} V_1 + \frac{Y_{32}}{Y_{33}} V_2^1 \right] \quad \dots\dots \text{Eq. 18}$$

The most updated voltage value is from this iteration

Start the second iteration

$$V_2^2 = \frac{1}{(V_2^1)^*} \frac{P_2 - jQ_2}{Y_{22}} - \left[\frac{Y_{21}}{Y_{22}} V_1 + \frac{Y_{23}}{Y_{22}} V_3^1 \right] \quad \begin{array}{l} \text{The most updated voltage} \\ \text{value is from previous} \\ \text{iteration} \end{array} \quad \dots \dots \text{Eq. 19}$$

$$V_3^2 = \frac{1}{(V_3^1)^*} \frac{P_3 - jQ_3}{Y_{33}} - \left[\frac{Y_{31}}{Y_{33}} V_1 + \frac{Y_{32}}{Y_{33}} V_2^2 \right] \quad \begin{array}{l} \text{The most updated voltage} \\ \text{value is from this iteration} \end{array} \quad \dots \dots \text{Eq. 20}$$

Compare the results for convergence

$$|\Delta V_i^{k+1}| = |V_i^{k+1}| - |V_i^k| < \varepsilon \quad \text{for } i = 1, 2, \dots, n$$

$$|\Delta V_2^2| = |V_2^2| - |V_2^1| < \varepsilon \quad \dots \dots \text{Eq. 21}$$


$$|\Delta V_3^2| = |V_3^2| - |V_3^1| < \varepsilon \quad \dots \dots \text{Eq. 22}$$

If Eqs. 21, 22 are not satisfied then start a new iteration.

EXAMPLE 1:

For the system shown in the figure, the line impedances are as indicated in per unit on 100MVA base.

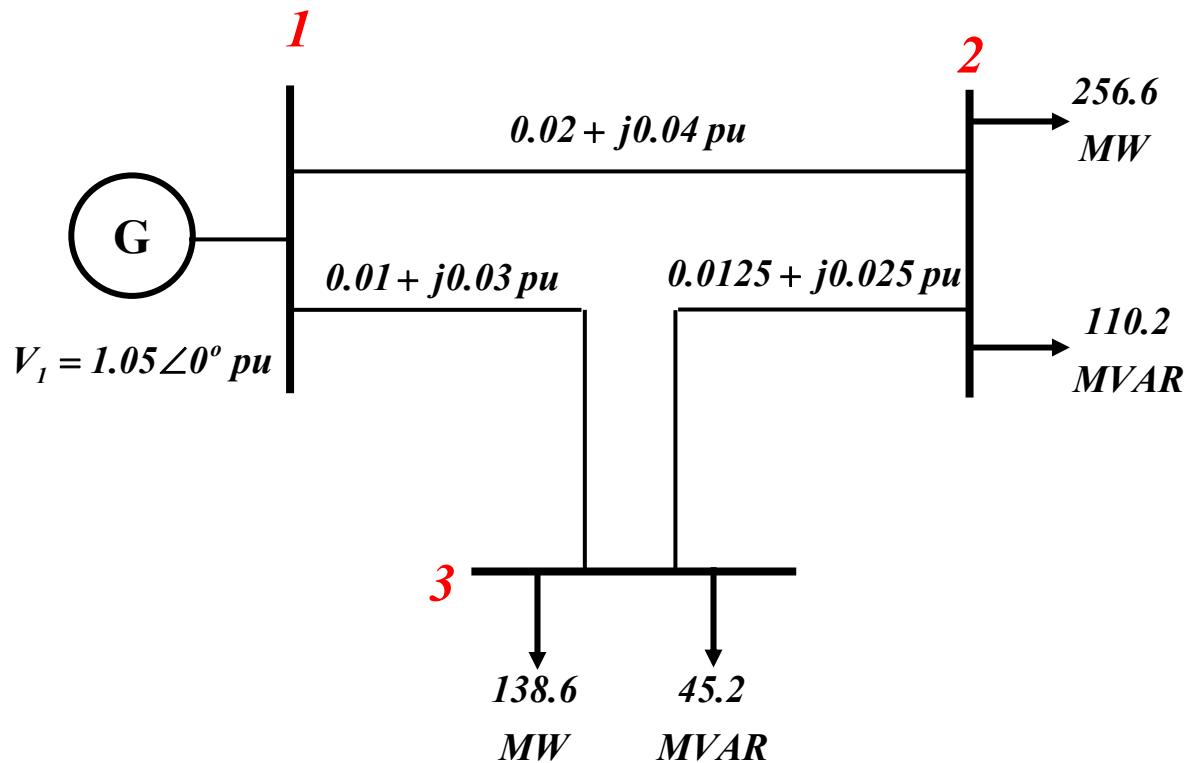- A. Using Gauss-Seidel method find the bus voltages after 7 iterations.
- B. Using the bus voltages find the Slack bus real and reactive power.




Formulation of the Bus Admittance Matrix

$$y_{12} = \frac{1}{0.02 + j0.04} = 10 - j20 = y_{21}$$

$$y_{13} = \frac{1}{0.01 + j0.03} = 10 - j30 = y_{31}$$
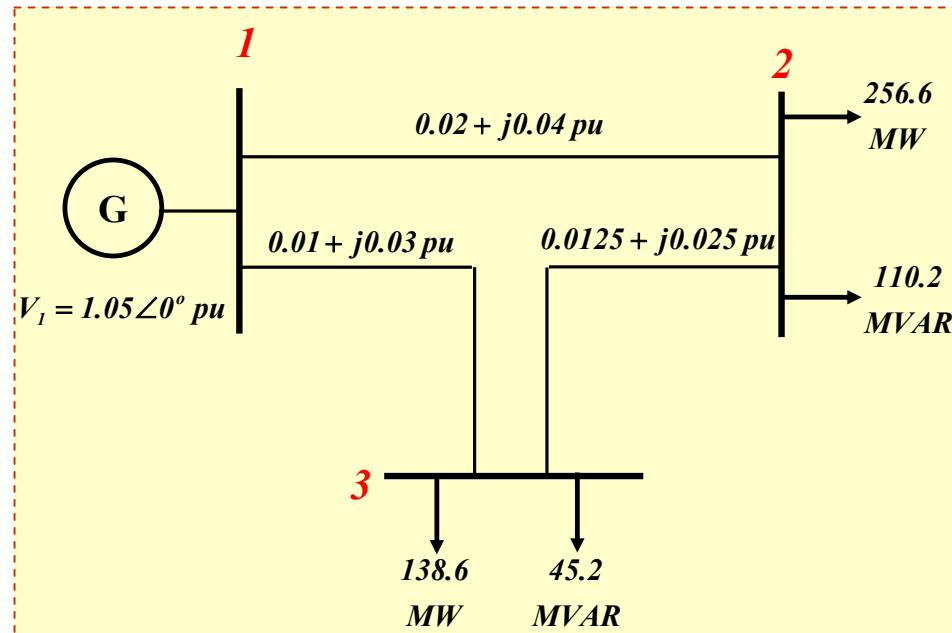
$$y_{23} = \frac{1}{0.0125 + j0.025} = 16 - j32 = y_{32}$$




$$Y_{bus} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} = \begin{bmatrix} y_{12} + y_{13} & -y_{12} & -y_{13} \\ -y_{21} & y_{21} + y_{23} & -y_{23} \\ -y_{31} & -y_{32} & y_{31} + y_{32} \end{bmatrix}$$

$$Y_{bus} = \begin{bmatrix} 20 - j50 & -10 + j20 & -10 + j30 \\ -10 + j20 & 26 - j52 & -16 + j32 \\ -10 + j30 & -16 + j32 & 26 - j62 \end{bmatrix}$$

Classification of buses:

Bus 1: Slack Bus

$$V_1 = 1.05 \angle 0^\circ \text{ pu}$$

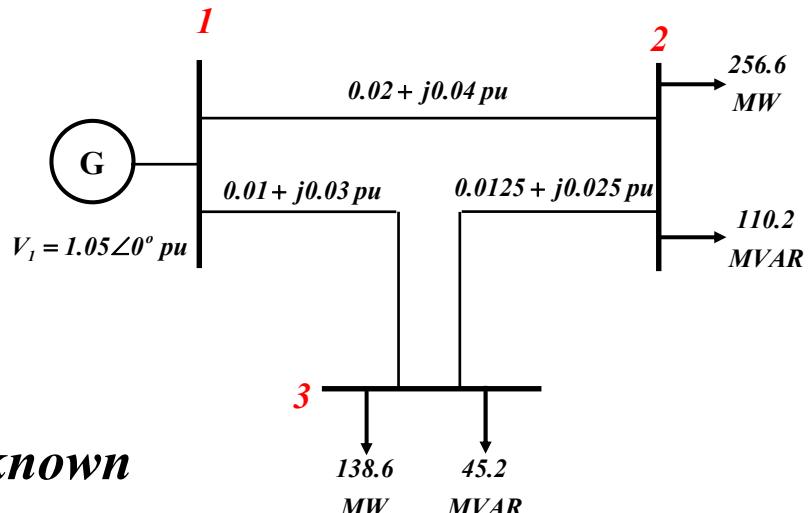

Buses 2 and 3: Load Buses (*PQ bus*)

P_2, P_3, Q_2 and Q_3 are known

V_2, V_3, δ_2 and δ_3 are unknown

$$P_{2,d} = 256.6 \text{ MW} \quad Q_{2,d} = 110.2 \text{ MVAR}$$

$$P_{3,d} = 138.6 \text{ MW} \quad Q_{3,d} = 45.2 \text{ MVAR}$$


$$P_{i,sch} = P_{gi} - P_{di}$$

&

$$Q_{i,sch} = Q_{gi} - Q_{di}$$

$$S_{i,sch} = P_{i,sch} + jQ_{i,sch}$$
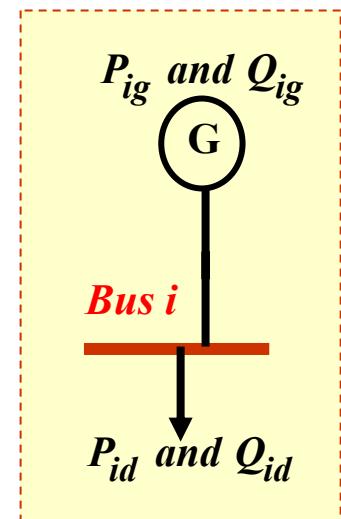
$$S_{2,sch} = (P_{2,g} - P_{2,d}) + j(Q_{2,g} - Q_{2,d})$$



$$S_{2,sch} = \frac{(P_{2,g} - P_{2,d}) + j(Q_{2,g} - Q_{2,d})}{Base\ MVA} \ pu$$

$$S_{2,sch} = \frac{(0 - 256.6) + j(0 - 110.2)}{100\ MVA} \ pu$$

$$S_{2,sch} = -2.566 - j1.102 \ pu$$

$$S_{3,sch} = -1.386 - j0.452 \ pu$$

Reminder
The bus admittance matrix
is

$$\begin{bmatrix} 20 - j50 & -10 + j20 & -10 + j30 \\ -10 + j20 & 26 - j52 & -16 + j32 \\ -10 + j30 & -16 + j32 & 26 - j62 \end{bmatrix}$$

Using GS method, select the **initial values** for the unknowns as:

$$V_2^o = V_3^o = 1\angle 0$$

Start the first iteration

$$V_2^1 = \frac{1}{(V_2^o)^*} \frac{P_{2,sch} - jQ_{2,sch}}{Y_{22}} - \left[\frac{Y_{21}}{Y_{22}} V_1 + \frac{Y_{23}}{Y_{22}} V_3^o \right]$$

$$S_{i,sch}^* = P_{i,sch} - jQ_{i,sch}$$

$$V_2^1 = \frac{1}{(1.0)^*} \frac{-2.566 + j1.102}{26 - j52} - \left[\frac{-10 + j20}{26 - j52} 1.05 + \frac{-16 + j32}{26 - j52} 1.0 \right]$$

OR, to simplify the calculations, we have:

$$V_i = \frac{1}{V_i^*} \frac{P_i - jQ_i}{Y_{ii}} - \sum_{\substack{p=1 \\ p \neq i}}^n \frac{Y_{ip}}{Y_{ii}} V_p$$

$$V_2 = \frac{K_2}{V_2^*} - \sum_{\substack{p=1 \\ p \neq 2}}^n L_{2p} V_p$$

$$V_2^I = \frac{K_2}{(V_2^o)^*} - [L_{21} V_1 + L_{23} V_3^o]$$

Reminder
The bus admittance matrix
is

$$\begin{bmatrix} 20-j50 & -10+j20 & -10+j30 \\ -10+j20 & 26-j52 & -16+j32 \\ -10+j30 & -16+j32 & 26-j62 \end{bmatrix}$$

The values for K_i and L_{ip} are computed once in the beginning and used in every iteration.

$$K_2 = \frac{P_2 - jQ_2}{Y_{22}}$$

$$L_{21} = \frac{Y_{21}}{Y_{22}} \quad \text{and} \quad L_{23} = \frac{Y_{23}}{Y_{22}}$$

$$K_2 = -0.0367 - j0.031$$

$$L_{21} = -0.3846$$

$$L_{23} = -0.6154$$

$$V_1 = 1.05 \angle 0^\circ \text{ pu} \quad \text{and} \quad V_3^o = 1 \angle 0$$

$$V_2^I = 0.9825 - j0.310$$

$$V_3^1 = \frac{K_3}{(V_3^o)^*} - [L_{31}V_1 + L_{32}V_2^1]$$

$$K_3 = \frac{P_3 - jQ_3}{Y_{33}} \quad \text{and} \quad L_{31} = \frac{Y_{31}}{Y_{33}} \quad \text{and} \quad L_{32} = \frac{Y_{32}}{Y_{33}}$$

$$K_3 = -0.0142 - j0.0164 \quad L_{31} = -0.4690 + 0.0354i \quad L_{32} = -0.5310 - 0.0354i$$

$$V_1 = 1.05 \angle 0^\circ pu \quad \text{and} \quad V_2^1 = 0.9825 - j0.310$$

$$V_3^1 = 1.0011 - j0.0353$$

Start the second iteration

$K_2, K_3, L_{21}, L_{23}, L_{31}, L_{32}$ constants will be the same.

$$V_2^2 = \frac{K_2}{(V_2^1)^*} - [L_{21}V_1 + L_{23}V_3^1] \quad V_2^2 = 0.9816 - j0.0520$$

$$V_3^2 = \frac{K_3}{(V_3^1)^*} - [L_{31}V_1 + L_{32}V_2^2] \quad V_3^2 = 1.0008 - j0.0459$$

Start the third iteration

$K_2, K_3, L_{21}, L_{23}, L_{31}, L_{32}$ constants will be the same.

$$V_2^3 = \frac{K_2}{(V_2^2)^*} - [L_{21} V_1 + L_{23} V_3^2] = 0.9808 - j0.0578$$

$$V_3^3 = \frac{K_3}{(V_3^2)^*} - [L_{31} V_1 + L_{32} V_2^3] = 1.0004 - j0.0488$$

Start the fourth iteration

$K_2, K_3, L_{21}, L_{23}, L_{31}, L_{32}$ constants will be the same.

$$V_2^4 = \frac{K_2}{(V_2^3)^*} - [L_{21} V_1 + L_{23} V_3^3] = 0.9803 - j0.0594$$


$$V_3^4 = \frac{K_3}{(V_3^3)^*} - [L_{31} V_1 + L_{32} V_2^4] = 1.0002 - j0.0497$$

After 7 iterations,

$$V_2^7 = 0.9800 - j0.0600 = 0.98183 \angle -3.5035^\circ \text{ pu}$$

$$V_3^7 = 1.0000 - j0.0500 = 0.00125 \angle -2.8624^\circ \text{ pu}$$

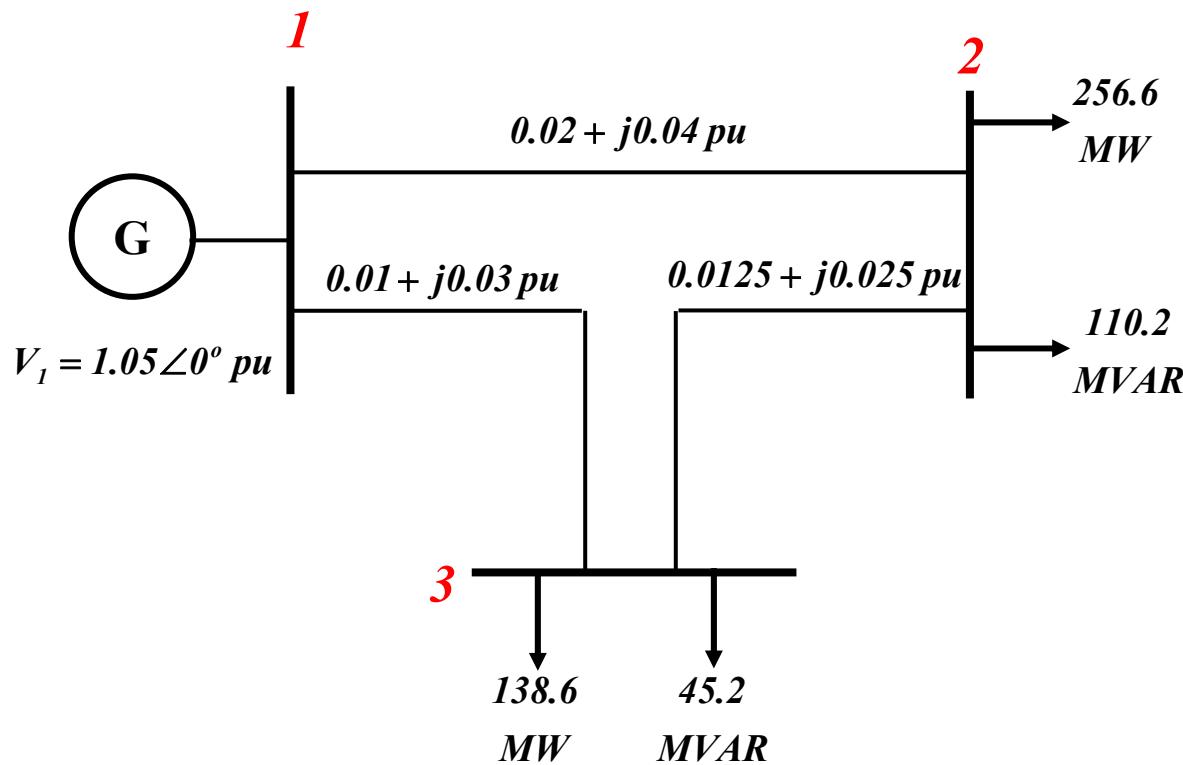B. Using the bus voltages find the Slack bus real and reactive power.



$$V_1 = 1.05 + j0.0^\circ \text{ pu}$$

$$V_2 = 0.9800 - j0.0600 = 0.98183\angle -3.5035^\circ \text{ pu}$$

$$V_3 = 1.0000 - j0.0500 = 0.00125\angle -2.8624^\circ \text{ pu}$$

Using the ***rectangular form*** of the load flow equations,
then the **net** active and reactive powers at ***1th* bus** are:

$$P_i = \text{Re}\{V_1^*(Y_{11} V_1 + Y_{12} V_2 + Y_{13} V_3)\}$$

$$Q_i = -\text{Im}\{V_1^*(Y_{11} V_1 + Y_{12} V_2 + Y_{13} V_3)\}$$

$$P_1 - jQ_1 = V_1^*(Y_{11} V_1 + Y_{12} V_2 + Y_{13} V_3)$$

$$P_i - jQ_i = 4.0938 - j1.8894$$

$$P_1 = 4.0938 \text{ pu}$$

$$Q_1 = 1.8894 \text{ pu}$$


Base MVA=100

$$P_1 = 409.38 \text{ MVA}$$

$$Q_1 = 188.94 \text{ MVA}$$

Reminder
The bus admittance matrix
is

$$\begin{bmatrix} 20 - j50 & -10 + j20 & -10 + j30 \\ -10 + j20 & 26 - j52 & -16 + j32 \\ -10 + j30 & -16 + j32 & 26 - j62 \end{bmatrix}$$

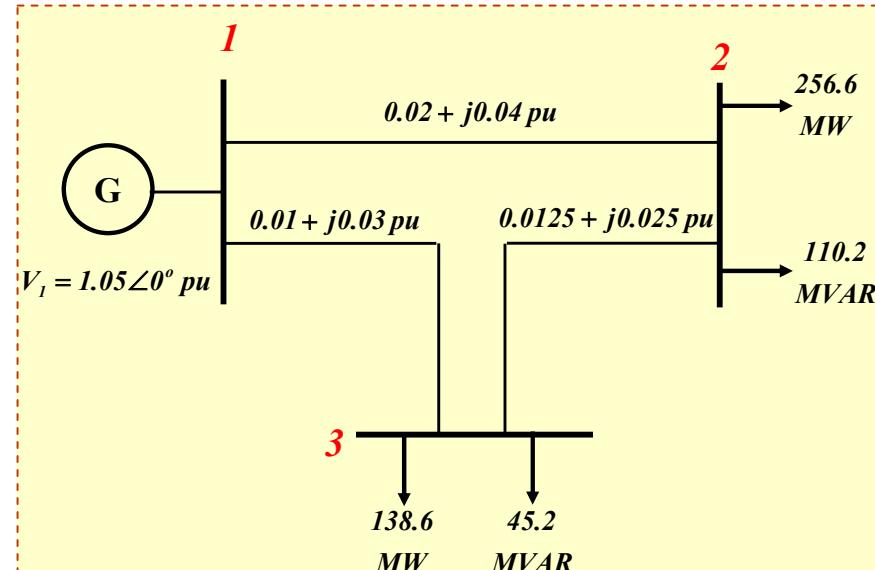


Problem 1:

The line impedances are as indicated in per unit on 100MVA base. Using Gauss-Seidel method:

1. Classify each bus
2. find bus admittance matrix
2. find bus 2 voltage after the first iteration.
3. find bus 1 real and reactive power.

NOTE: select the initial value for bus 2 voltage as:

$$V_2^0 = 1 \angle -22.0169^\circ$$

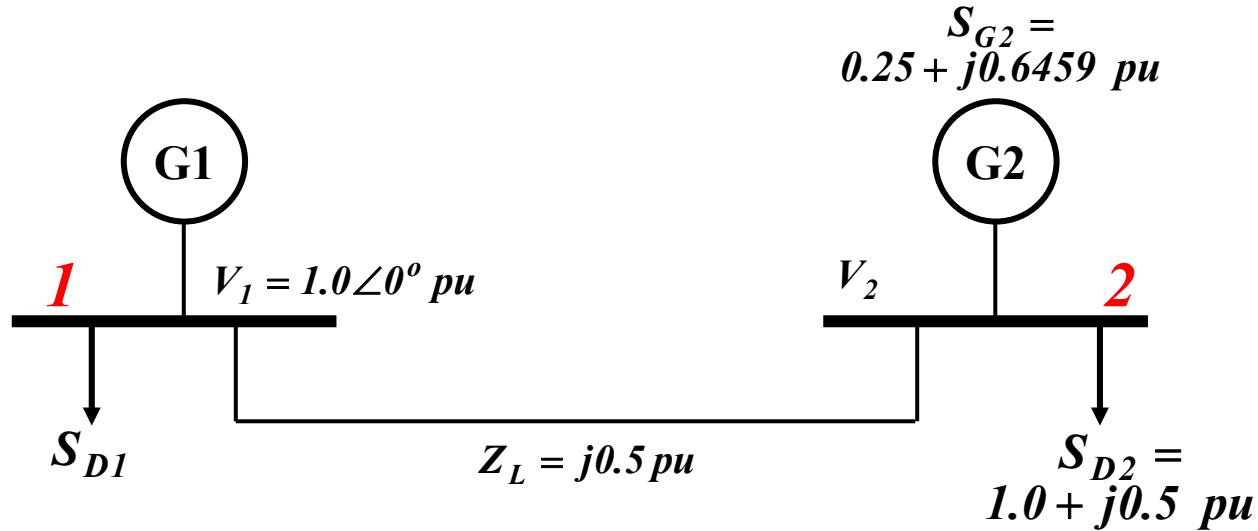

$$Y_{bus} = \begin{bmatrix} -j2.0 & j2.0 \\ j2.0 & -j2.0 \end{bmatrix}$$

$$S_{2,sch} = (P_{2,g} - P_{2,d}) + j(Q_{2,g} - Q_{2,d})$$

$$S_{2,sch} = -0.7500 + j0.1459 \text{ pu}$$

Using GS method, select the initial values for the unknowns as:

$$V_2^o = 1\angle -22.0169^\circ \quad V_1 = 1.0\angle 0^\circ \text{ pu}$$

Start the first iteration

$$V_2^1 = \frac{1}{(V_2^o)^*} \frac{P_{2,sch} - jQ_{2,sch}}{Y_{22}} - \left[\frac{Y_{21}}{Y_{22}} V_1 \right]$$

$$V_2^1 = 1\angle -22.0238^\circ = 0.9271 - j0.3749$$

Power at bus 1

$$P_1 - jQ_1 = V_1^* (Y_{11} V_1 + Y_{12} V_2)$$

$$P_1 + jQ_1 = 0.7500 + j0.1459$$

II. Modifying G-S Method when PV buses are present

Assuming a power system has n buses, then; one bus will be considered as a slack bus and the other buses are load buses (PQ-buses) and voltage controlled buses (PV-buses). Let the system buses be numbered as:

$$i = 1 \quad \text{Slack bus}$$

$$i = 2, 3, \dots, m \quad \text{PV-buses}$$


$$i = m + 1, m + 2, \dots, n \quad \text{PQ-buses}$$

For the voltage controlled buses,

P_i and $|V_i|$ are known & Q_i and δ_i are unknown

$$|V_i| = |V_i|_{\text{Specified}} \quad \dots \text{Eq. 23}$$
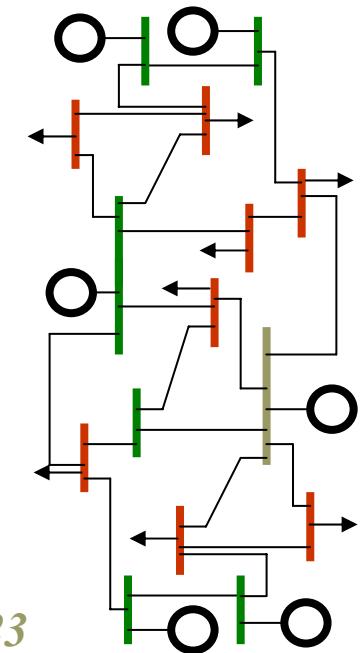
$$Q_{i,\min} < Q_i < Q_{i,\max} \quad \dots \text{Eq. 24}$$



The second requirement for the voltage controlled bus may be violated if the bus voltage becomes too high or too small. It is to be noted that we can control the bus voltage by controlling the bus reactive power.

Therefore, during any iteration, if the PV-bus reactive power violates its limits then set it according to the following rule.

$$Q_{i,min} < Q_i < Q_{i,max}$$

$$Q_i > Q_{i,max} \quad \text{set } Q_i = Q_{i,max}$$

$$Q_i < Q_{i,min} \quad \text{set } Q_i = Q_{i,min}$$

And treat this bus as PQ-bus.

NOTE

For PQ-bus

P_i and Q_i are known

& $|V_i|$ and δ_i are unknown

Load flow solution when PV buses are present

a. Calculate Q_i

In the polar form,

$$Q_i = |V_i| \sum_{p=1}^n |Y_{ip}| |V_p| \sin(\delta_i - \delta_p - \gamma_{ip})$$

For the (k^{th+1}) iteration,

$$Q_i^{(k+1)} = |V_i|_{speci} \sum_{p=1}^{i-1} |Y_{ip}| |V_p^{(k+1)}| \sin(\delta_i^{(k)} - \delta_p^{(k+1)} - \gamma_{ip})$$

$$+ |V_i|_{speci} \sum_{p=i}^n |Y_{ip}| |V_p^{(k)}| \sin(\delta_i^{(k)} - \delta_i^{(k)} - \gamma_{ip})$$

For $p=1$ to $(i-1)$, use $|V_p|$ & δ_p of $(k^{th} + 1)$ iteration

For $p=i$ to n , use $|V_p|$ & δ_p of (k^{th}) iteration

Set $|V_i| = |V_i|_{speci}$

In the rectangular form,

$$P_i - jQ_i = V_i^* (Y_{i1} V_1 + Y_{i2} V_2 + \dots + Y_{ii} V_i + \dots + Y_{in} V_n)$$

$$Q_i = -Im\{V_i^* (Y_{i1} V_1 + Y_{i2} V_2 + \dots + Y_{ii} V_i + \dots + Y_{in} V_n)\}$$

b. Check Q_i^{k+1} to see if it is within the limits

$$Q_{i,min} < Q_i < Q_{i,max}$$

Case 1: If the reactive power limits are not violated,
calculate V_i^{k+1}

$$V_i^{k+1} = \frac{K_i}{(V_i^k)^*} - \sum_{p=1}^{i-1} L_{ip} V_p^{(k+1)} - \sum_{p=i+1}^n L_{ip} V_p^k = |V_i^{k+1}| \angle \delta_i^{k+1}$$

- Use the most updated value of Q_i to calculate K_i .
- New Voltage magnitude and angle are obtained

Use $|V_i|_{speci}$ and δ_i^{k+1} For the **PV-bus voltage**.

Reset the magnitude

$$|V_i^{k+1}| = |V_i|_{Speci}$$

Voltage magnitude is known for PV bus, therefore the new calculated magnitude will not be used.

$$V_i^{k+1} = |V_i|_{Speci}^{\angle \delta_i^{k+1}}$$

Only the calculated angle will be updated and used.

Case 2: If the reactive power limits are violated,

$$Q_i^{k+1} > Q_{i,max} \quad \text{set} \quad Q_i^{k+1} = Q_{i,max}$$

Or

$$Q_i^{k+1} < Q_{i,min} \quad \text{set} \quad Q_i^{k+1} = Q_{i,min}$$

Consider this bus as a **PQ-Bus**, calculate bus voltage V_i^{k+1}


$$V_i^{k+1} = \frac{K_i}{(V_i^k)^*} - \sum_{p=1}^{i-1} L_{ip} V_p^{(k+1)} - \sum_{p=i+1}^n L_{ip} V_p^k$$

$$V_i^{k+1} = |V_i^{k+1}|^{\angle \delta_i^{k+1}}$$

The PV-bus becomes PQ-bus and both Voltage magnitude and angle are calculated and used

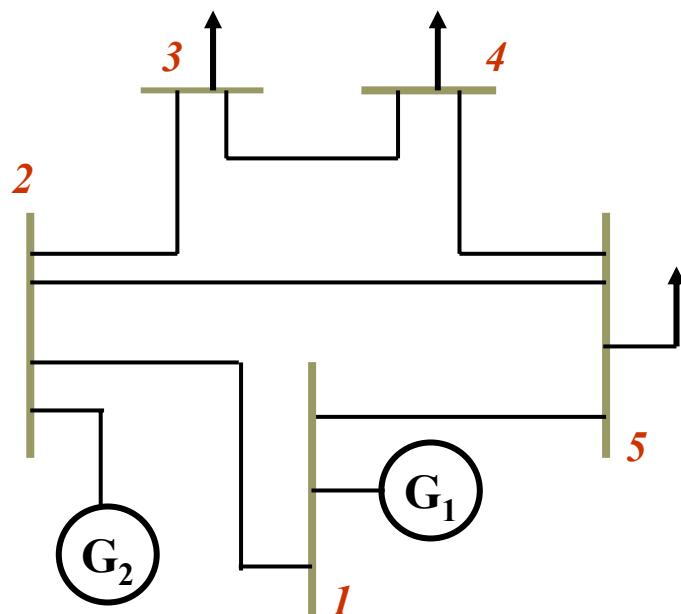EXAMPLE:

Each line has an impedance of $0.05+j0.15$



Line Data for the 5 buses Network

From Bus	To Bus	R	X
1	2	0.0500	0.1500
2	3	0.0500	0.1500
2	4	0.0500	0.1500
3	4	0.0500	0.1500
1	5	0.0500	0.1500
4	5	0.0500	0.1500

The shunt admittance is neglected

Bus Data for the the 5 buses Network Before load flow solution

Bus No.	Bus code	Volt Mag.	Volt Angle	Load MW	Load MVAR	Gen. MW	Gen. MVAR	Q Min.	Q Max.	Inject MVAR
1	Slack	1.0200	0	100	50	?	?	0	0	0
2	PV	1.0200	?	0	0	200	?	20	60	0
3	PQ	?	?	50	20	0	0	0	0	0
4	PQ	?	?	50	20	0	0	0	0	0
5	PQ	?	?	50	20	0	0	0	0	0


For the ‘5’ bus system

Construct the bus admittance matrix Y_{bus}

Find Q_2, δ_2, V_3, V_4 and V_5

$$Q_{max} = 0.6 \text{ pu}$$

$$Q_{min} = 0.2 \text{ pu}$$

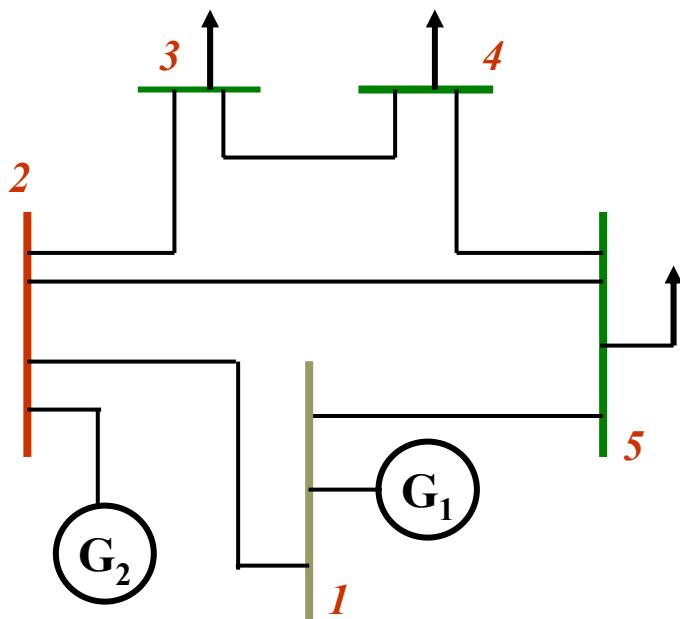

SOLUTION:

Y_{bus} Construction

$$y = \frac{1}{z} = \frac{1}{0.05 + j0.15} = 2 - j6$$


$$Y_{11} = y_{12} + y_{15} = 4 - j12$$

$$Y_{22} = y_{21} + y_{23} + y_{25} = 6 - j18$$

$$Y_{33} = y_{32} + y_{34} = 4 - j12$$

$$Y_{44} = y_{43} + y_{45} = 4 - j12$$
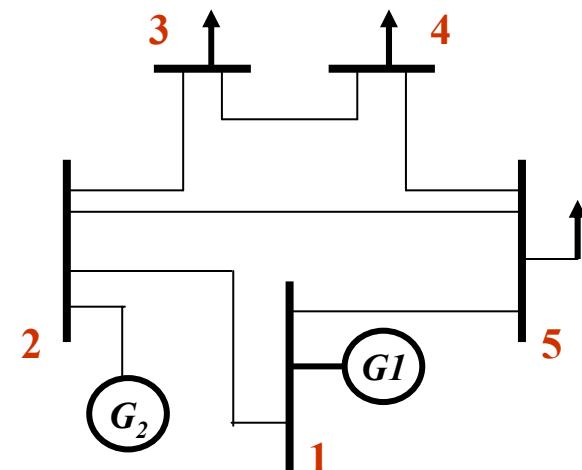
$$Y_{55} = y_{51} + y_{52} + y_{54} = 6 - j18$$




$$Y_{12} = -y_{12} = -2 + j6$$

$$Y_{15} = -y_{15} = -2 + j6$$

$$Y_{13} = Y_{14} = 0$$

$$Y_{bus} = \begin{bmatrix} 4.0 - J12.0 & -2.0 + J6.0 & 0 & 0 & -2.0 + J6.0 \\ -2.0 + J6.0 & 6.0 - J18.0 & -2.0 + J6.0 & 0 & -2.0 + J6.0 \\ 0 & -2.0 + J6.0 & 4.0 - J12.0 & -2.0 + J6.0 & 0 \\ 0 & 0 & -2.0 + J6.0 & 4.0 - J12.0 & -2.0 + J6.0 \\ -2.0 + J6.0 & -2.0 + J6.0 & 0 & -2.0 + J6.0 & 6.0 - J18.0 \end{bmatrix}$$

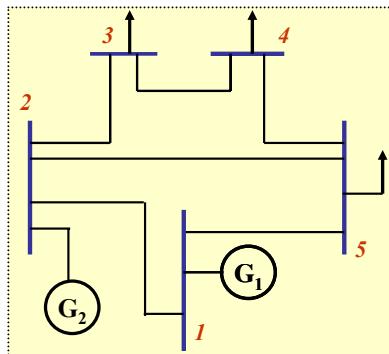The net scheduled power *injected* at each bus is:



Bus No.	Bus code	Volt Mag.	Volt Angle	Load MW	Load MVAR	Gen. MW	Gen. MVAR	Q Min.	Q Max.	Inject MVAR
1	Slack	1.0200	0	100	50	?	?	0	0	0
2	PV	1.0200	?	0	0	200	?	20	60	0
3	PQ	?	?	50	20	0	0	0	0	0
4	PQ	?	?	50	20	0	0	0	0	0
5	PQ	?	?	50	20	0	0	0	0	0

$$S_{1,sch} = (P_{1,g} - P_{1,d}) + j(Q_{1,g} - Q_{1,d})$$

$$S_{1,sch} = (P_{1,g} - 1.0) + j(Q_{1,g} - 0.5)$$

$$S_{2,sch} = (P_{2,g} - P_{2,d}) + j(Q_{2,g} - Q_{2,d})$$

$$S_{2,sch} = (2.0 - 0) + j(0 - 0)$$

$$S_{3,sch} = (0 - 0.5) + j(0 - 0.2)$$

$$S_{3,sch} = -0.5 - j0.2$$

$$S_{4,sch} = -0.5 - j0.2$$

$$S_{5,sch} = -0.5 - j0.2$$

The known values are:

$$V_1 = 1.02 \angle 0^\circ$$

$$|V_2|_{spec} = 1.02$$

The bus admittance matrix is

$$\begin{bmatrix} 4.0 - J12.0 & -2.0 + J6.0 & 0 & 0 & -2.0 + J6.0 \\ -2.0 + J6.0 & 6.0 - J18.0 & -2.0 + J6.0 & 0 & -2.0 + J6.0 \\ 0 & -2.0 + J6.0 & 4.0 - J12.0 & -2.0 + J6.0 & 0 \\ 0 & 0 & -2.0 + J6.0 & 4.0 - J12.0 & -2.0 + J6.0 \\ -2.0 + J6.0 & -2.0 + J6.0 & 0 & -2.0 + J6.0 & 6.0 - J18.0 \end{bmatrix}$$

$$Q_{2,min} = 0.2$$

and

$$Q_{2,max} = 0.6$$

Using GS method, *select the initial values for the unknowns* as:

$$V_3^o = V_4^o = V_5^o = 1 \angle 0^\circ \quad \text{and} \quad \delta_2^o = 0$$

Start the first iteration

Bus 2 is PV Bus

Check Q_2 is within the limits $Q_{2,min} < Q_2 < Q_{2,max}$

$$P_i - jQ_i = V_i^* (Y_{i1} V_1 + Y_{i2} V_2 + \dots + Y_{ii} V_i + \dots + Y_{in} V_n)$$

$$Q_2^I = -Im\{V_2^* (Y_{21} V_1 + Y_{22} V_2^o + Y_{23} V_3^o + Y_{24} V_4^o + Y_{25} V_5^o)\}$$

$$Q_2^I = 0.2448$$

$$Q_{2,min} < Q_2 < Q_{2,max} \quad \text{i.e.}; \quad 0.20 < 0.2448 < 0.6$$

The reactive power limits are not violated,

Calculate:

$$V_2^I = \frac{K_2}{(V_2^o)^*} - [L_{21}V_1 + L_{23}V_3^o + L_{24}V_4^o + L_{25}V_5^o]$$

The values for K_i and L_{ip} are computed once in the beginning and used in every iteration.

$$K_2 = \frac{P_2 - jQ_2}{Y_{22}} \quad L_{21} = \frac{Y_{21}}{Y_{22}} \quad L_{23} = \frac{Y_{23}}{Y_{22}} \quad L_{24} = \frac{Y_{24}}{Y_{22}} \quad L_{25} = \frac{Y_{25}}{Y_{22}}$$

$$S_{2,sch} = 2.0 + j0.2448$$

$$K_2 = 0.0456 + j0.0959 \quad L_{21} = -0.3333 \quad L_{23} = -0.3333 \quad L_{24} = 0.0 \quad L_{25} = -0.3333$$

$$V_2^I = 1.0555 \angle 5.1113^\circ$$

Reset the magnitude

$$|V_2^I| = |V_2|_{Speci} = 1.02$$

Therefore,

$$\delta_2^I = 5.1113^\circ$$

$$V_2^I = 1.02 \angle 5.1113^\circ$$

Voltage magnitude is known and fixed for a PV bus, therefore the new calculated magnitude will not be used.

Bus 3 is PQ Bus

$$V_3^1 = \frac{K_3}{(V_3^o)^*} - [L_{31}V_1 + L_{32}V_2^1 + L_{34}V_4^o + L_{35}V_5^o]$$

$$K_3 = \frac{P_3 - jQ_3}{Y_{33}} \quad L_{31} = \frac{Y_{31}}{Y_{33}} \quad L_{32} = \frac{Y_{32}}{Y_{33}} \quad L_{34} = \frac{Y_{34}}{Y_{33}} \quad L_{35} = \frac{Y_{35}}{Y_{33}}$$

$$K_3 = -0.0275 - j0.0325 \quad L_{31} = 0.0 \quad L_{32} = -0.5000 \quad L_{34} = -0.5000 \quad L_{35} = 0.0$$

$$V_3^1 = 0.9806 \angle 0.7559^\circ$$

Bus 4 is PQ Bus

$$V_4^1 = \frac{K_4}{(V_4^o)^*} - [L_{41}V_1 + L_{42}V_2^1 + L_{43}V_3^1 + L_{45}V_5^o]$$

$$K_4 = \frac{P_4 - jQ_4}{Y_{44}} \quad L_{41} = \frac{Y_{41}}{Y_{44}} \quad L_{42} = \frac{Y_{42}}{Y_{44}} \quad L_{43} = \frac{Y_{43}}{Y_{44}} \quad L_{45} = \frac{Y_{45}}{Y_{44}}$$

$$K_4 = -0.0275 - j0.0325 \quad L_{41} = 0.0 \quad L_{42} = 0.0 \quad L_{43} = -0.5000 \quad L_{45} = -0.5000$$

$$V_4^1 = 0.9631 \angle -1.5489^\circ$$

Bus 5 is PQ Bus

$$V_5^1 = \frac{K_5}{(V_5^o)^*} - [L_{51}V_1 + L_{52}V_2^1 + L_{53}V_3^3 + L_{54}V_4^1]$$

$$K_5 = -0.0183 - 0.0217i \quad L_{51} = -0.3333 \quad L_{52} = -0.3333 \quad L_{53} = 0.0 \quad L_{54} = -0.3333$$

$$V_5^1 = 0.9812 \angle -0.0031^\circ$$

Start the second iteration

Bus 2 is PV Bus

Check Q_2 is within the limits $0.2 < Q_2 < 0.6$

$$Q_2^2 = -\text{Im}\{V_2^{1*}(Y_{21}V_1 + Y_{22}V_2^1 + Y_{23}V_3^1 + Y_{24}V_4^1 + Y_{25}V_5^1)\}$$

$$Q_2^2 = 0.0290$$

The reactive power limits are violated

$$Q_2 < Q_{i,min} \quad \text{set} \quad Q_2 = Q_{i,min} = 0.2$$

And treat this bus as PQ-bus


$$S_{2,sch} = 2.0 + j0.2$$

Use the most updated value of Q_2 to calculate the constant K_2

All Buses 2, 3, 4 and 5 are PQ Buses. Find the bus voltages using GS method

Problem 2:

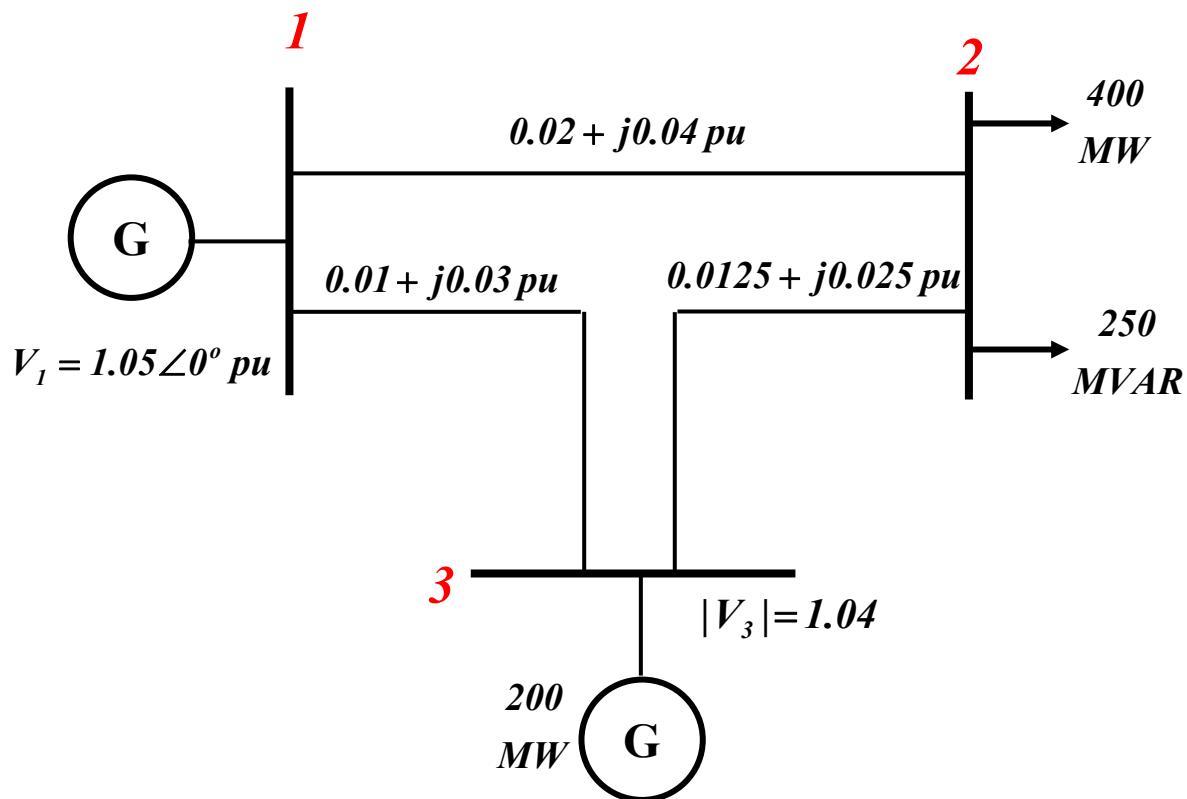
A. The line impedances are as indicated in per unit on 100MVA base. The line charging susceptances are neglected. Using Gauss-Seidel method find the power flow solution of the system. Ignoring the limits of Q_3 .



$$y_{12} = \frac{1}{0.02 + j0.04} = 10 - j20 = y_{21}$$

$$y_{13} = \frac{1}{0.01 + j0.03} = 10 - j30 = y_{31}$$
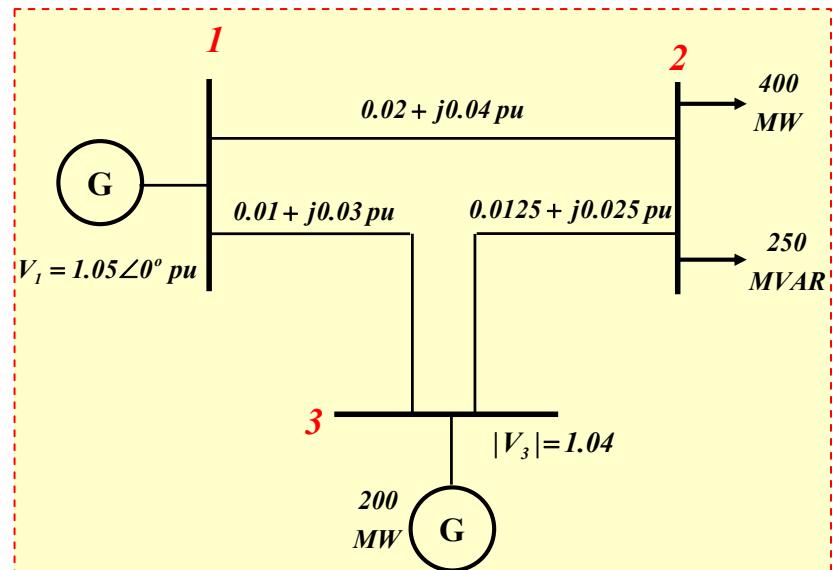
$$y_{23} = \frac{1}{0.0125 + j0.025} = 16 - j32 = y_{32}$$



$$Y_{bus} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} = \begin{bmatrix} y_{12} + y_{13} & -y_{12} & -y_{13} \\ -y_{21} & y_{21} + y_{23} & -y_{23} \\ -y_{31} & -y_{32} & y_{31} + y_{32} \end{bmatrix}$$


$$Y_{bus} = \begin{bmatrix} 20 - j50 & -10 + j20 & -10 + j30 \\ -10 + j20 & 26 - j52 & -16 + j32 \\ -10 + j30 & -16 + j32 & 26 - j62 \end{bmatrix}$$

Classification of buses:

Bus 1: Slack Bus

$$V_1 = 1.05 \angle 0^\circ \text{ pu}$$

Bus 2: Load Bus (*PQ bus*)

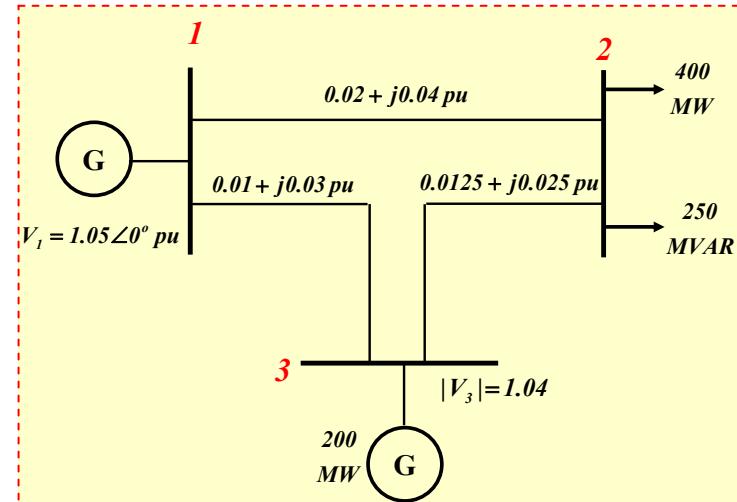

P_2 and Q_2 are known

V_2 and δ_2 are unknown

$$S_{2,sch} = \frac{(P_{2,g} - P_{2,d}) + j(Q_{2,g} - Q_{2,d})}{\text{Base MVA}} \text{ pu}$$

$$S_{2,sch} = \frac{(0 - 400) + j(0 - 250)}{100} \text{ pu}$$

$$S_{2,sch} = -4 - j2.5 \text{ pu}$$

Bus 3: Voltage Controlled Bus (*PV bus*)

$|V_3|$ and $P_{g,3}$ are known

$Q_{3,sch}$ and δ_3 are unknown

$$P_{3,sch} = 2.0 \text{ pu}$$

Using GS method, select the initial values for the unknowns as:

$$V_1 = 1.05 \angle 0^\circ \text{ pu} \quad V_2^o = 1 \angle 0^\circ \quad |V_3| = 1.04 \quad \delta_3^o = 0^\circ$$

Start the first iteration

Bus 2 is PQ Bus

$$V_2 = \frac{K_2}{V_2^*} - \sum_{\substack{p=1 \\ p \neq 2}}^n L_{2p} V_p$$

$$V_2^I = \frac{K_2}{(V_2^*)^*} - [L_{21} V_1 + L_{23} V_3^o]$$

$$K2 = -0.0692 - j0.0423 \quad L21 = -0.3846 \quad L23 = -0.6154$$

$$V_2^I = 0.9746 - j0.0423$$

Bus 3 is PV Bus

Calculate and Check Q_3 is within the limits $Q_{3,min} < Q_3 < Q_{3,max}$

$$Q_3^I = -\operatorname{Im}\{V_3^*(Y_{31} V_1 + Y_{32} V_2^I + Y_{33} V_3^o)\}$$

$$Q_3^I = j1.1600$$

$$V_3^I = \frac{K_3}{(V_3^o)^*} - [L_{31} V_1 + L_{32} V_2^I]$$

$$K3 = 0.0274 + j0.0208 \quad L31 = -0.4690 + j0.0354 \quad L32 = -0.5310 - j0.0354$$

$$V_3^I = 1.0378 - j0.0052 = 1.0378 \angle -0.2854^\circ$$

Reset the magnitude

$$|V_3^I| = |V_i|_{Speci} = 1.04$$

$$V_3^I = 1.04 \angle -0.2854^\circ$$

$$V_3^I = 1.0400 - j0.0052$$

Voltage magnitude is fixed for a PV bus, therefore the new calculated magnitude will not be used.

Start the second iteration

K_2, L_{21}, L_{23} are constants and will be the same.

Bus 2 is PQ Bus

$$V_2^2 = \frac{K_2}{(V_2^1)^*} - [L_{21} V_1 + L_{23} V_3^1]$$

$$V_2^2 = 0.9711 - j0.0434$$

Bus 3 is PV Bus

Calculate and check Q_3 is within the limits $Q_{3,min} < Q_3 < Q_{3,max}$

$$Q_3^2 = -Im\{V_3^*(Y_{31} V_1 + Y_{32} V_2^2 + Y_{33} V_3^1)\}$$

$$Q_3^2 = j1.3881$$

$$V_3^2 = \frac{K_3}{(V_3^1)^*} - [L_{31} V_1 + L_{32} V_2^2]$$

L_{31} and L_{32} are constants and will be the same.
 K_3 is changed as Q_3 change

$$K_3 = \frac{P_3 - jQ_3^2}{Y_{33}}$$

$$K3 = 0.0305 + j0.0194$$


$$V_3^2 = 1.0391 - j0.0073 = 1.0391 \angle -0.4028^\circ$$

Reset the magnitude

$$V_3^2 = 1.04 \angle -0.4028^\circ = 1.0400 - j0.0073$$

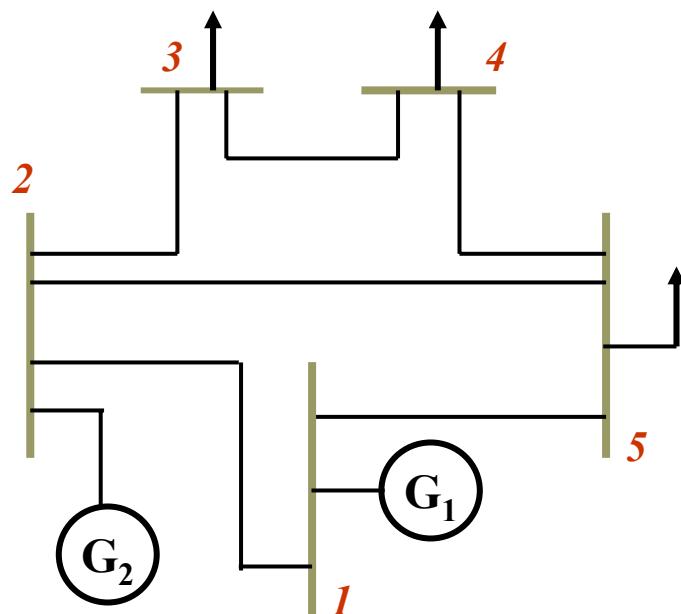EXAMPLE:

Each line has an impedance of $0.05+j0.15$



Line Data for the 5 buses Network

From Bus	To Bus	R	X
1	2	0.0500	0.1500
2	3	0.0500	0.1500
2	4	0.0500	0.1500
3	4	0.0500	0.1500
1	5	0.0500	0.1500
4	5	0.0500	0.1500

The shunt admittance is neglected

Bus Data for the the 5 buses Network Before load flow solution

Bus No.	Bus code	Volt Mag.	Volt Angle	Load MW	Load MVAR	Gen. MW	Gen. MVAR	Q Min.	Q Max.	Inject MVAR
1	Slack	1.0200	0	100	50	?	?	0	0	0
2	PV	1.0200	?	0	0	200	?	20	60	0
3	PQ	?	?	50	20	0	0	0	0	0
4	PQ	?	?	50	20	0	0	0	0	0
5	PQ	?	?	50	20	0	0	0	0	0

For the ‘5’ bus system

Construct the bus admittance matrix Y_{bus}

Find Q_2, δ_2, V_3, V_4 and V_5

$$Q_{max} = 0.6 \text{ pu}$$

$$Q_{min} = 0.2 \text{ pu}$$

SOLUTION:

Y_{bus} Construction

$$y = \frac{1}{z} = \frac{1}{0.05 + j0.15} = 2 - j6$$


$$Y_{11} = y_{12} + y_{15} = 4 - j12$$

$$Y_{22} = y_{21} + y_{23} + y_{25} = 6 - j18$$

$$Y_{33} = y_{32} + y_{34} = 4 - j12$$

$$Y_{44} = y_{43} + y_{45} = 4 - j12$$
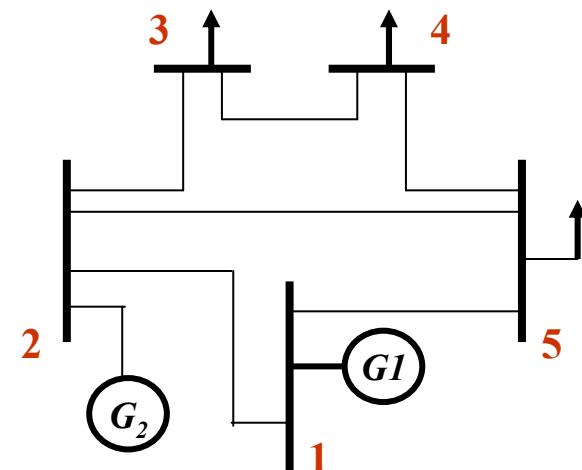
$$Y_{55} = y_{51} + y_{52} + y_{54} = 6 - j18$$




$$Y_{12} = -y_{12} = -2 + j6$$

$$Y_{15} = -y_{15} = -2 + j6$$

$$Y_{13} = Y_{14} = 0$$

$$Y_{bus} = \begin{bmatrix} 4.0 - J12.0 & -2.0 + J6.0 & 0 & 0 & -2.0 + J6.0 \\ -2.0 + J6.0 & 6.0 - J18.0 & -2.0 + J6.0 & 0 & -2.0 + J6.0 \\ 0 & -2.0 + J6.0 & 4.0 - J12.0 & -2.0 + J6.0 & 0 \\ 0 & 0 & -2.0 + J6.0 & 4.0 - J12.0 & -2.0 + J6.0 \\ -2.0 + J6.0 & -2.0 + J6.0 & 0 & -2.0 + J6.0 & 6.0 - J18.0 \end{bmatrix}$$

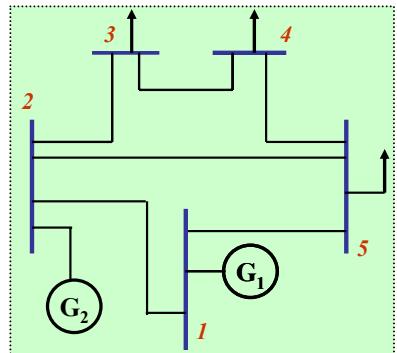The net scheduled power *injected* at each bus is:



Bus No.	Bus code	Volt Mag.	Volt Angle	Load MW	Load MVAR	Gen. MW	Gen. MVAR	Q Min.	Q Max.	Inject MVAR
1	Slack	1.0200	0	100	50	?	?	0	0	0
2	PV	1.0200	?	0	0	200	?	20	60	0
3	PQ	?	?	50	20	0	0	0	0	0
4	PQ	?	?	50	20	0	0	0	0	0
5	PQ	?	?	50	20	0	0	0	0	0

The known values are:

The bus admittance matrix is

$$\begin{bmatrix} 4.0 - J12.0 & -2.0 + J6.0 & 0 & 0 & -2.0 + J6.0 \\ -2.0 + J6.0 & 6.0 - J18.0 & -2.0 + J6.0 & 0 & -2.0 + J6.0 \\ 0 & -2.0 + J6.0 & 4.0 - J12.0 & -2.0 + J6.0 & 0 \\ 0 & 0 & -2.0 + J6.0 & 4.0 - J12.0 & -2.0 + J6.0 \\ -2.0 + J6.0 & -2.0 + J6.0 & 0 & -2.0 + J6.0 & 6.0 - J18.0 \end{bmatrix}$$

Using GS method, *select the initial values for the unknowns* as:

Start the first iteration

Bus 2 is PV Bus

Check Q_2 is within the limits $Q_{2,min} < Q_2 < Q_{2,max}$

$$P_i - jQ_i = V_i^* (Y_{i1} V_1 + Y_{i2} V_2 + \dots + Y_{ii} V_i + \dots + Y_{in} V_n)$$

$$Q_2^I = -\operatorname{Im}\{V_2^* (Y_{21} V_1 + Y_{22} V_2^o + Y_{23} V_3^o + Y_{24} V_4^o + Y_{25} V_5^o)\}$$

$$Q_2^I =$$

$$Q_{2,min} < Q_2 < Q_{2,max} \quad i.e.; \quad 0.20 < 0.448 < 0.6$$

The reactive power limits are not violated,

Calculate:

$$V_2^I = \frac{K_2}{(V_2^o)^*} - [L_{21}V_1 + L_{23}V_3^o + L_{24}V_4^o + L_{25}V_5^o]$$

The values for K_i and L_{ip} are computed once in the beginning and used in every iteration.

$$K_2 = \frac{P_2 - jQ_2}{Y_{22}} \quad L_{21} = \frac{Y_{21}}{Y_{22}} \quad L_{23} = \frac{Y_{23}}{Y_{22}} \quad L_{24} = \frac{Y_{24}}{Y_{22}} \quad L_{25} = \frac{Y_{25}}{Y_{22}}$$

$$K_2 = 0.0456 + j0.0959 \quad L_{21} = -0.3333 \quad L_{23} = -0.3333 \quad L_{24} = 0.0 \quad L_{25} = -0.3333$$

$$V_2^I =]$$

Reset the magnitude

$$|V_2^I| =$$

$$\delta_2^I =$$

Therefore,

$$V_2^I =]$$

Voltage magnitude is known and fixed for a PV bus, therefore the new calculated magnitude will not be used.

Bus 3 is PQ Bus

$$V_3^1 = \frac{K_3}{(V_3^o)^*} - [L_{31}V_1 + L_{32}V_2^1 + L_{34}V_4^o + L_{35}V_5^o]$$

$$K_3 = \frac{P_3 - jQ_3}{Y_{33}} \quad L_{31} = \frac{Y_{31}}{Y_{33}} \quad L_{32} = \frac{Y_{32}}{Y_{33}} \quad L_{34} = \frac{Y_{34}}{Y_{33}} \quad L_{35} = \frac{Y_{35}}{Y_{33}}$$

$$K_3 = -0.0275 - j0.0325 \quad L_{31} = 0.0 \quad L_{32} = -0.5000 \quad L_{34} = -0.5000 \quad L_{35} = 0.0$$

$$V_3^1 = 0.9806 \angle 0.7559^\circ$$

Bus 4 is PQ Bus

$$V_4^1 = \frac{K_4}{(V_4^o)^*} - [L_{41}V_1 + L_{42}V_2^1 + L_{43}V_3^1 + L_{45}V_5^o]$$

$$K_4 = \frac{P_4 - jQ_4}{Y_{44}} \quad L_{41} = \frac{Y_{41}}{Y_{44}} \quad L_{42} = \frac{Y_{42}}{Y_{44}} \quad L_{43} = \frac{Y_{43}}{Y_{44}} \quad L_{45} = \frac{Y_{45}}{Y_{44}}$$

$$K_4 = -0.0275 - j0.0325 \quad L_{41} = 0.0 \quad L_{42} = 0.0 \quad L_{43} = -0.5000 \quad L_{45} = -0.5000$$

$$V_4^1 = 0.9631 \angle -1.5489^\circ$$

Bus 5 is PQ Bus

$$V_5^1 = \frac{K_5}{(V_5^o)^*} - [L_{51}V_1 + L_{52}V_2^1 + L_{53}V_3^3 + L_{54}V_4^1]$$

$$K_5 = -0.0183 - 0.0217i \quad L_{51} = -0.3333 \quad L_{52} = -0.3333 \quad L_{53} = 0.0 \quad L_{54} = -0.3333$$


$$V_5^1 = 0.9812 \angle -0.0031^\circ$$

Start the second iteration

Bus 2 is PV Bus

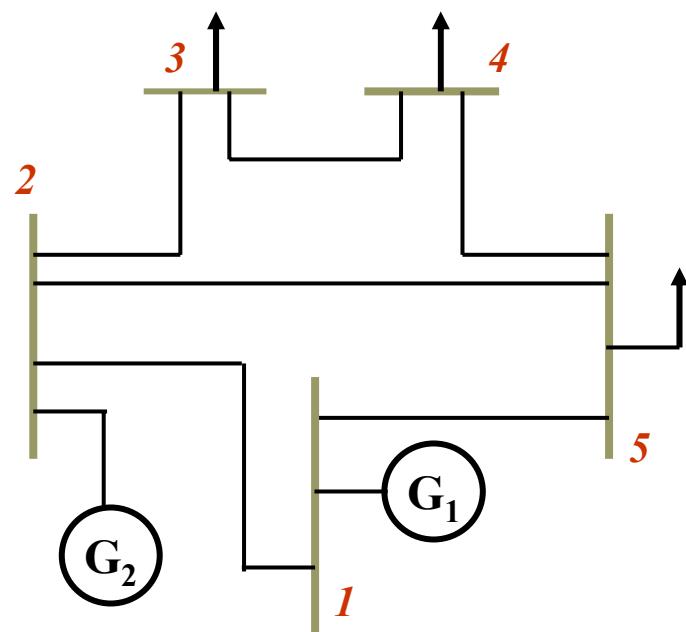EXAMPLE:

Each line has an impedance of $0.05+j0.15$



Line Data for the 5 buses Network

Bus nl	Bus nr	R	X
1	2	0.0500	0.1500
2	3	0.0500	0.1500
2	4	0.0500	0.1500
3	4	0.0500	0.1500
1	5	0.0500	0.1500
4	5	0.0500	0.1500

The shunt admittance is neglected

Bus Data for the the 5 buses Network Before load flow solution

Bus No.	Bus code	Volt Mag.	Volt Angle	Load MW	Load MVAR	Gen. MW	Gen. MVAR	Q Min.	Q Max.	Inject MVAR
1	Slack	1.0200	0	100	50	?	?	0	0	0
2	PV	1.0200	?	0	0	200	?	20	60	0
3	PQ	?	?	50	20	0	0	0	0	0
4	PQ	?	?	50	20	0	0	0	0	0
5	PQ	?	?	50	20	0	0	0	0	0

For the ‘5’ bus system

Construct the bus admittance matrix Y_{bus}

Find Q_2, δ_2, V_3, V_4 and V_5


$$Q_{max} = 0.6 \text{ pu}$$

$$Q_{min} = 0.2 \text{ pu}$$

SOLUTION:

Solution

Y_{bus} Construction

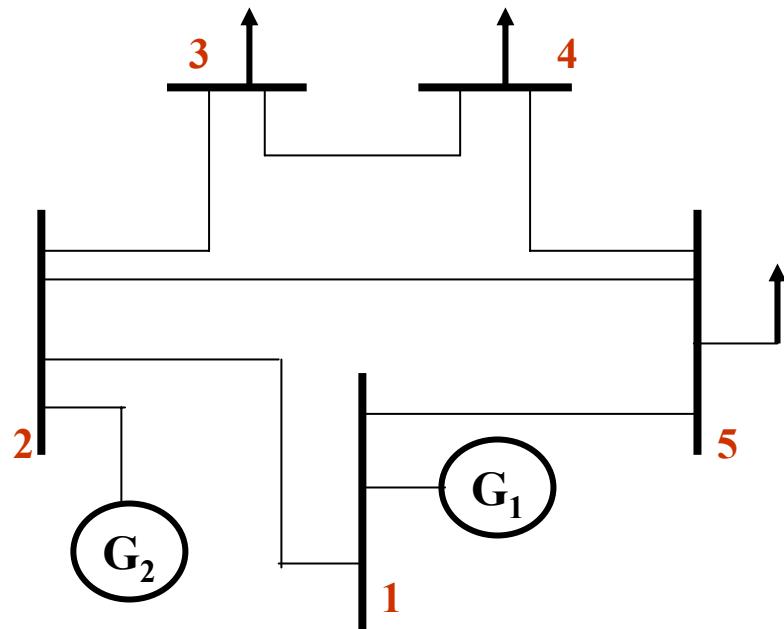

Bus nl	Bus nr	R	X
1	2	0.0500	0.1500
2	3	0.0500	0.1500
2	4	0.0500	0.1500
3	4	0.0500	0.1500
1	5	0.0500	0.1500
4	5	0.0500	0.1500

for each line $y = \frac{1}{z}$

$$y = \frac{1}{z} = \frac{1}{0.05 + j0.15}$$

$$y = (2 - j6)$$


$$Y_{11} = Y_{12} + Y_{15} = 4 - j12$$

$$Y_{12} = -Y_{12} = -2 + j6$$

$$Y_{15} = -Y_{15} = -2 + j6$$

$$Y_{13} = Y_{14} = 0$$

Solution

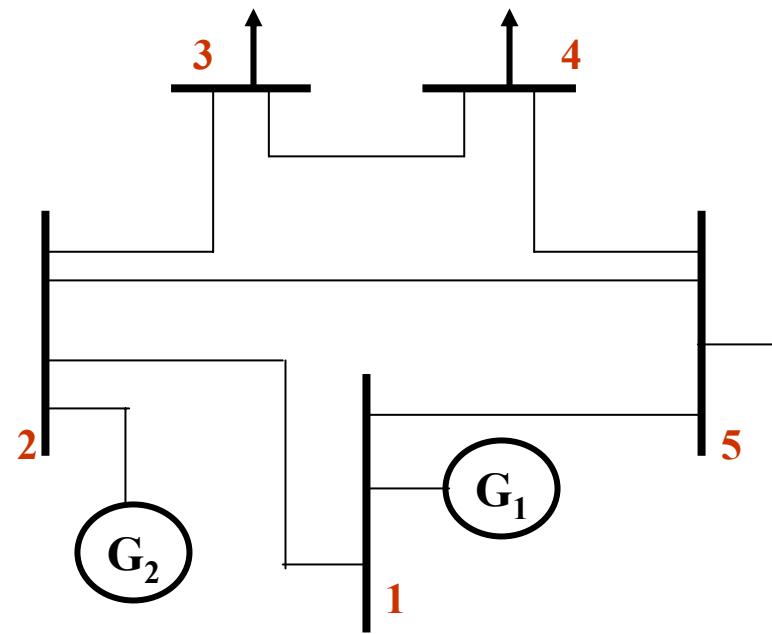

$$Y_{bus} = \begin{bmatrix} 4-j12 & -2+j6 & 0 & 0 & -2+j6 \\ -2+j6 & 6-j18 & -2+j6 & 0 & -2+j6 \\ 0 & -2+j6 & 4-j12 & -2+j6 & 0 \\ 0 & 0 & -2+j6 & 4-j12 & -2+j6 \\ -2+j6 & 0 & -2+j6 & -2+j6 & 6-j18 \end{bmatrix}$$

6. The power injected into the network by each bus is $S_i = P_i + j Q_i$

$$S_2 = P_2 + j Q_2 = 2 + j Q_2$$

$$\begin{aligned} S_3 &= P_3 + j Q_3 = (0 - 0.5) + j (0 - 0.2) \\ &= -0.5 - j 0.2 \end{aligned}$$

$$\begin{aligned} S_4 &= P_4 + j Q_4 = 0 - 0.5 + j (0 - 0.2) \\ &= -0.5 - j 0.2 \end{aligned}$$

$$S_5 = P_5 + j Q_5 = -0.5 - j 0.2$$

Assume $V_3^\circ = V_4^\circ = V_5^\circ = 1.0 \angle 0$

assume $S_2^\circ = 0$
 $|V_2|_{\text{spec}} = 1.02$

$$V_1 = 1.02 \angle 0$$

$$Y_{21} = Y_{23} = Y_{25} = -2 + j 6 = 6.3245 \angle 108.43^\circ$$

$$Y_{22} = 6 - j 18 = 18.97366 \angle -71.57^\circ$$

$$Q_i = |V_i| \sum_{p=1}^n |Y_{ip}| |V_p| \sin(\delta_i - \gamma_{ip} - \delta_p)$$

FOR bus 2:

$$Q'_2 = |V_2|_{\text{speci}} \left[|Y_{21}| |V_1| \sin(\delta_2^\circ - \gamma_{21} - \delta_1^\circ) \right.$$

$$\left. + |Y_{22}| |V_2| \sin(\delta_2^\circ - \gamma_{22} - \delta_2^\circ) \right]$$

$$\left. + |Y_{23}| |V_3| \sin(\delta_2^\circ - \gamma_{23} - \delta_3^\circ) \right]$$

$$\left. + |Y_{24}| |V_4| \sin(\delta_2^\circ - \gamma_{24} - \delta_4^\circ) \right]$$

$$\left. + |Y_{25}| |V_5| \sin(\delta_2^\circ - \gamma_{25} - \delta_5^\circ) \right]$$

$$Q_2' = 1.02 \left[(6.3245)(1.02) \sin(0 - 108.43 - 0) + (18.97366)(1.02) \sin(0 - (-71.57) - 0) + (6.3245)(1.0) \sin(0 - 108.43 - 0) + \text{zero} + (6.3245)(1.0) \sin(0 - 108.43 - 0) \right]$$

$$Q_2' = 0.2448 \text{ pu}$$

The value of Q_2' is within the limits imposed by $Q_{2,\min}$ and $Q_{2,\max}$.

Using Q_2' , find χ_2' ,

$$V_i^{(k+1)} = \frac{K_i}{(V_i^k)^*} - \sum_{p=1}^{i-1} L_{ip} V_p^{(k+1)} - \sum_{p=i+1}^n L_{ip} V_p^k$$

$i=2$, $k=0$ and $n=5$

$$V_2' = \frac{K_2}{(V_2^0)^*} - L_{21} V_1' - [L_{23} V_3^0 + L_{24} V_4^0 + L_{25} V_5^0]$$

$$K_2 = \frac{P_2 - jQ_2'}{Y_{22}} \quad \text{and} \quad L_{ip} = \frac{Y_{ip}}{Y_{ii}}$$

$$V_2' = \frac{1}{Y_{22}} \left[\frac{P_2 - jQ_2'}{Y_{22}} - Y_{21} V_1 - Y_{23} V_3^0 - Y_{25} V_5^0 \right]$$

$$V_2' = \frac{1}{6-j18} \left[\frac{2 - j0.2448}{1.02 - j0} - (-2+j6)(1.02 \angle 0^\circ) - (-2+j6)(1 \angle 0^\circ) - (2+j6) 1 \angle 0^\circ \right]$$

$$V_2' = \frac{8-j18.36}{6-j18} = 1.0555 \angle 5.11^\circ$$

Therefore, $\delta_2' = 5.11^\circ$

Set $|V_2'| = |V_2|_{\text{spec}}$ and retain

the phase shift angle δ_2'

$$\therefore V_2' = 1.02 \angle 5.11^\circ$$

$$V_3' = \frac{1}{Y_{33}} \left[\frac{P_3 - jQ_3}{(V_3^o)^*} - Y_{32} V_2' - Y_{34} V_4^o \right]$$

$$= \frac{1}{4-j12} \left[\frac{-0.5+j0.2}{1 \angle 0} - (-2+j6)(1.02 \angle 5.11^\circ) - (-2+j6) \angle 90^\circ \right]$$

$$V_4' = \frac{1}{Y_{44}} \left[\frac{P_4 - jQ_4}{(V_4^\circ)^*} - Y_{43} V_3' - Y_{45} V_5^\circ \right]$$

$$= 0.963 \angle -1.53^\circ \quad |V_4'| = 0.963 \text{ and } \delta_4' = -1.53^\circ$$

$$V_5' = \frac{1}{Y_{55}} \left[\frac{P_5 - jQ_5}{(V_5^\circ)^*} - Y_{51} V_1 - Y_{52} V_2' - Y_{54} V_4' \right]$$

$$V_5' = 0.9836 \angle -0.04^\circ \quad |V_5'| = 0.9836 \text{ and } \delta_5' = -0.04^\circ$$