

(1)


power-angle characteristic of a synchronous M/C:-

The maximum power that a synch M/C can deliver is determined by the maximum torque that can be applied without losing synchronism.

The expression of the power supplied will be expressed in terms of ~~with~~ the machine parameters and the the system that is connected to it (infinite bus).
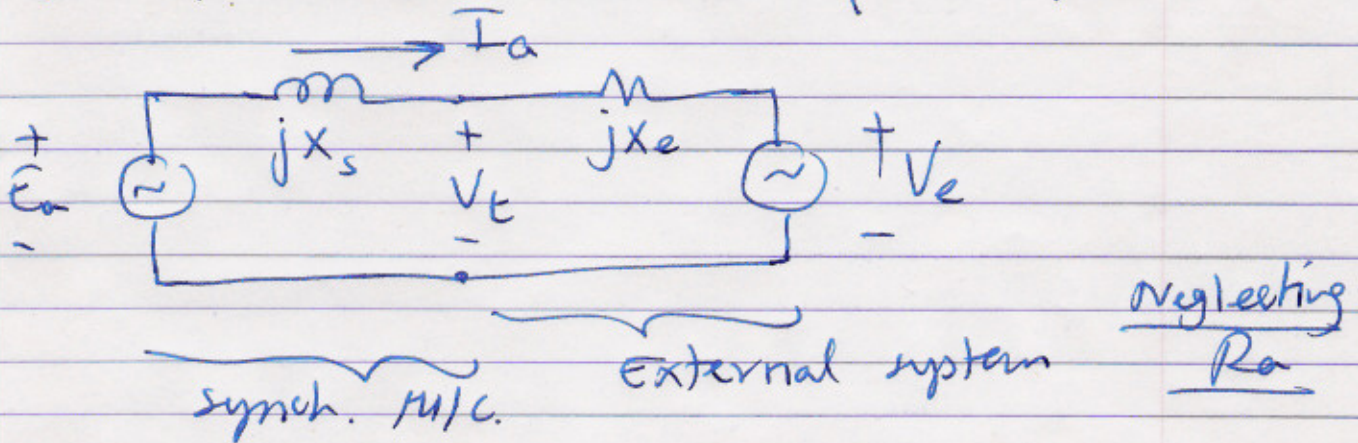
### I) Round-Rotor Machine:

consider the following per-phase equivalent circuit connected to an infinite bus.



take  $V_t$  as a reference phasor.

$$\vec{V}_t = V_t \angle 0^\circ, \quad \vec{E}_a = E_a \angle \delta$$

$\delta$  - power-angle or torque angle.

$$\therefore I_a = \frac{\vec{E}_a - \vec{V}_t}{jX_s}$$

& the complex power

$$\vec{S} = P + jQ = 3 \vec{V}_t \vec{I}_a^*$$




$$P + jQ = 3 V_t \angle 0^\circ \left( \frac{E_a \angle -\delta - V_t \angle 0^\circ}{-jX_s} \right)$$

$$= 3 \left( \frac{E_a V_t}{X_s} \angle -\delta + 90^\circ - j \frac{V_t^2}{X_s} \right)$$

$$P = 3 \frac{E_a V_t}{X_s} \sin \delta$$
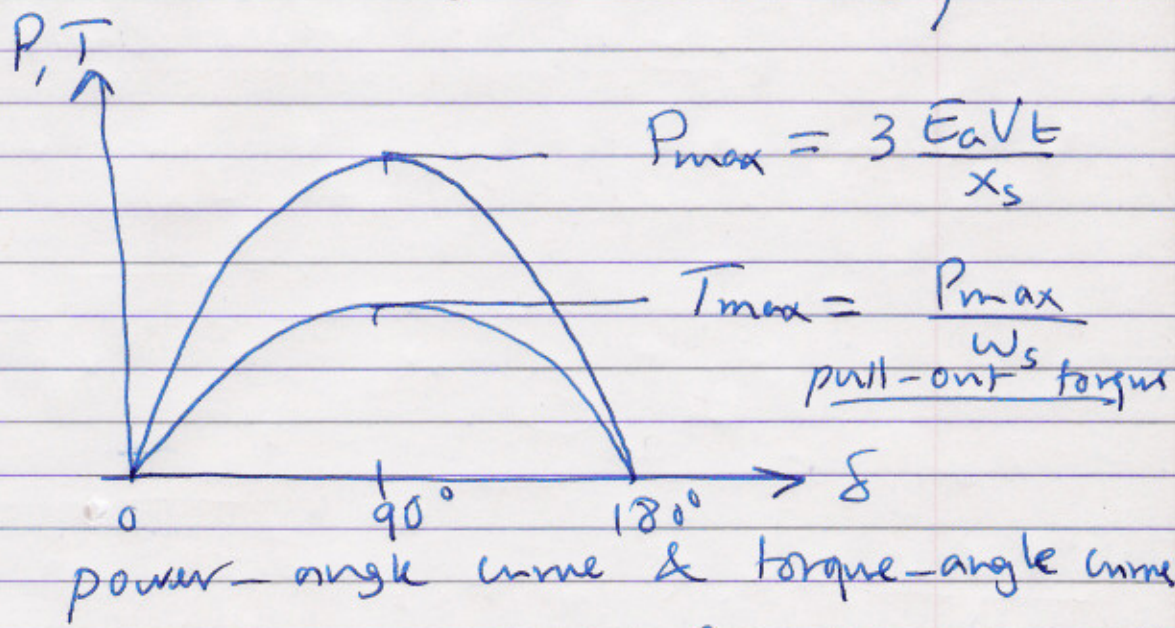
$$Q = 3 \left( \frac{E_a V_t}{X_s} \cos \delta - \frac{V_t^2}{X_s} \right)$$



$\omega_s$  - ~~synch~~ synch ~~sp~~ frequency in rad/s


$$\omega_s = \frac{n_s}{60} \cdot 2\pi \quad (n_s = \text{synch. speed in rpm})$$

observations:

- The max power & torque occurs when  $\delta = 90^\circ$ .
- if  $\delta > 90^\circ$ , the generator steps out of synchronism.




Salient-pole Machine:

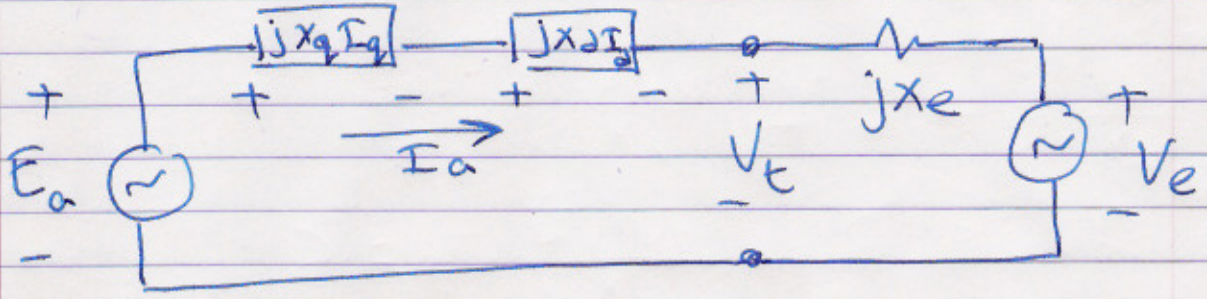

Equivalent circuit of salient-pole generator connected to external system.

Take the generated voltage as a reference,
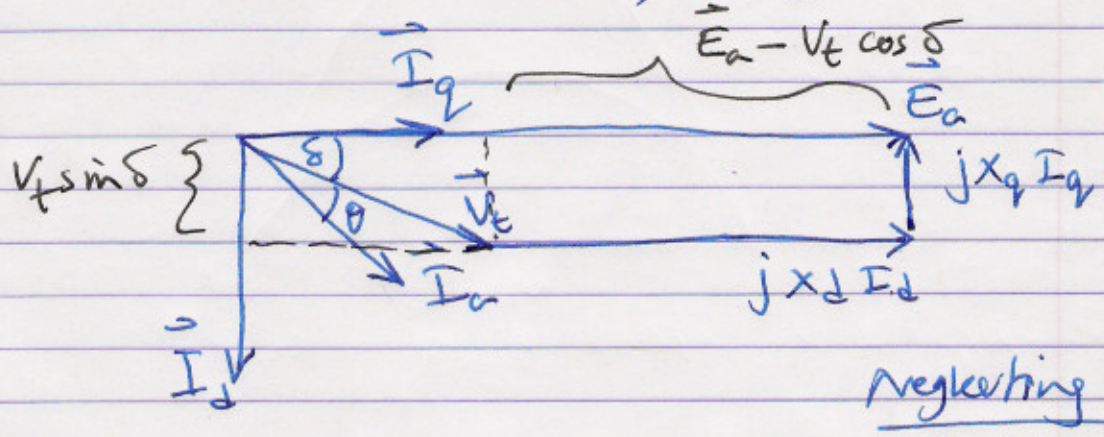
$$\vec{E}_a = E_a \angle 0^\circ, \quad \vec{V}_t = V_t \angle -\delta$$



using the above phasor diagram.

$$I_q = \frac{V_t \sin \delta}{X_q}, \quad I_d = \frac{E_a - V_t \cos \delta}{X_d}$$

$$\vec{S} = P + jQ = 3 \vec{V}_t \vec{I}_a^* \\ = 3 V_t \angle -\delta (I_q - j I_d)^*$$

remember, the current  $I_a$  is referred to  $\vec{E}_a$  in the above phasor diagram




$$\therefore P + jQ = 3V_t L^{-\delta} (I_q L^{0^\circ} + I_d L^{-90^\circ})$$

substitute for  $I_q$  &  $I_d$  and simplify,

$$\therefore P = 3 \left[ \frac{E_a V_t}{X_d} \sin \delta + \frac{V_t^2}{2} \left[ \frac{1}{X_q} - \frac{1}{X_d} \right] \sin 2\delta \right]$$
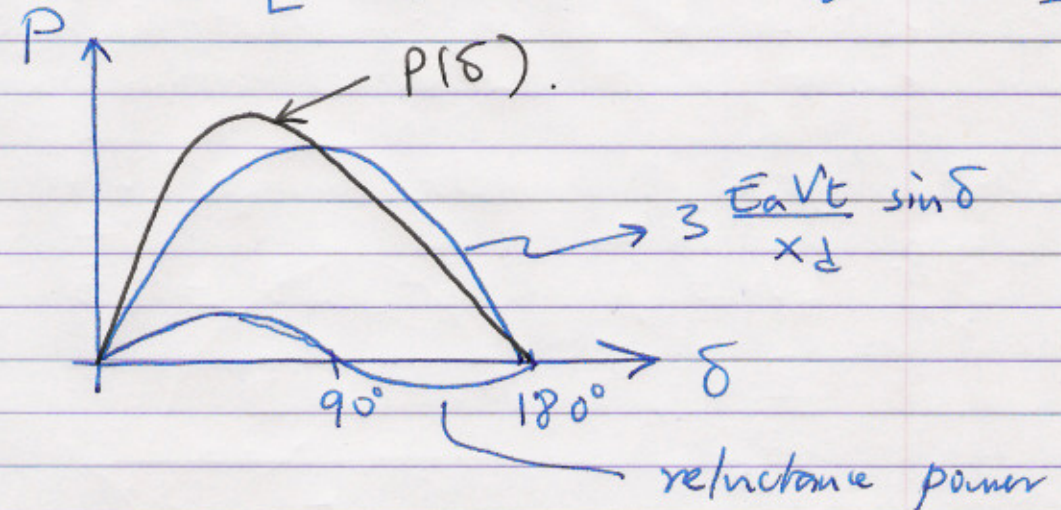
$$Q = 3 \left[ \frac{E_a V_t}{X_d} \cos \delta - V_t^2 \left( \frac{\sin^2 \delta}{X_q} + \frac{\cos^2 \delta}{X_d} \right) \right]$$



power-angle curve of a salient-pole synch generator.

Observations:

- The first term of  $P$  is identical to the power delivered by a round-type synch. M/C.
- The second term represents the effect of generator saliency, and it is called the reluctance power.
- In salient-pole m/c,  $X_d > X_q$ . When the salient-pole m/c approaches a round rotor, the values of  $X_d$  &  $X_q$  will both approach  $X_s \Rightarrow P$  &  $Q$  for salient m/c reduced to  $P$  &  $Q$  eqns of round type.