

Lecture Notes


ELE 7B

Ramadan El Shatshat


Single Phase circuit

Circuit Elements

- Sources

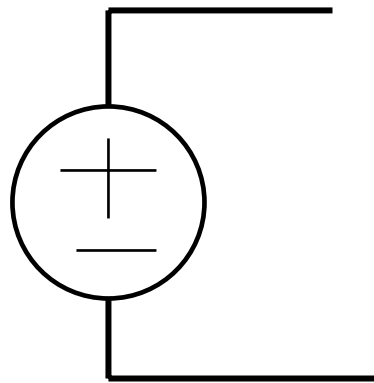

Voltage Source

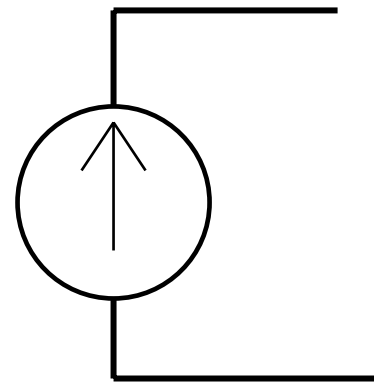


Current Source


- Sinks



Resistor

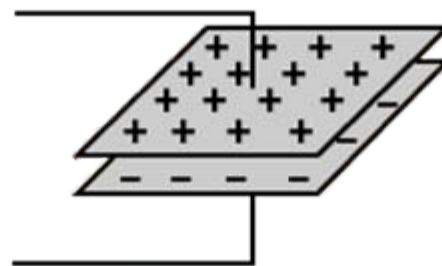


Capacitor

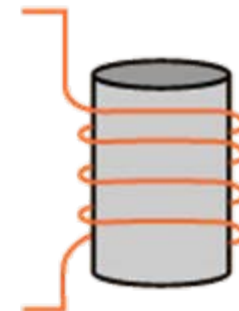


Inductor

Resistor Connections

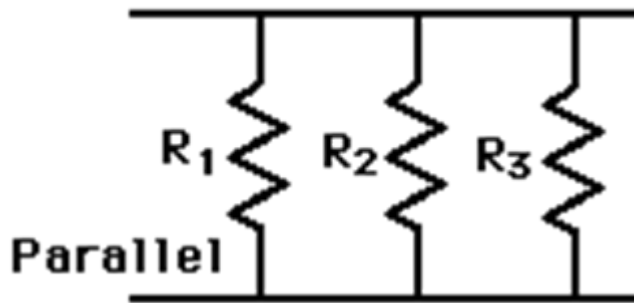
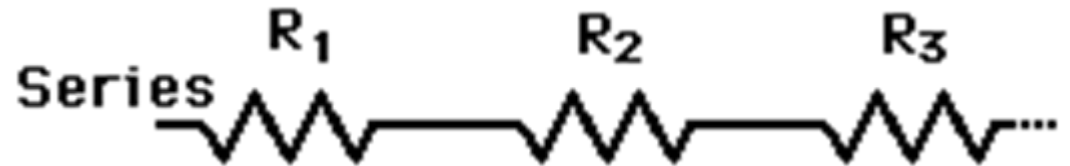
$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



$$R_{total} = R_1 + R_2 + R_3$$

Ohms Law

$$V = I * R$$

Where :

V = voltage

I= current


R = resistance

KCL

For any node in the circuit:

$$I_A = I_B + I_C + I_D$$

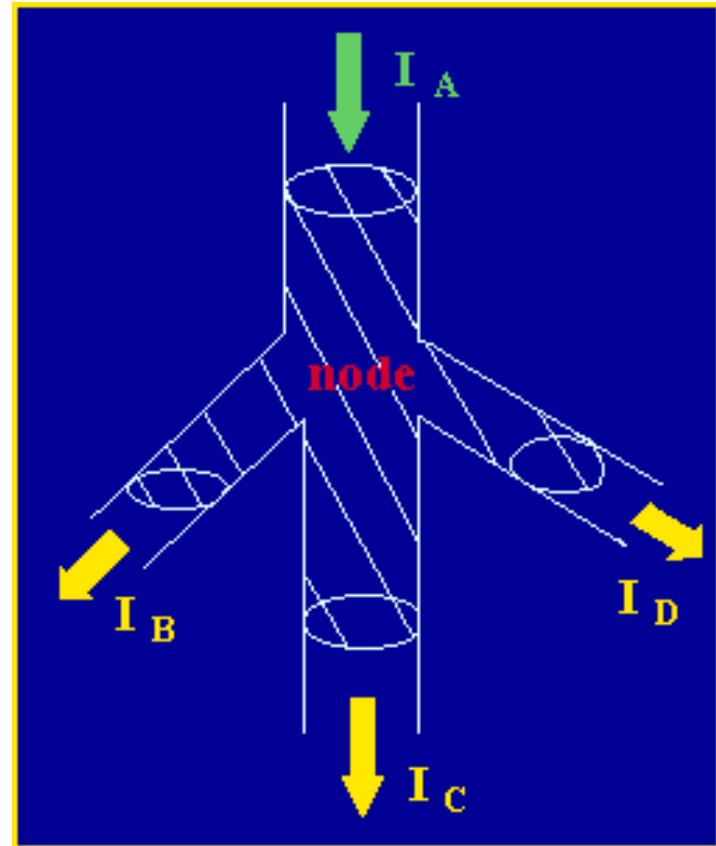The summation of currents entering a node is equal to the currents leaving a node.




KVL

For any closed loop:


$$\sum V = 0$$

The summation of voltages in any closed loop is equal to zero.

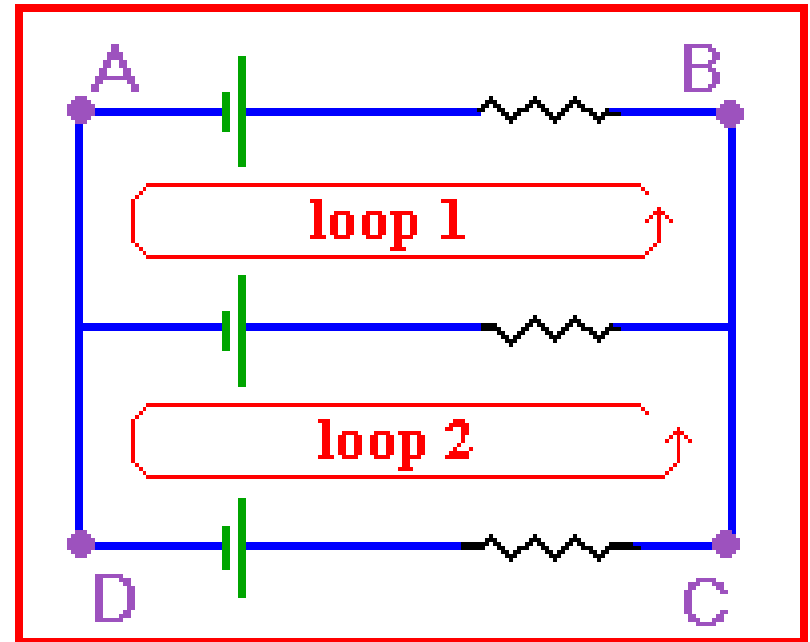


Example 1

- Find I_o (-0.25 mA)

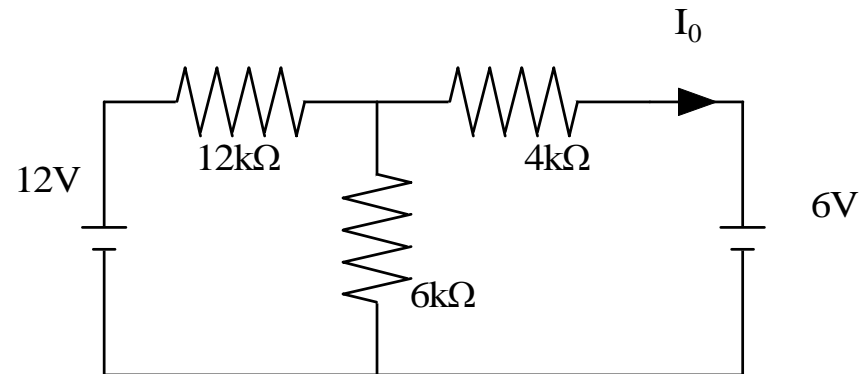

Example 2



- Find I_2 (1 A)

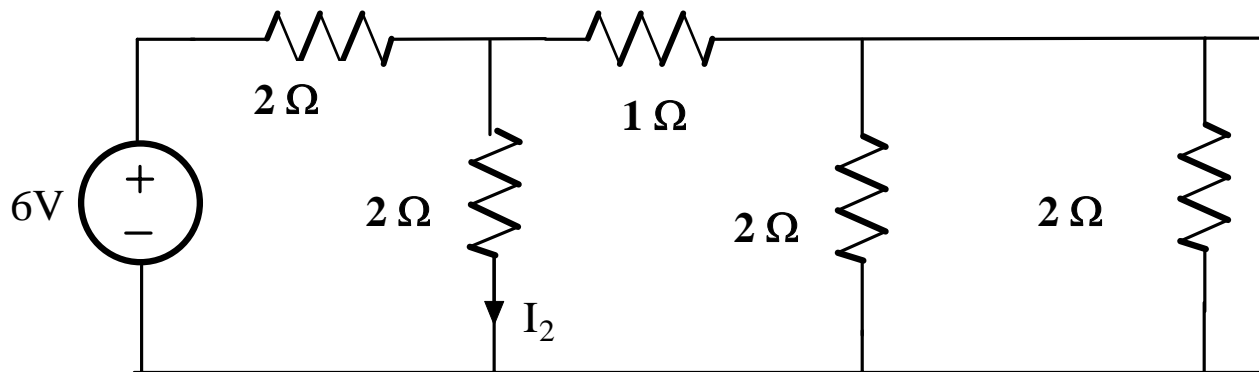

Single Phase Circuit (AC)

Review

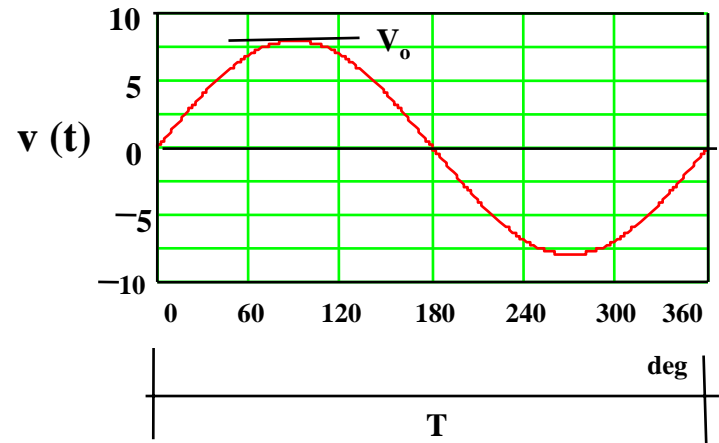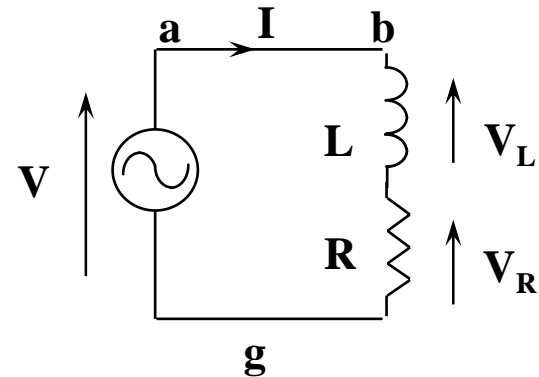- Single phase circuit components:
- Voltage or current sources.
- Impedances (resistance, inductance, and capacitance).
- The components are connected in series or in parallel.
- The figure shows a simple circuit where a voltage source (generator) supplies a load (resistance and inductance in series).



Single Phase Circuit (AC)

Review

- **The voltage source produces a sinusoidal voltage wave**

$$v(t) = \sqrt{2} V_{\text{rms}} \sin(\omega t)$$

where: V_{rms} is the rms value of the voltage (volts)

ω is the angular frequency of the sinusoidal function (rad/sec)

$$\omega = 2\pi f = \frac{2\pi}{T} \text{ rad/sec} \quad f = \frac{1}{T} \text{ Hz}$$

f is the frequency (60 Hz in USA, 50 Hz in Europe).

T is the time period (seconds).

Single Phase Circuit (AC)

Review

The RMS value is calculated by

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

For sinusoidal signal the RMS value =

$$V_{\text{rms}} = \frac{V_{\text{peak}}}{\sqrt{2}}$$

Unless it is stated in the question, all the given values are in RMS value.

Single Phase Circuit (AC)

Review

- **The current is also sinusoidal**

$$i(t) = \sqrt{2} I_{\text{rms}} \sin(\omega t - \phi)$$

where: I_{rms} is the rms value of the current.

ϕ is the phase-shift between current and voltage.

- **The RMS current is calculated by the Ohm's Law:**

where: Z is the impedance

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z}$$

Single Phase Circuit (AC)

Review

- The impedances (in Ohms) are :

- a) **Resistance (R)**

- b) **Inductive reactance** $X_L = \omega L$

- c) **Capacitive reactance** $X_C = \frac{1}{\omega C}$

Single Phase Circuit (AC)

Review


- **The impedance of a resistance and a reactance connected in series is :**

$$Z = \sqrt{R^2 + X^2}$$

- **The phase angle is :**

$$\phi = \tan^{-1} \frac{X}{R}$$

- Impedance calculation


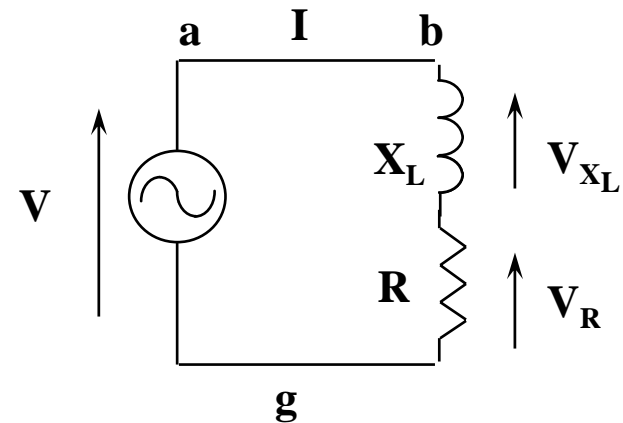


Single Phase Circuit (AC)

Review

Inductive circuit

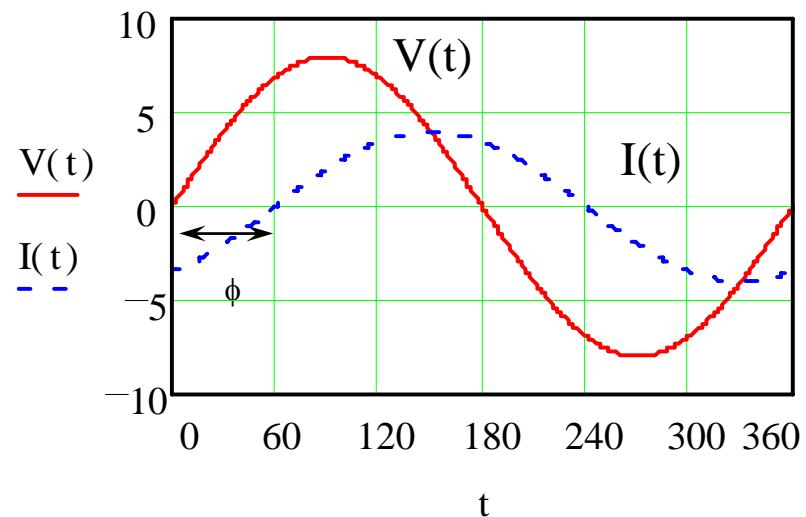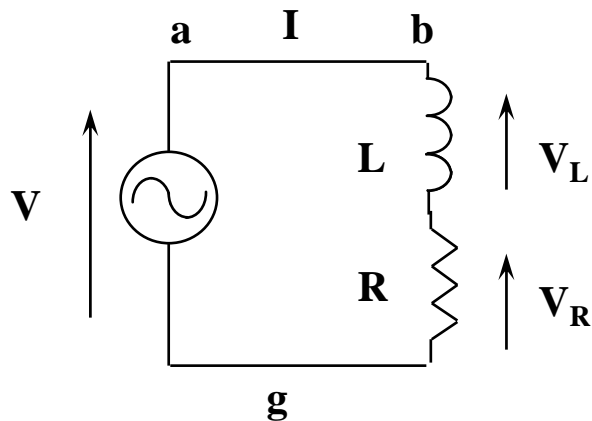- The ϕ phase-shift between the current and voltage is negative.
- The current is lagging with respect to the voltage.





Single Phase Circuit (AC)

Review

Capacitive circuit

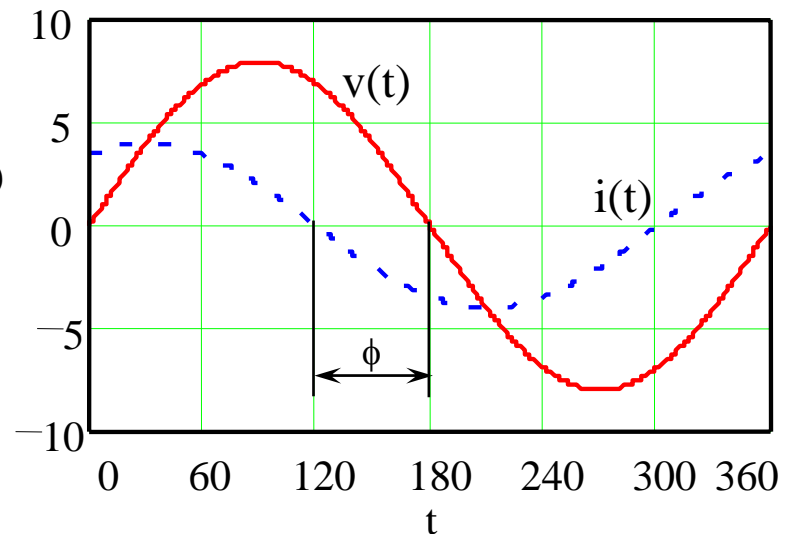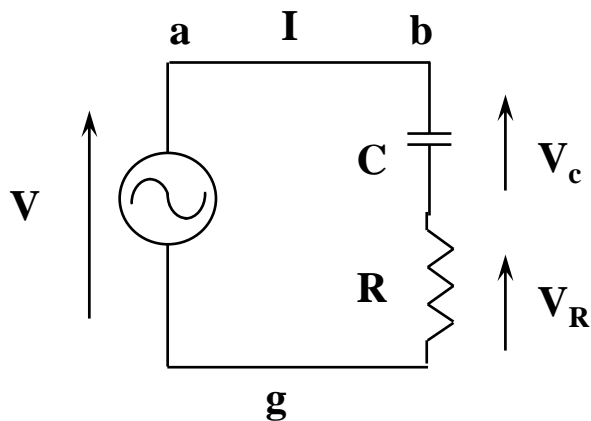- The ϕ phase shift between the current and voltage is positive.
- The current is leading with respect to the voltage.



Single Phase Circuit (AC)

Review

Complex Notation

- **Engineering calculations need the amplitude (rms value) and phase angle of voltage and current.**
- **The amplitude and phase angle can be calculated using complex notation.**
- **The voltage, current, and impedance are expressed by complex phasors.**

Single Phase Circuit (AC)

Review

Complex Notation

Impedance phasor: (resistance, capacitor, and inductance connected in series)


Rectangular form:

$$\mathbf{Z} = R + j\omega L + \left(\frac{1}{j\omega C}\right) = R + j(X_L - X_C) = R + jX_T$$

Polar form:

$$\mathbf{Z} = |\mathbf{Z}| \angle \phi$$

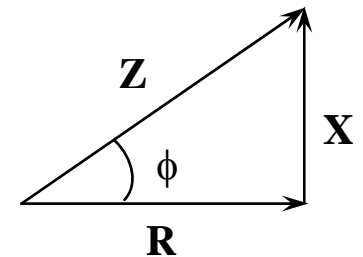where: $\mathbf{Z} = \sqrt{R^2 + X_T^2}$ $\phi = \tan^{-1} \left(\frac{X}{R}\right)$



$$R = \mathbf{Z} \cos (\phi) \qquad X = \mathbf{Z} \sin (\phi)$$

Single Phase Circuit (AC)

Review

Complex Notation

- Voltage phasor:

$$\mathbf{V} = |V| \angle \delta = |V| \cos \delta + \mathbf{j} |V| \sin \delta$$

where : V is the rms value, and δ is the phase angle

Note: The supply voltage phase angle is often selected as the reference with $\delta = 0$

Single Phase Circuit (AC)

Review

Complex Notation

- Current phasor


$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{|V| \angle \delta}{|Z| \angle \phi} = \left| \frac{V}{Z} \right| \angle (\delta - \phi) = \left| \frac{V}{Z} \right| [\cos (\delta - \phi) + j \sin (\delta - \phi)]$$

Single Phase Circuit (AC)

Review

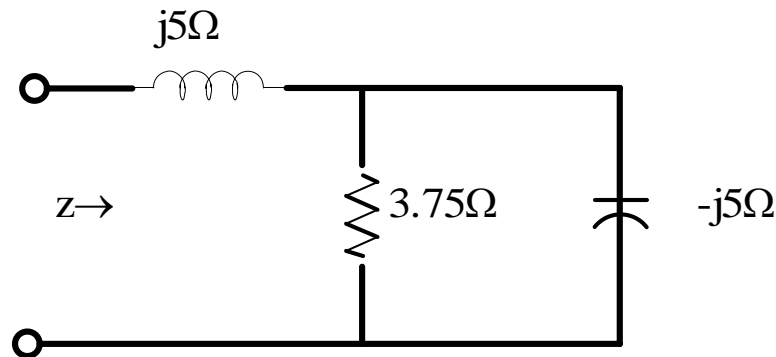Example 1:

$$Z = 5j + (-5j \parallel 3.75) = 5j + \frac{-18.75j}{3.75 - 5j} = 5j + \frac{18.74 \angle -90^\circ}{6.25 \angle -53.1^\circ} = 5j + 3 \angle -36.9^\circ = 2.4 + j3.2 = 4 \angle 53^\circ \Omega$$




Single Phase Circuit (AC)

Review

Example 2:

– Find V_0

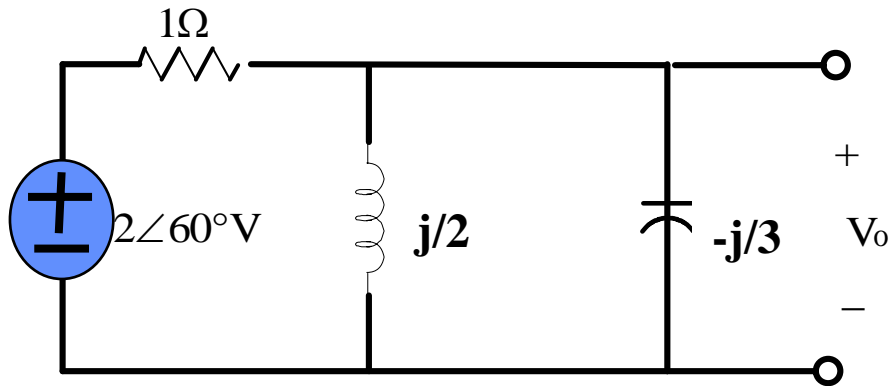

$$Z = \frac{j}{2} \parallel \frac{-j}{3} = \frac{1}{\frac{j}{2} - \frac{j}{3}} = -j$$

$$I = \frac{2\angle 60}{1-j} = \frac{2\angle 60}{\sqrt{2}\angle -45} = \sqrt{2}\angle 105$$

$$V_0 = I * Z = \sqrt{2}\angle 15$$

Single Phase Circuit (AC)

Review

Power calculation.

1) Instantaneous power

$$p(t) = v(t)i(t) = \sqrt{2} V \sin(\omega t) \sqrt{2} I \sin(\omega t - \phi)$$

2) Real Power (Average Power)

$$P = VI \cos(\phi)$$



Power factor

3) Reactive Power

$$Q = VI \sin(\phi)$$

Single Phase Circuit (AC)

Review

4) Complex Power

- The complex notation can be used for power calculation.
- The complex power is defined as : Voltage times the conjugate of the current.

$$S = V \bar{I} = V I [\cos (\phi) \pm j \sin (\phi)] = P \pm j Q$$

Positive for
Inductive load

Negative for
Capacitive load

Single Phase Circuit (AC)

Review

Example 3

A generator supplies a load through a feeder whose impedance is $Z_{\text{feeder}} = 1 + j2$. The load impedance is $Z_1 = 8 + j6$. The voltage across the load is 120 V.

Find the real power and reactive power supplied by the generator.

