

Lecture Notes

ELEC B7

Ramadan El Shatshat

Three Phase circuits

Three-phase Circuits



Advantages of Three-phase Circuits

- Smooth flow of power (instantaneous power is constant).
- Constant torque (reduced vibrations).
- The power delivery capacity tripled (increased by 200%) by increasing the number of conductors from 2 to 3 (increased by 50%).

Three-phase Circuits


Wye-Connected System

- The neutral point is grounded
- The three-phase voltages have equal magnitude.
- The phase-shift between the voltages is 120 degrees.

$$V_{an} = |V| \angle 0^\circ = V$$

$$V_{bn} = |V| \angle -120^\circ$$

$$V_{cn} = |V| \angle -240^\circ$$

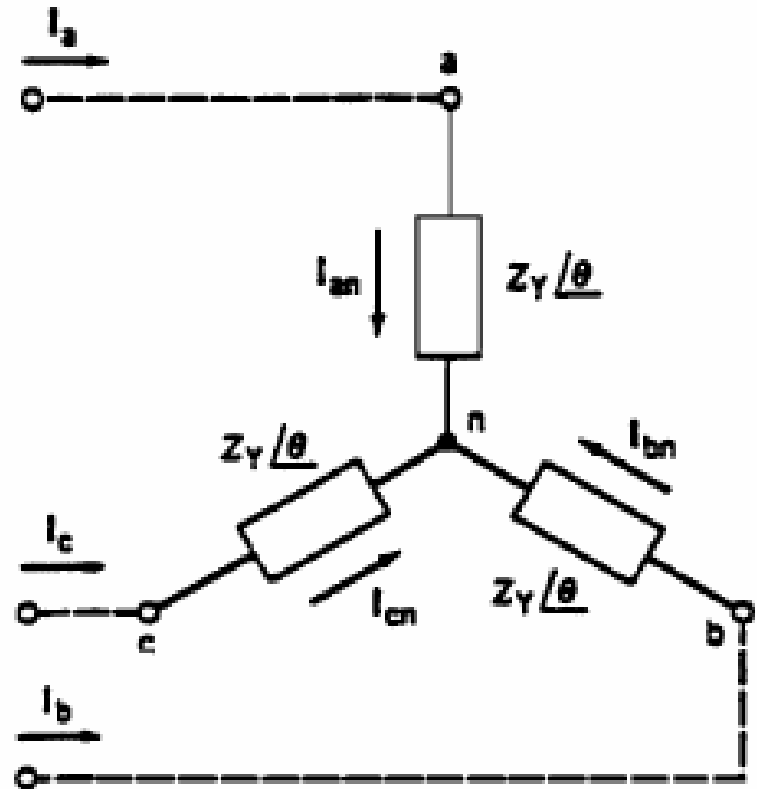

Three-phase Circuits


Wye-Connected System

- Line-to-line voltages are the difference of the phase voltages

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V \angle 30$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V \angle -90$$

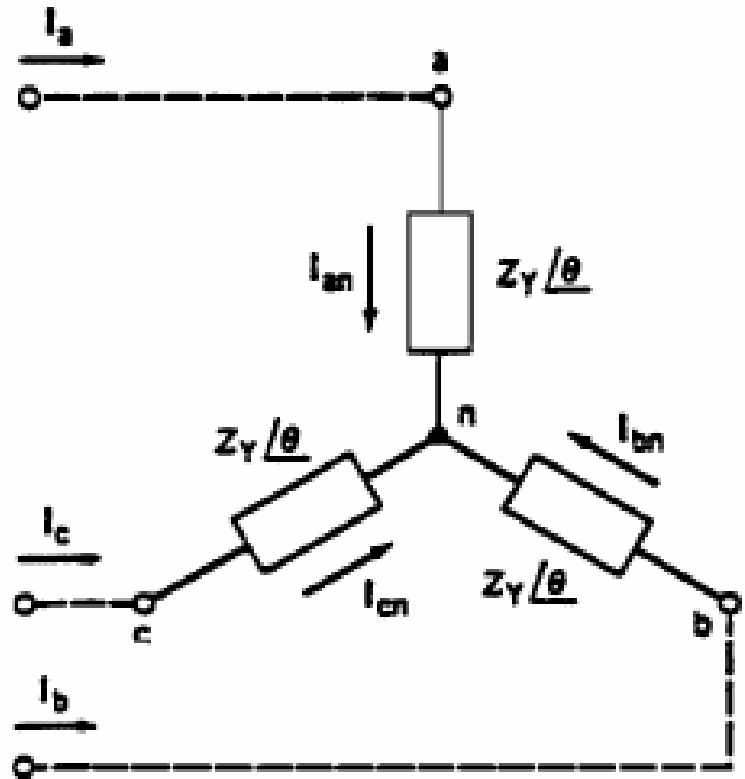
$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V \angle 150$$



Three-phase Circuits

Wye-Connected System

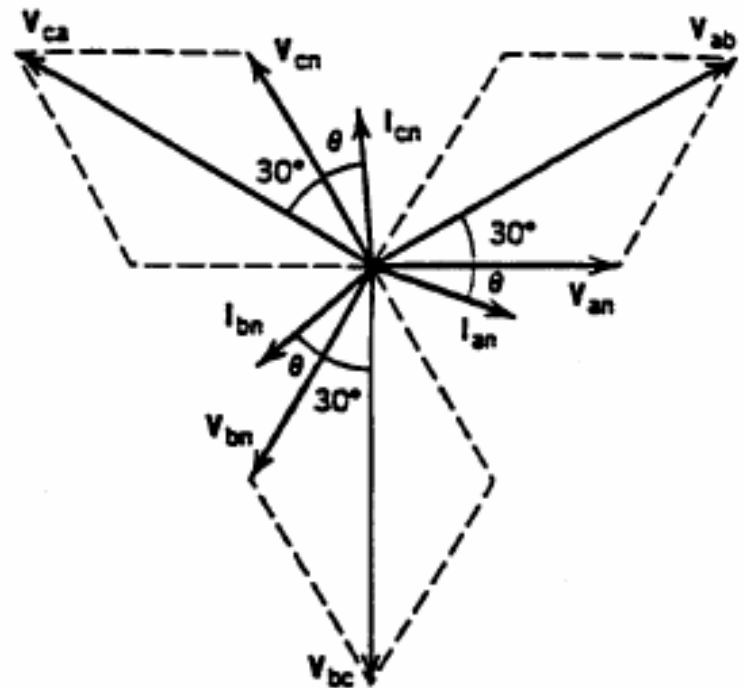- Phasor diagram is used to visualize the system voltages
- Wye system has two type of voltages: Line-to-neutral, and line-to-line.
- The line-to-neutral voltages are shifted with 120°
- The line-to-line voltage leads the line to neutral voltage with 30°
- The line-to-line voltage is $\sqrt{3}$ times the line-to-neutral voltage




Three-phase Circuits

Wye-Connected Loaded System

- The load is a balanced load and each one = Z
- Each phase voltage drives current through the load.
- The phase current expressions are:

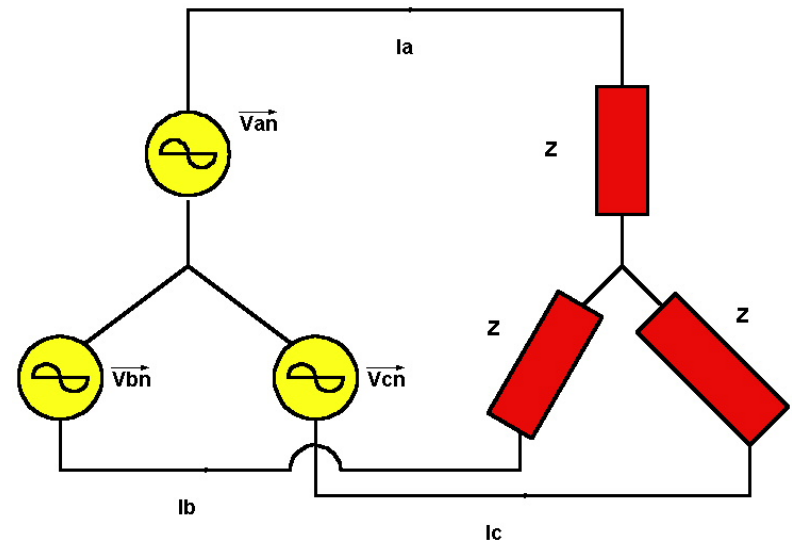
$$I_a = \frac{V_{an}}{Z}, \quad I_b = \frac{V_{bn}}{Z}, \quad I_c = \frac{V_{cn}}{Z}$$



Three-phase Circuits

Wye-Connected Loaded System

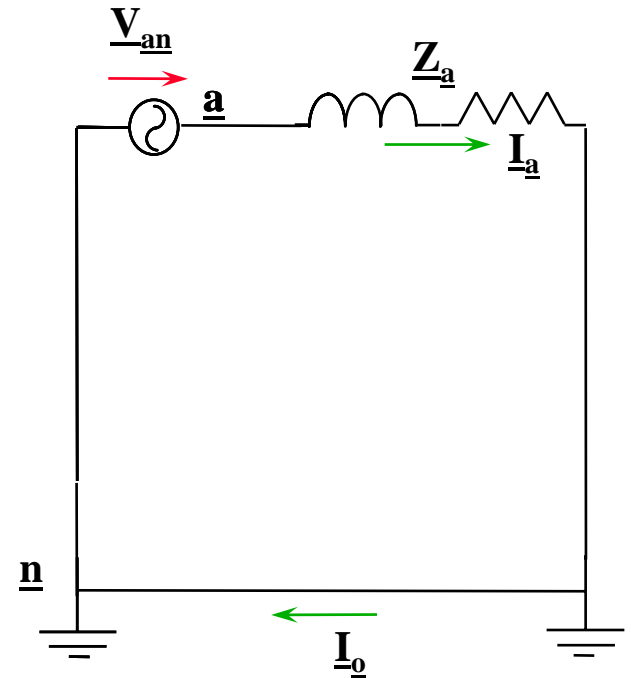
- Since the load is balanced ($Z_a = Z_b = Z_c$) then: Neutral current = 0
- This case single phase equivalent circuit can be used (phase a, for instance, only)
- Phase b and c are eliminated



Three-phase Circuits

Wye-Connected System with balanced load

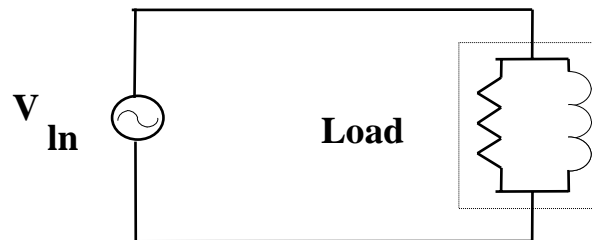- A single-phase equivalent circuit is used
- Only phase **a** is drawn, because the magnitude of currents and voltages are the same in each phase. Only the phase angles are different (-120° phase shift)
- The supply voltage is the line to neutral voltage.
- The single phase loads are connected to neutral or ground.




Three-phase Circuits

Balanced Delta-Connected System

- The system has only one voltage :
the line-to-line voltage (v_{LL})
- The system has two currents
 - line current
 - phase current
- The phase currents are:

$$I_a = \frac{V_{ab}}{Z}$$

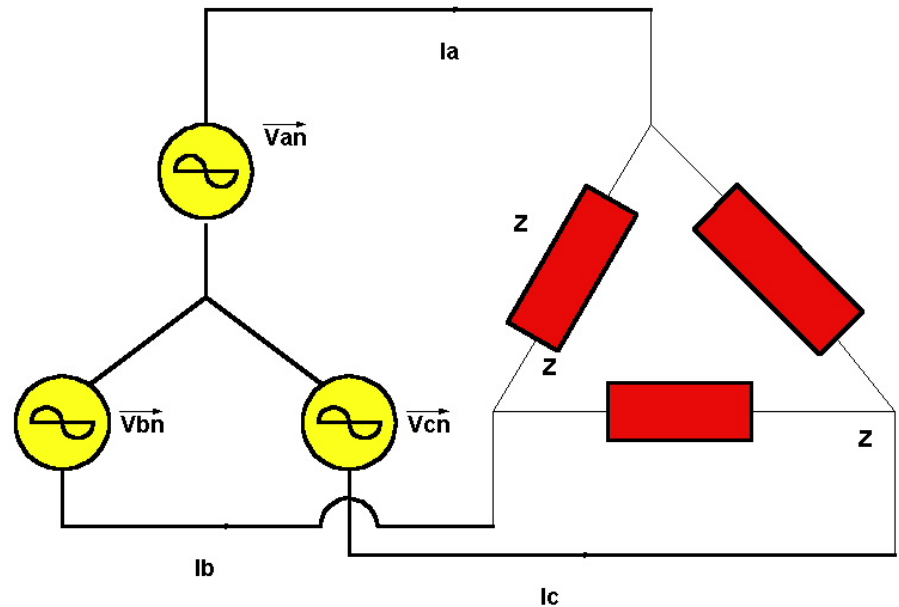

Three-phase Circuits

Delta-Connected System

The line currents are:


$$\mathbf{I}_a = \mathbf{I}_{ab} - \mathbf{I}_{ca}$$

$$\mathbf{I}_b = \mathbf{I}_{bc} - \mathbf{I}_{ab}$$

$$\mathbf{I}_c = \mathbf{I}_{ca} - \mathbf{I}_{bc}$$

- In a balanced case the line currents are:

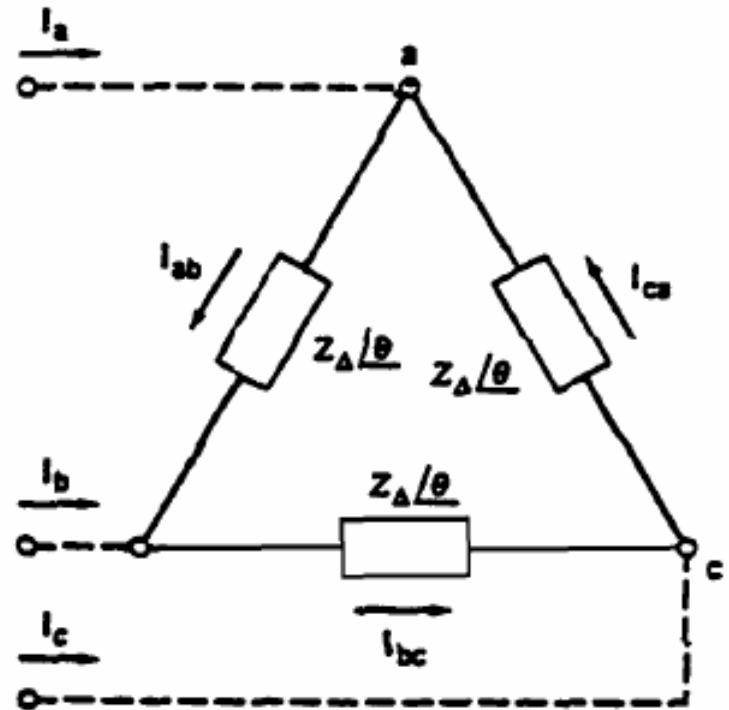
$$I_{line} = \sqrt{3}I_{phase} \angle -30$$



Three-phase Circuit

Delta-Connected System

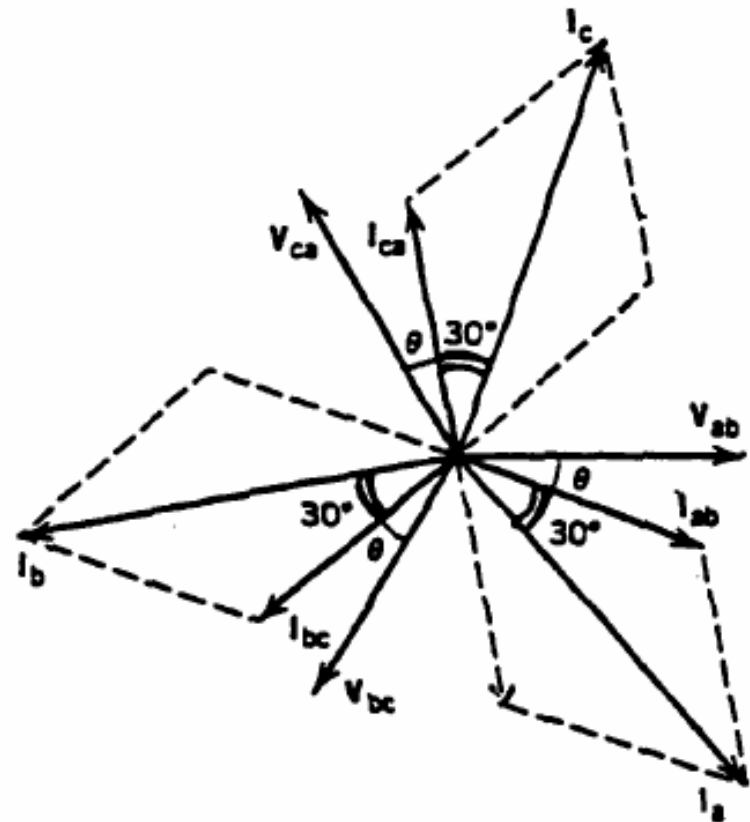- The phasor diagram is used to visualize the system currents
- **The system has two type of currents: line and phase currents.**
- **The delta system has only line-to-line voltages, that are shifted by**
- **The phase currents lead the line currents by 30°**
- **The line current is $\sqrt{3}$ times the phase current and shifted by 30 degree.**



Three-phase Circuit

- **Circuit conversions**

- A delta circuit can be converted to an equivalent wye circuit. The equation for phase a is:

$$\mathbf{Z}_a = \frac{\mathbf{Z}_{ab} \mathbf{Z}_{ca}}{\mathbf{Z}_{ab} + \mathbf{Z}_{bc} + \mathbf{Z}_{ca}}$$

- Conversion equation for a balanced system is:

$$\mathbf{Z}_a = \frac{\mathbf{Z}_{ab}}{3}$$

Three-phase Circuit

Power Calculation

- The three phase power is equal the sum of the phase powers

$$\mathbf{P} = \mathbf{P}_a + \mathbf{P}_b + \mathbf{P}_c$$

- If the load is balanced:

$$\mathbf{P} = 3 \mathbf{P}_{\text{phase}} = 3 \mathbf{V}_{\text{phase}} \mathbf{I}_{\text{phase}} \cos(\phi)$$

- Wye system: $\mathbf{V}_{\text{phase}} = \mathbf{V}_{\text{LN}}$ $\mathbf{I}_{\text{phase}} = \mathbf{I}_L$ $\mathbf{V}_{\text{LL}} = \sqrt{3} \mathbf{V}_{\text{LN}}$

$$\mathbf{P} = 3 \mathbf{V}_{\text{phase}} \mathbf{I}_{\text{phase}} \cos(\phi) = \sqrt{3} \mathbf{V}_{\text{LL}} \mathbf{I}_L \cos(\phi)$$

- Delta system: $\mathbf{I}_{\text{Line}} = \sqrt{3} \mathbf{I}_{\text{phase}}$ $\mathbf{V}_{\text{LL}} = \mathbf{V}_{\text{phase}}$

$$\mathbf{P} = 3 \mathbf{V}_{\text{phase}} \mathbf{I}_{\text{phase}} \cos(\phi) = \sqrt{3} \mathbf{V}_{\text{LL}} \mathbf{I}_L \cos(\phi)$$