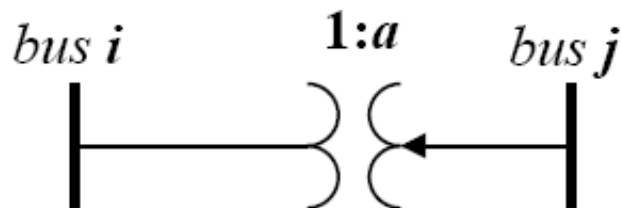


# ELE-B7 Power Systems Engineering

## Tap-Changing Transformers Modeling

# Tap-Changing Transformers


- The tap-changing transform gives some control of the power network by changing the voltages and current magnitudes and angles by small amounts
  - ◆ The flow of real power along a network branch is controlled by the angular difference of the terminal voltages
  - ◆ The flow of reactive power along a network branch is controlled by the magnitude difference of the terminal voltages
  - ◆ Real and reactive powers can be adjusted by voltage-regulating transformers and by phase-shifting transformers



$a$  can be a complex number
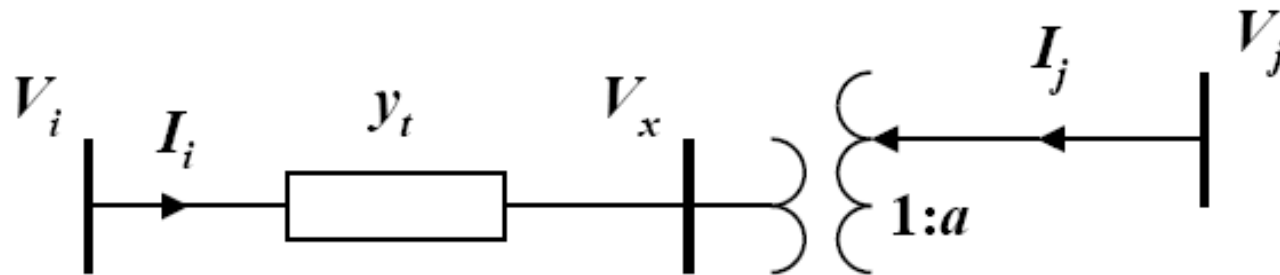
# Modeling of Tap-Changers

- ◆ the off-nominal tap ratio is given as  $1:a$
- ◆ the nominal turns-ratio ( $N_1/N_2$ ) was addressed with the conversion of the network to per unit
- ◆ the transformer is modeled as two elements joined together at a fictitious bus  $x$



- ◆ basic circuit equations:

$$V_x = \frac{1}{a} V_j \quad I_i = -a^* \cdot I_j \quad I_i = y_t (V_i - V_x)$$

# Modeling of Tap-Changers, cont'd

- Making substitutions

$$V_x = \frac{1}{a} V_j \quad I_i = y_t (V_i - V_x)$$

$$I_i = y_t \left( V_i - \frac{1}{a} V_j \right)$$

$$I_i = -a^* \cdot I_j$$

$$I_j = -\frac{1}{a^*} I_i$$

$$I_j = -\frac{y_t}{a^*} \left( V_i - \frac{1}{a} V_j \right) = -\frac{y_t}{a^*} V_i + \frac{y_t}{|a|^2} V_j$$

# YBus Formation of Tap-Changers

- **Matrix formation**

$$I_i = \{y_t\}V_i + \left\{-\frac{y_t}{a}\right\}V_j$$

$$I_j = \left\{-\frac{y_t}{a^*}\right\}V_i + \left\{\frac{y_t}{|a|^2}\right\}V_j$$

$$\begin{bmatrix} I_i \\ I_j \end{bmatrix} = \begin{bmatrix} y_t & -y_t/a \\ -y_t/a^* & y_t/|a|^2 \end{bmatrix} \cdot \begin{bmatrix} V_i \\ V_j \end{bmatrix}$$

# Pi-Circuit Model of Tap-Changers

- Valid for real values of  $a$
- Taking the  $y$ -bus formation, break the diagonal elements into two components
  - ◆ the off-diagonal element represent the impedance across the two buses
  - ◆ the remainder form the shunt element

